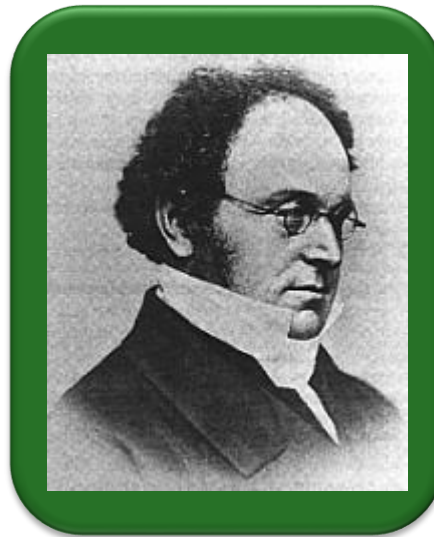


Binary Logic → continue

DeMorgan Theorems

Augustus DeMorgan (1806-1871)



British mathematician born in India

DeMorgan's theorems

- $\overline{x+y} = \overline{x} \bullet \overline{y}$

- $\overline{x \bullet y} = \overline{x} + \overline{y}$

- breaking the bar changes the logic operation (**OR**) under the **bar**
- breaking the bar changes the logic operation (**AND**) under the **bar**

Proof of the DeMorgan's theorem

Proof of the DeMorgan's theorem


x	y	\overline{x}	\overline{y}	$x y$	$\overline{x y}$	$\overline{x+y}$	$\overline{x} \overline{y}$	$x + y$	$\overline{x + y}$
0	0								
0	1								
1	0								
1	1								

Proof of the DeMorgan's theorem

x	y	\overline{x}	\overline{y}	xy	\overline{xy}	$\overline{x+y}$	$\overline{x} \overline{y}$	$x + y$	$\overline{x + y}$
0	0	1	1	0					
0	1	1	0	0					
1	0	0	1	0					
1	1	0	0	1					


Proof of the first DeMorgan's theorem

x	y	\overline{x}	\overline{y}	$x y$	$\overline{x y}$	$\overline{x+y}$	$\overline{x} \overline{y}$	$x + y$	$\overline{x + y}$
0	0	1	1	0	1	1			
0	1	1	0	0	1	1			
1	0	0	1	0	1	1			
1	1	0	0	1	0	0			

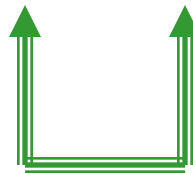

Proof of both DeMorgan's theorems

x	y	\overline{x}	\overline{y}	$x y$	$\overline{x y}$	$\overline{x+y}$	$\overline{x} \overline{y}$	$x + y$	$\overline{x + y}$
0	0	1	1	0	1	1	1	0	1
0	1	1	0	0	1	1	0	1	0
1	0	0	1	0	1	1	0	1	0
1	1	0	0	1	0	0	0	1	0

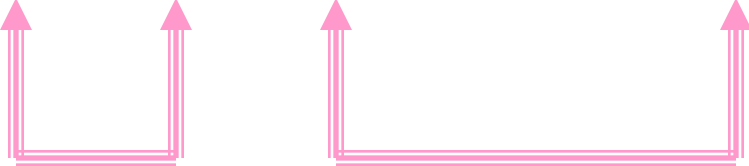

Perfect Induction

Example: Using DeMorgan's

$$\overline{A \overline{B} + C}$$

First application of the theorem

$$\overline{A \overline{B} + C} = \boxed{\overline{A \overline{B}} \quad \overline{C}}$$

Second application of theorem

$$\begin{aligned}\overline{A \overline{B} + C} &= \overline{A \overline{B}} \overline{C} \\ &= (\overline{A} + \overline{\overline{B}}) \overline{C}\end{aligned}$$

Distribute...

$$\begin{aligned}\overline{A \overline{B} + C} &= \overline{A \overline{B}} \overline{C} \\ &= (\overline{A} + \overline{\overline{B}}) \overline{C} \\ &= (\overline{A} + B) \overline{C} \\ &= \overline{A} \overline{C} + B \overline{C}\end{aligned}$$

Sum-of-products form


$$\begin{aligned}\overline{A \overline{B} + C} &= \overline{A \overline{B}} \overline{C} \\ &= (\overline{A} + \overline{\overline{B}}) \overline{C} \\ &= (\overline{A} + B) \overline{C} \\ &= \overline{A} \overline{C} + B \overline{C}\end{aligned}$$




Implement with gates

Sum-of-Products form

Ready to see the circuit?

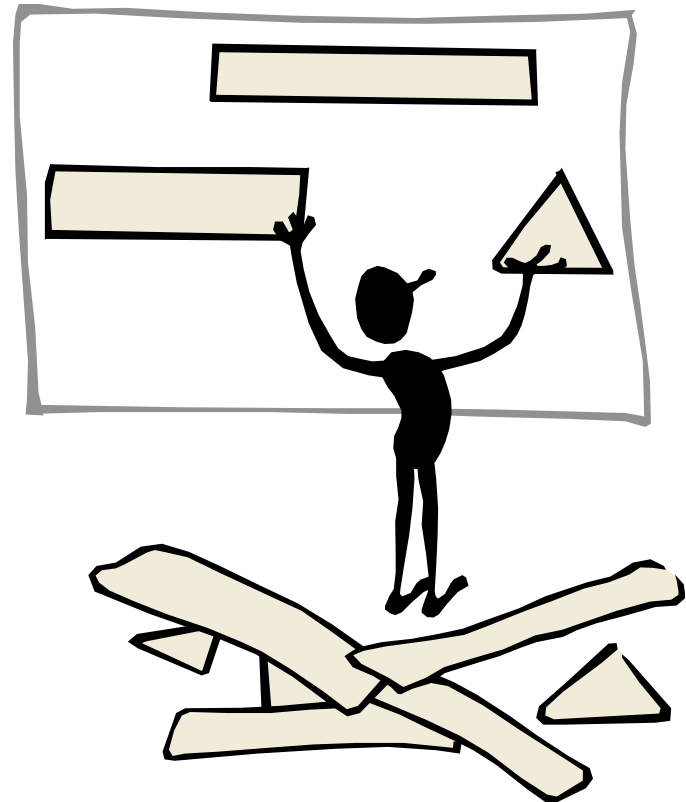


The SOP leads to “two-level-realization”

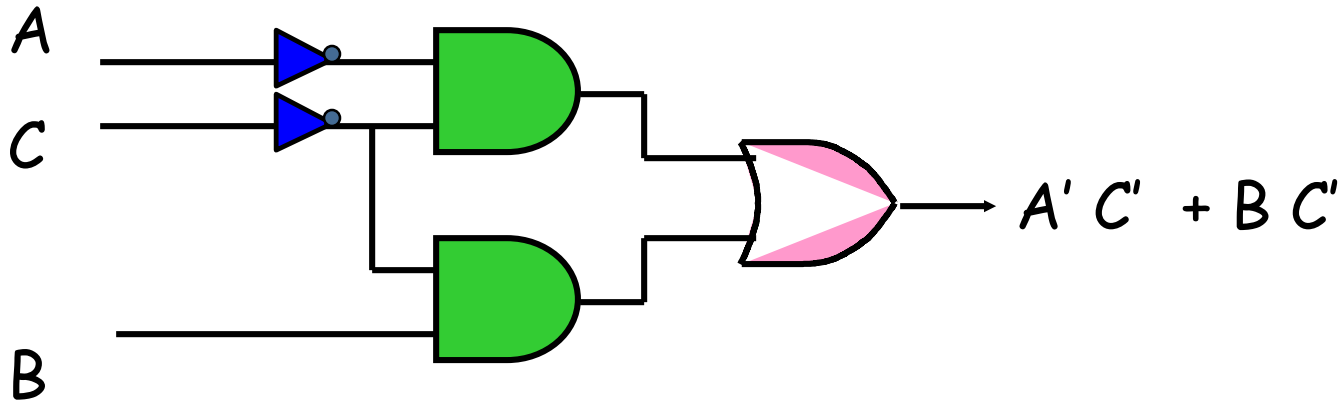


factor ... “multi-level-realization”

$$A' C' + B C' = C'(A' + B)$$

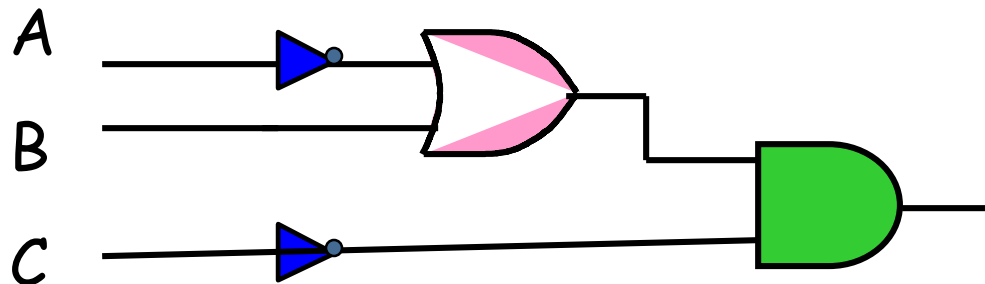

Fun-in & Fan-out

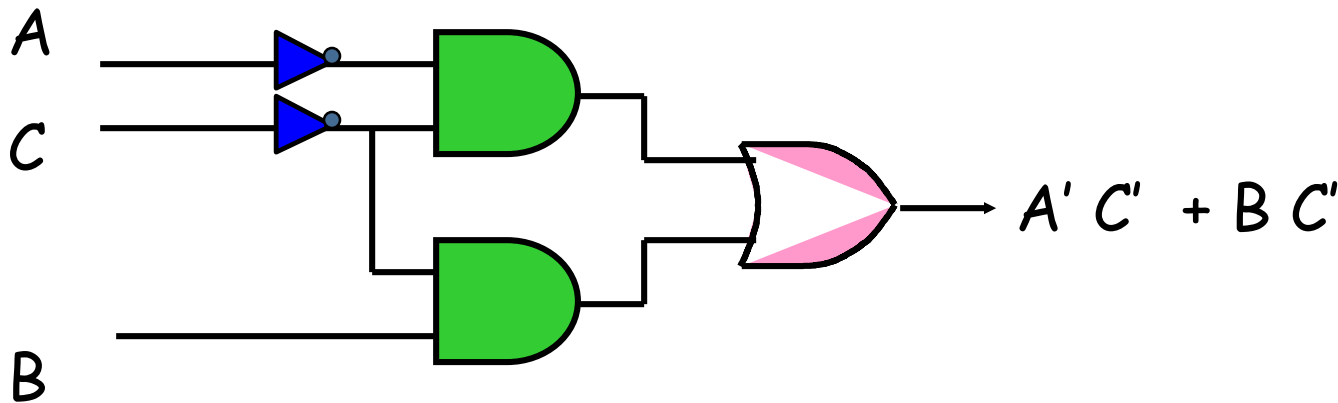

Fan-in: max number of inputs a gate can accept

Fan-out: max number of inputs a gate can drive

More gates....

More Gates

- NOR (Not OR)
- NAND (Not AND)

OR

A	B	OR	NOR
0	0	0	
0	1	1	
1	0	1	
1	1	1	




NOR

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0




NOR

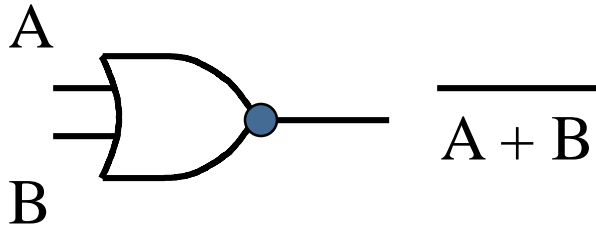


Using
DeMorgan's
theorem

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

NOR

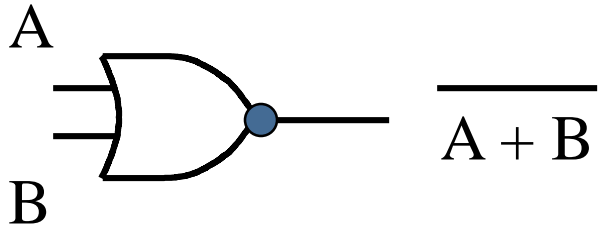

Using
DeMorgan's
theorem

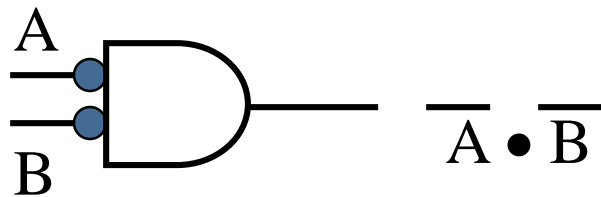

$$\overline{A} \bullet \overline{B} = \overline{A + B}$$

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

AND ... Not AND

A	B	AND	NAND
0	0	0	
0	1	0	
1	0	0	
1	1	1	




NAND

A	B	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0




NAND

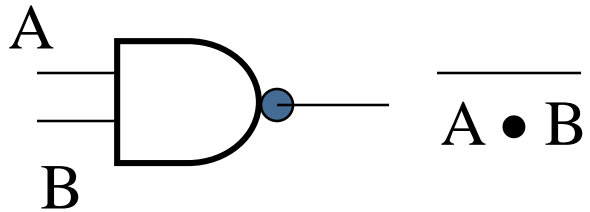


Using DeMorgan's
theorem

A	B	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

NAND

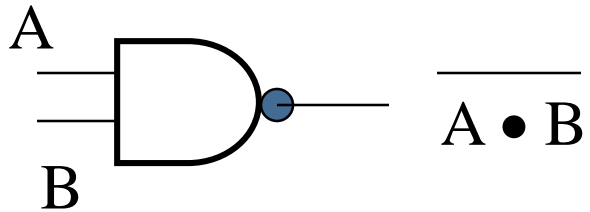



Using DeMorgan's
theorem

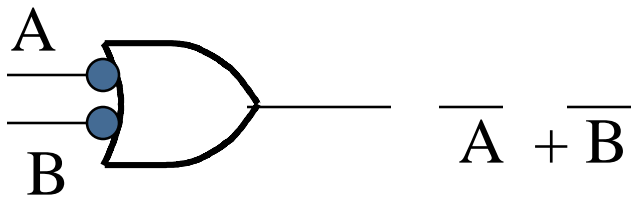

$$\overline{A \bullet B} = \overline{A} + \overline{B}$$

A	B	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

NAND: CMOS and gate layout

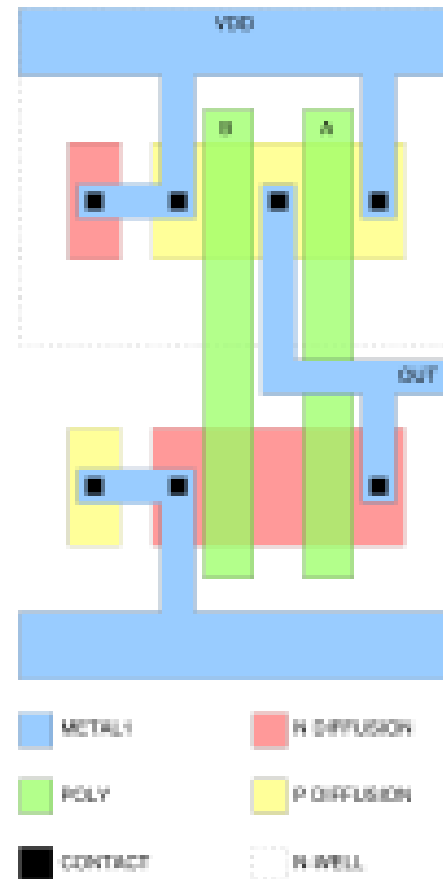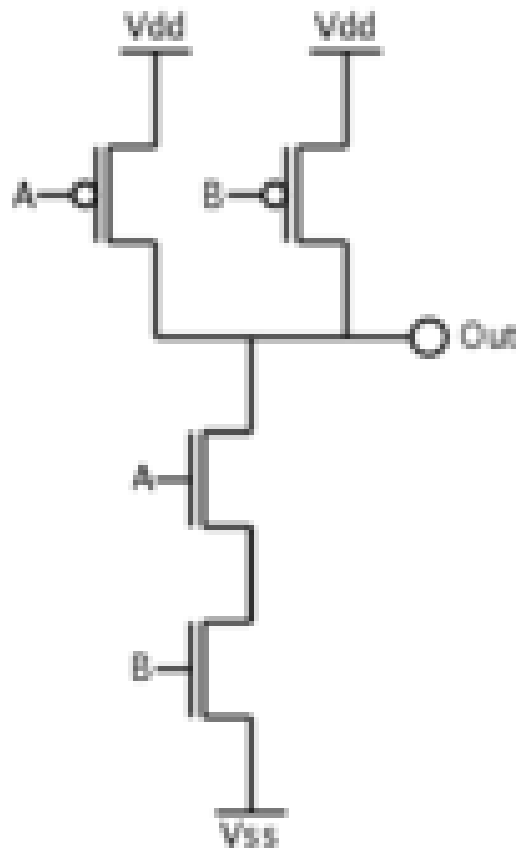

Universality of NAND and NOR Gates

...can implement any Boolean expression

Universality of NAND: NOT



Proof



A	AND	NAND
0	0	1

Proof




A	AND	NAND
0	0	1
1	1	0

Proof




A	AND	NAND
0	0	1
1	1	0



Universality of NAND: AND

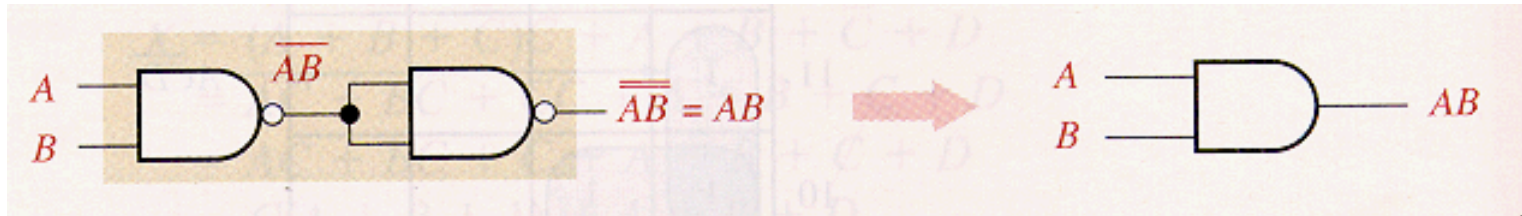


Universality of NAND: OR

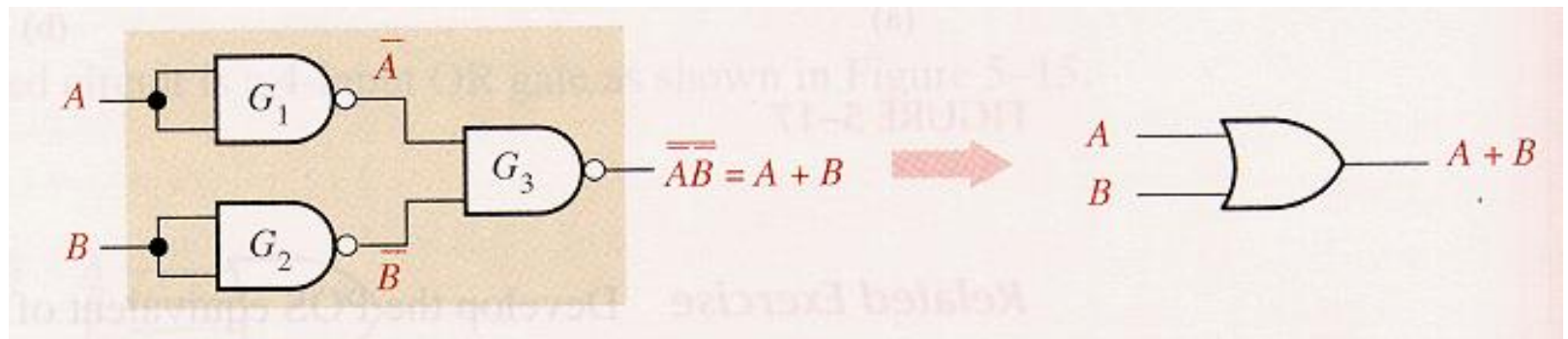


All

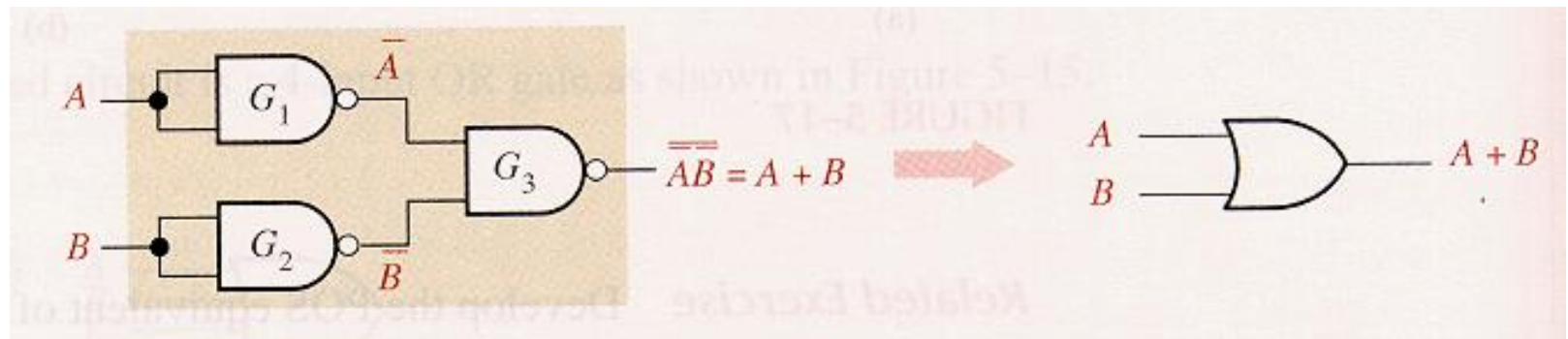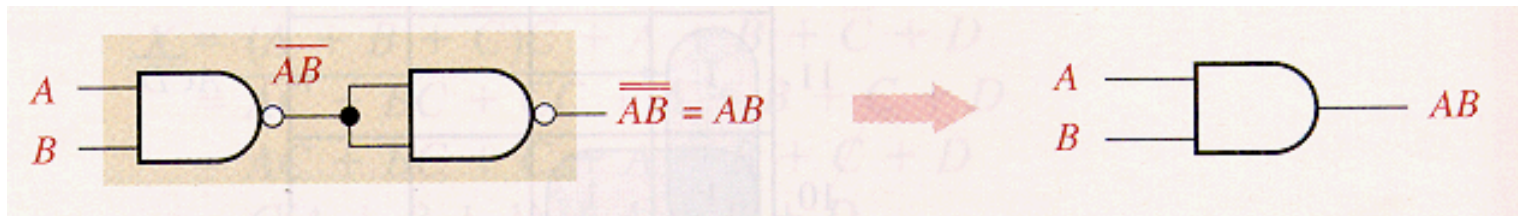


Universality of NOR: NOT

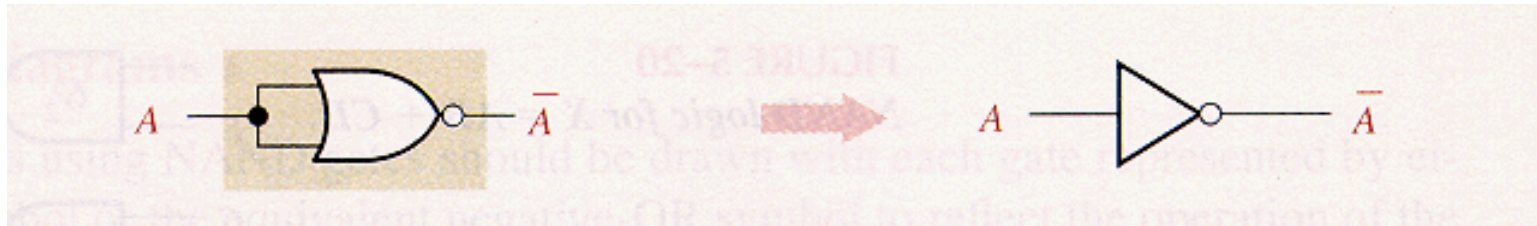

Universality of NOR: OR

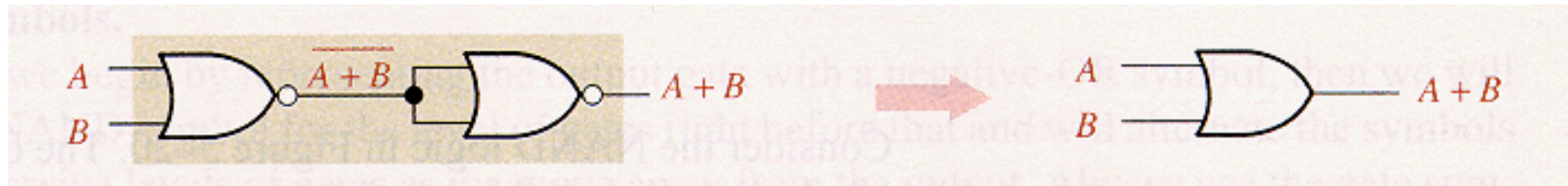

Universality of NOR: AND

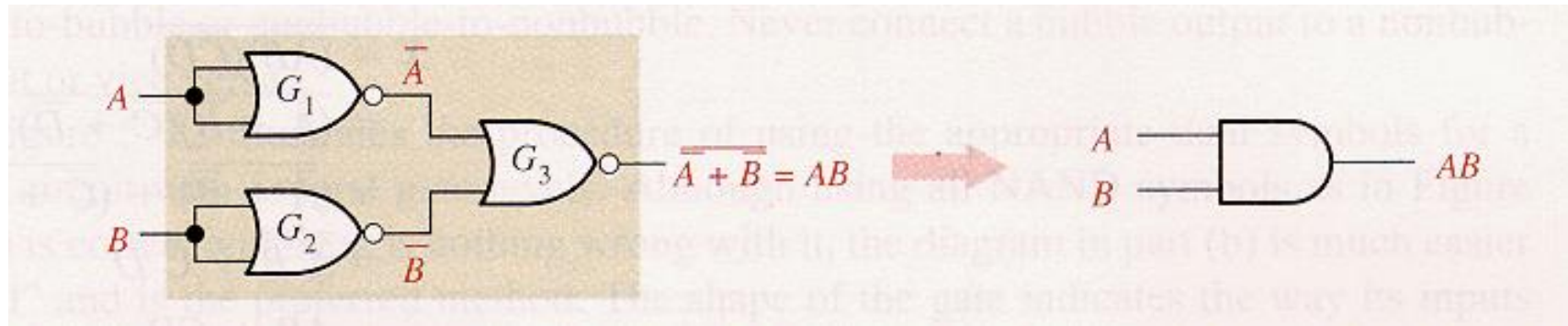


Example: implement (two-level-realization) the Boolean function: $X = AB + CD$, using:


1. AND, OR, NOR gates
2. NAND gates

You have ...5 minutes ...

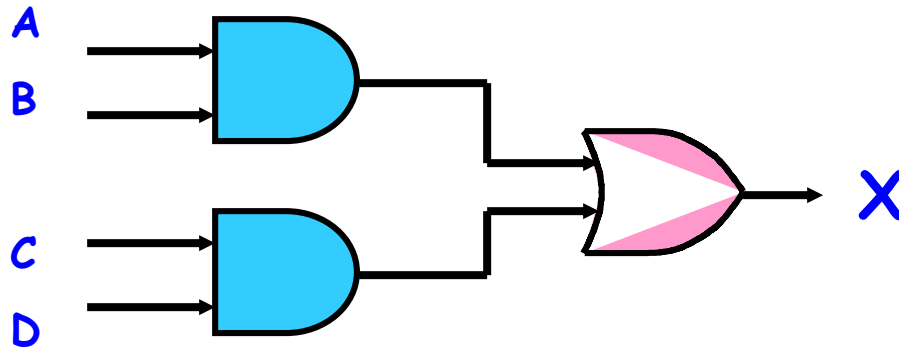
1) $X = AB + CD$; Using AND, OR, NOT gates



$X = AB + CD$; Using Chips

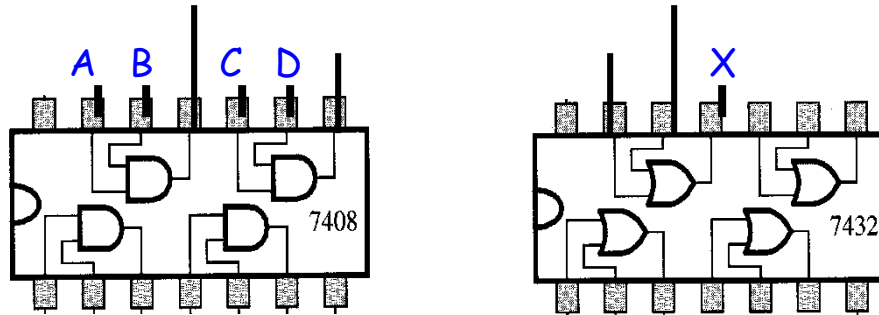

$X = AB + CD$; Using Chips

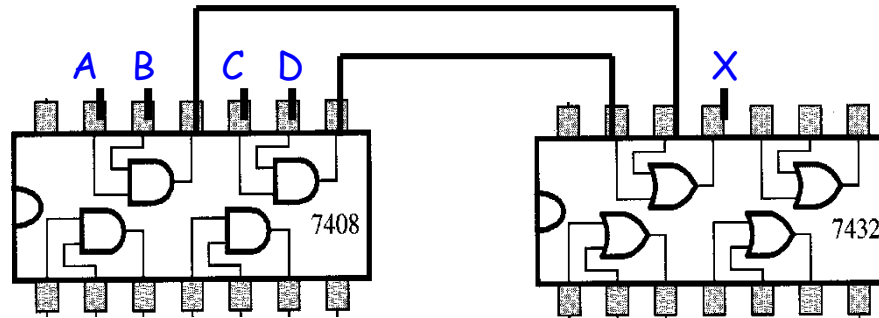

$X = AB + CD$; Using NAND gates


A

B


C

D


$X = AB + CD$; Using NAND gates

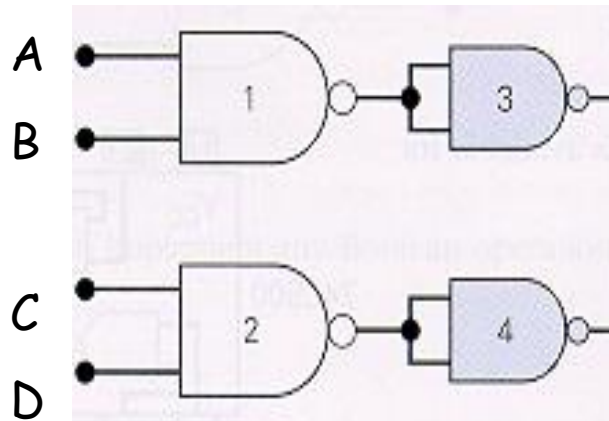


$X = AB + CD$; Using NAND gates

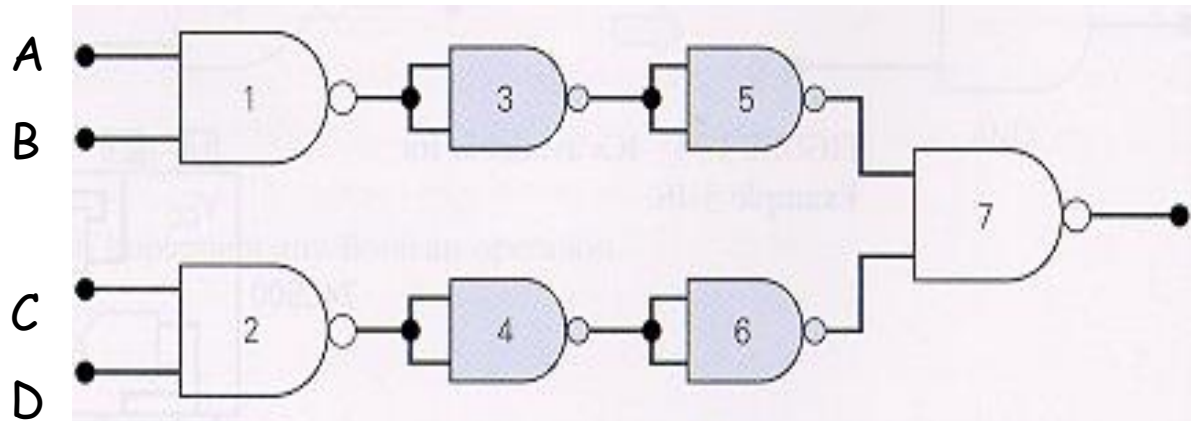


Two inverters cancel each other

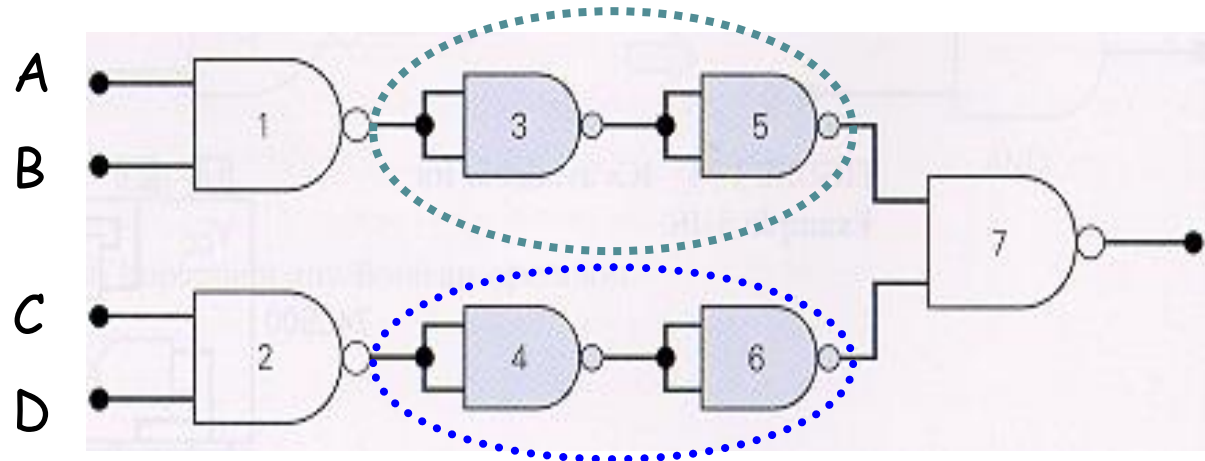

$X = AB + CD$; Using NAND gates

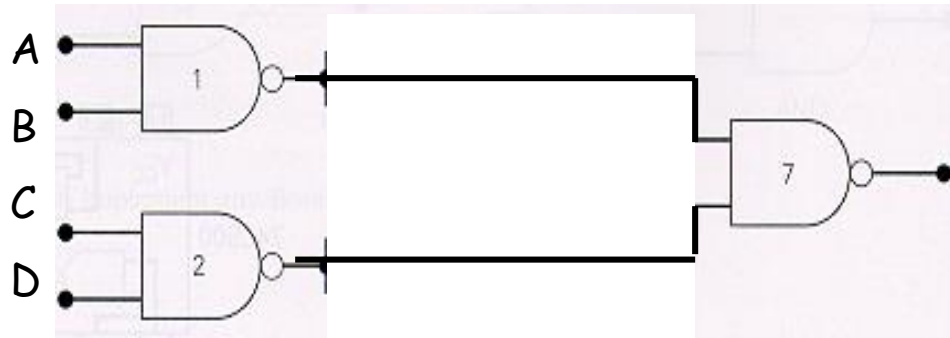


$$X = AB + CD$$

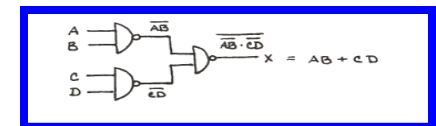


Note: 2 inverts in series cancel each other


$X = AB + CD$; Using NAND chips

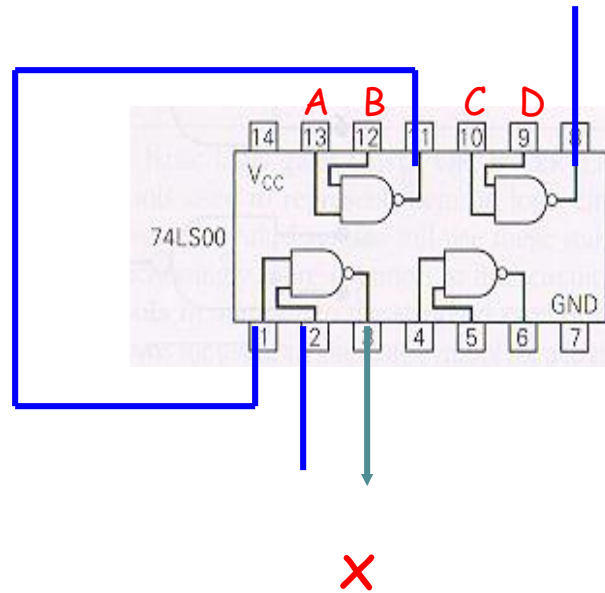


$X = AB + CD$; Using NAND chips

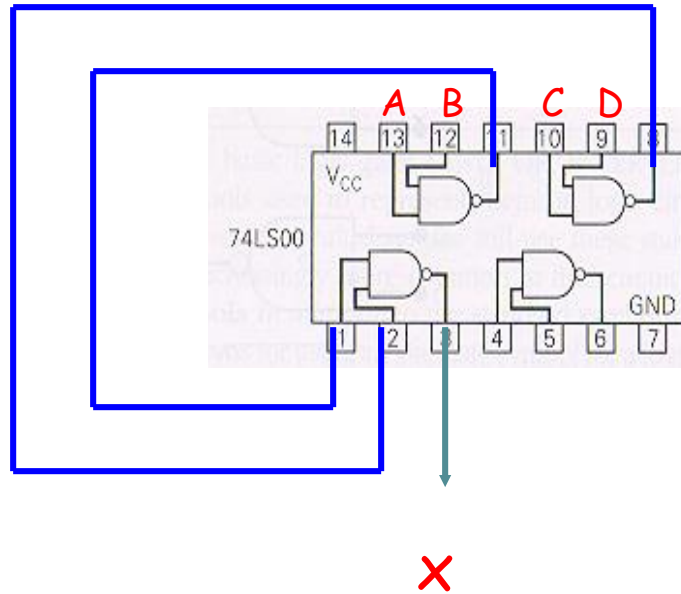

$X = AB + CD$; Using VHDL

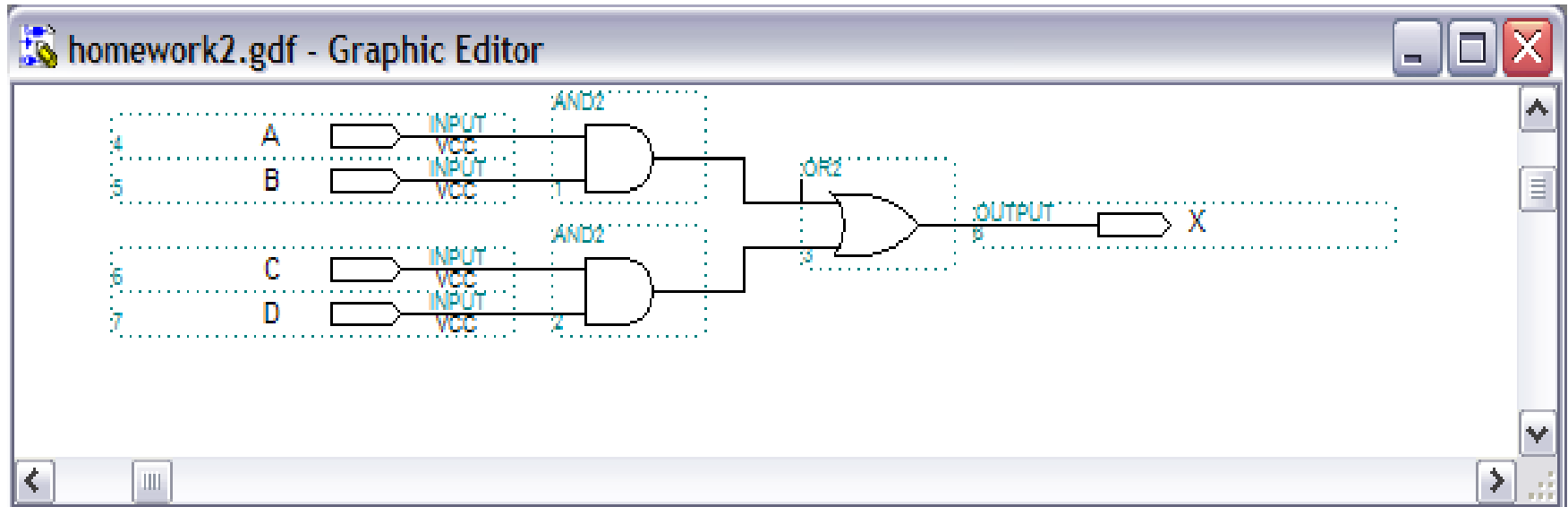

VHDL Code: $X = AB + CD$

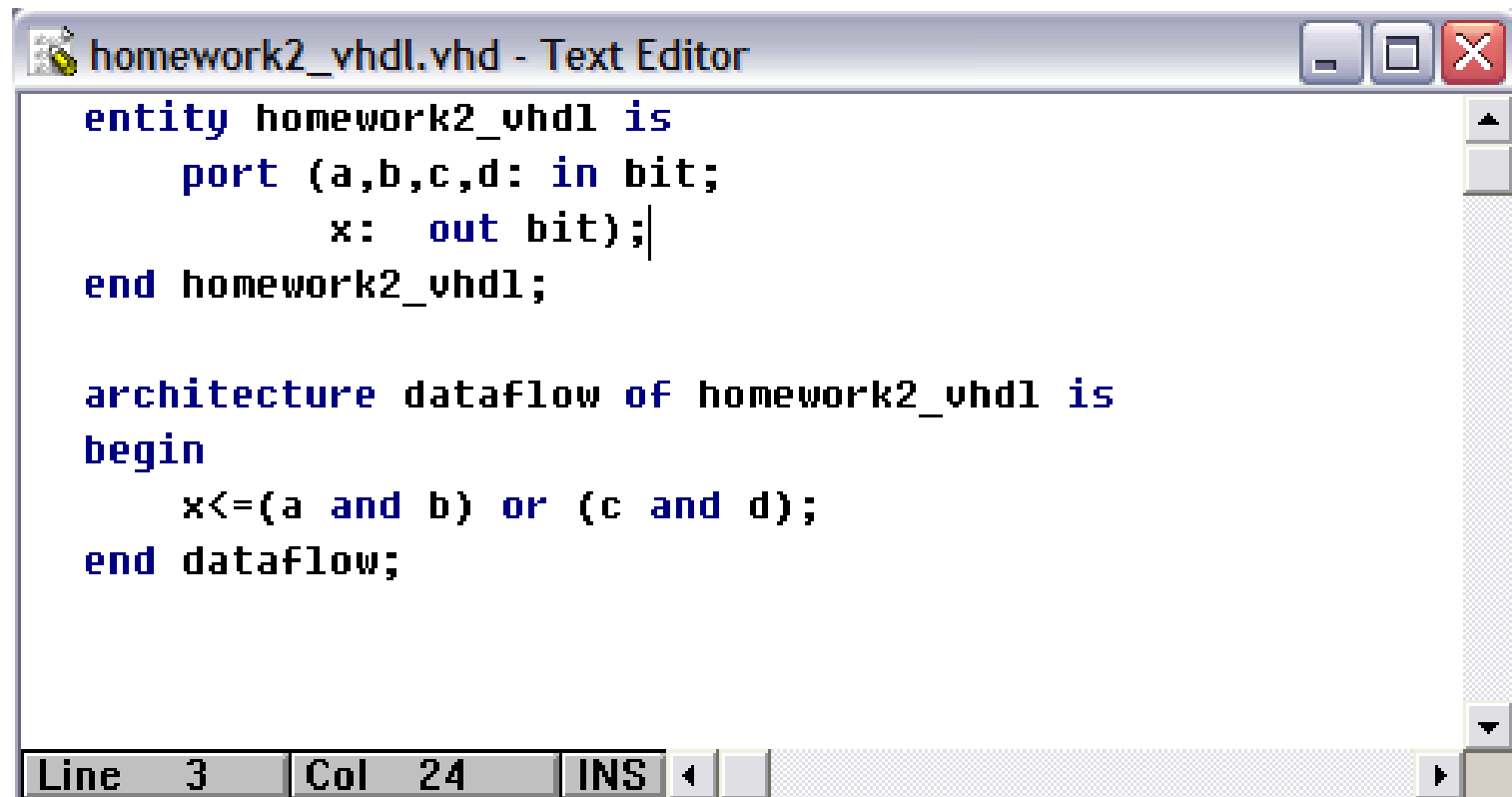


```
entity homework2_vhdl is
    port (a,b,c,d: in bit;
          x: out bit);
end homework2_vhdl;

architecture dataflow of homework2_vhdl is
begin
    x<=(a and b) or (c and d);
end dataflow;
```

Line 3 Col 24 INS

Waveform

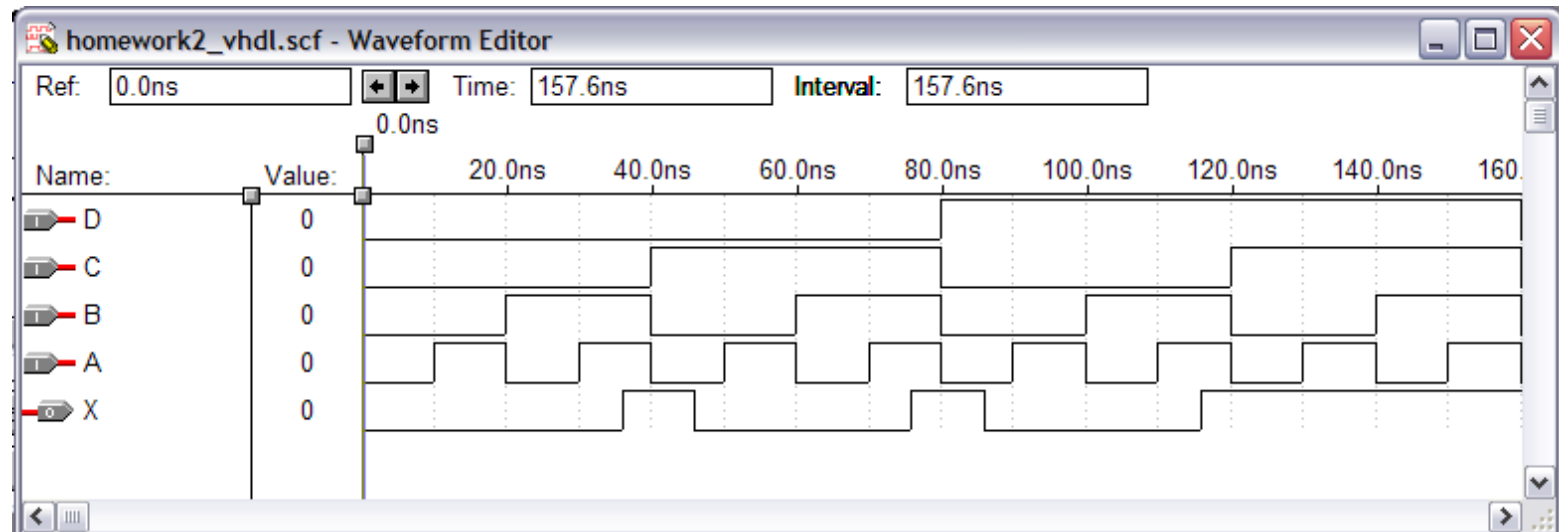

An array with many NAND gates

Sea-of-Gates Array Technology


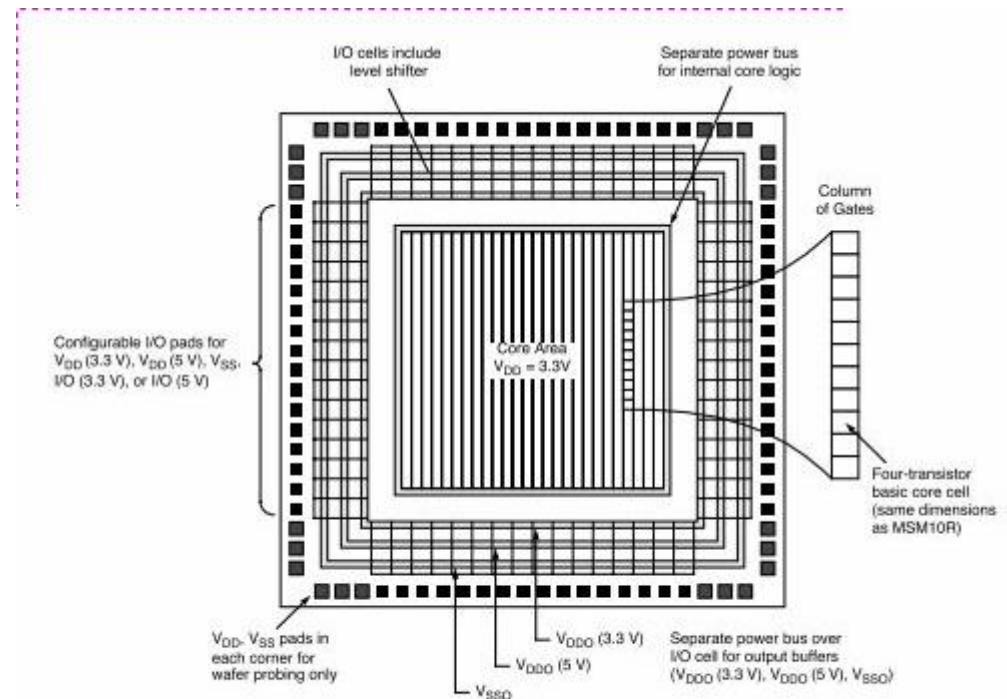
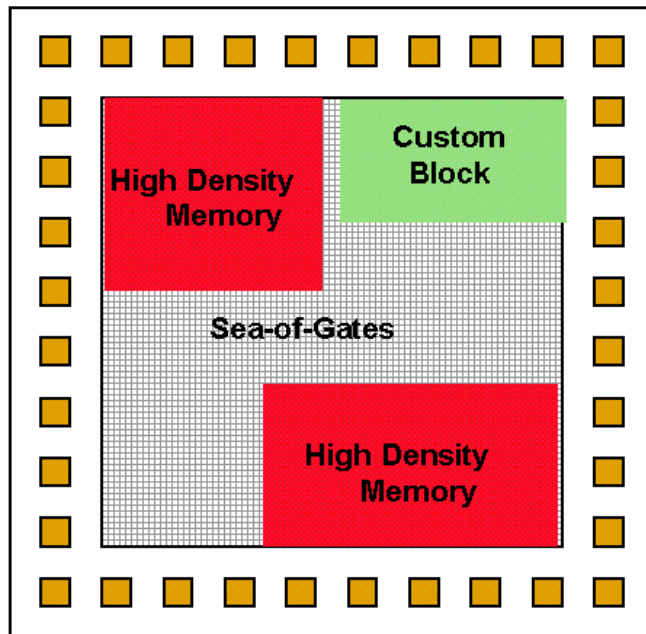


Figure 7. MSM13R0000 Array Architecture

An array with many NAND gates

Sea-of-Gates Array Technology

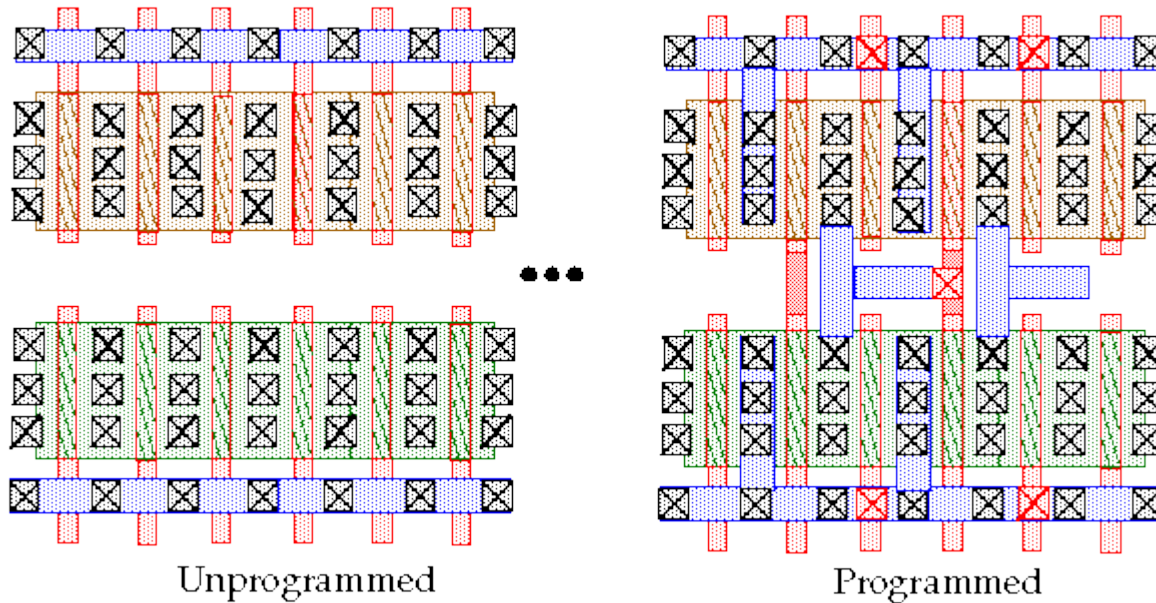

... two more gates

✓ XOR

✓ XNOR



OR gate

A	B	OR gate
0	0	0
0	1	1
1	0	1
1	1	1

XOR (eXclusiveOR) gate

A	B	OR gate	XOR gate
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	0

XOR (eXclusiveOR) gate



A	B	OR gate	XOR gate
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	0

$$A \text{ XOR } B = A \oplus B$$
$$= \overline{A} B + A \overline{B}$$


It produces a high output whenever the two inputs are at opposite levels

XOR (eXclusiveOR) gate

A	B	OR gate	XOR gate
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	0

$$A \text{ XOR } B = A \oplus B \\ = \bar{A}B + A\bar{B}$$

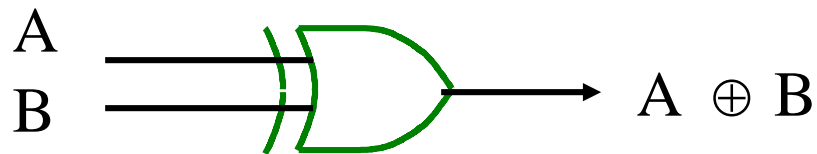It produces a high output whenever the two inputs are at opposite levels



Another gate ... XNOR

$$\overline{A \oplus B} = ?$$

XNOR (eXclusiveNOR) gate

A	B	XOR gate	XNOR gate
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1




XNOR (eXclusiveNOR) gate



A	B	XOR gate	XNOR gate
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1
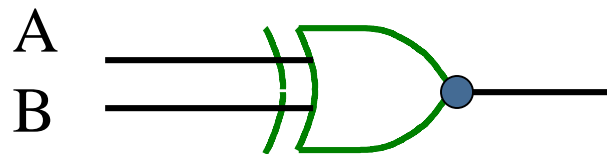
$$\begin{aligned} A \text{ XNOR } B &= \overline{A \oplus B} \\ &= \overline{A} \overline{B} + A B \end{aligned}$$



$$\overline{A \oplus B} = A \odot B$$