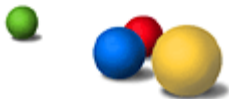


# K-MAP SIMPLIFICATION

# We know how to derive the output expression from ...

- ✓ Logic circuits



We **will learn** how to derive the output expression from ...

✓ Logic circuits


▪ **Truth tables**




# Truth table ...

Given a  
Truth Table


# Output expressions ...

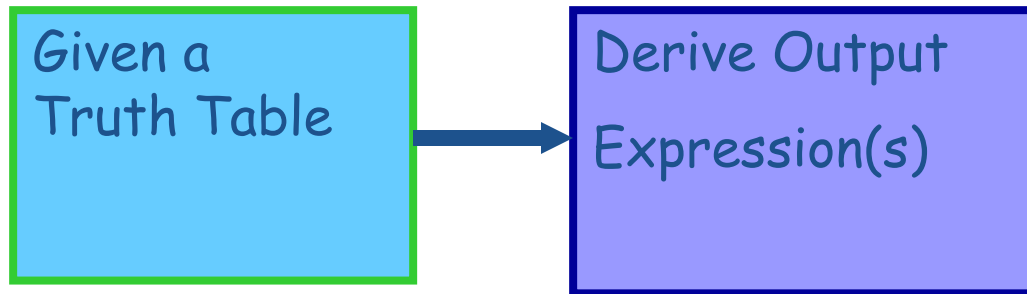


# Simplify ...

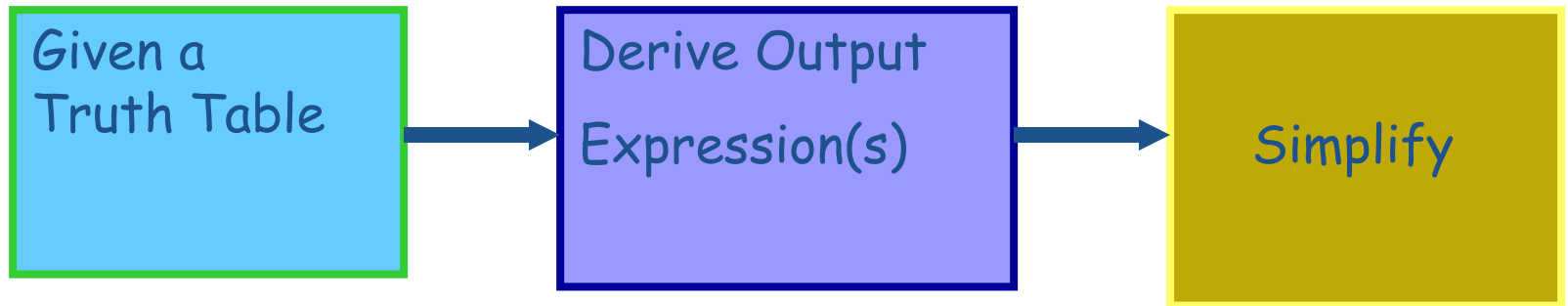

# Gates and VHDL coding

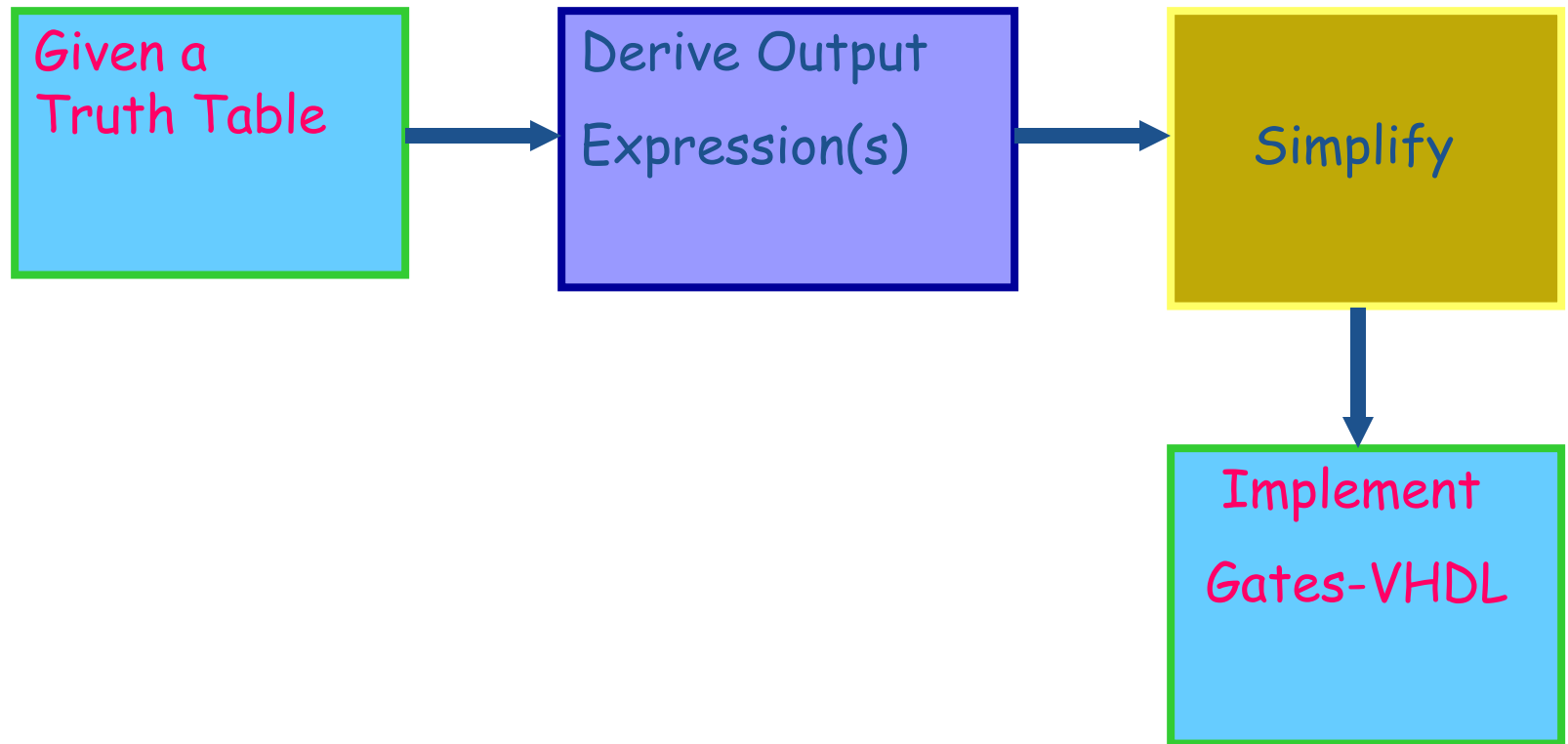

# Truth table → Simplified circuit

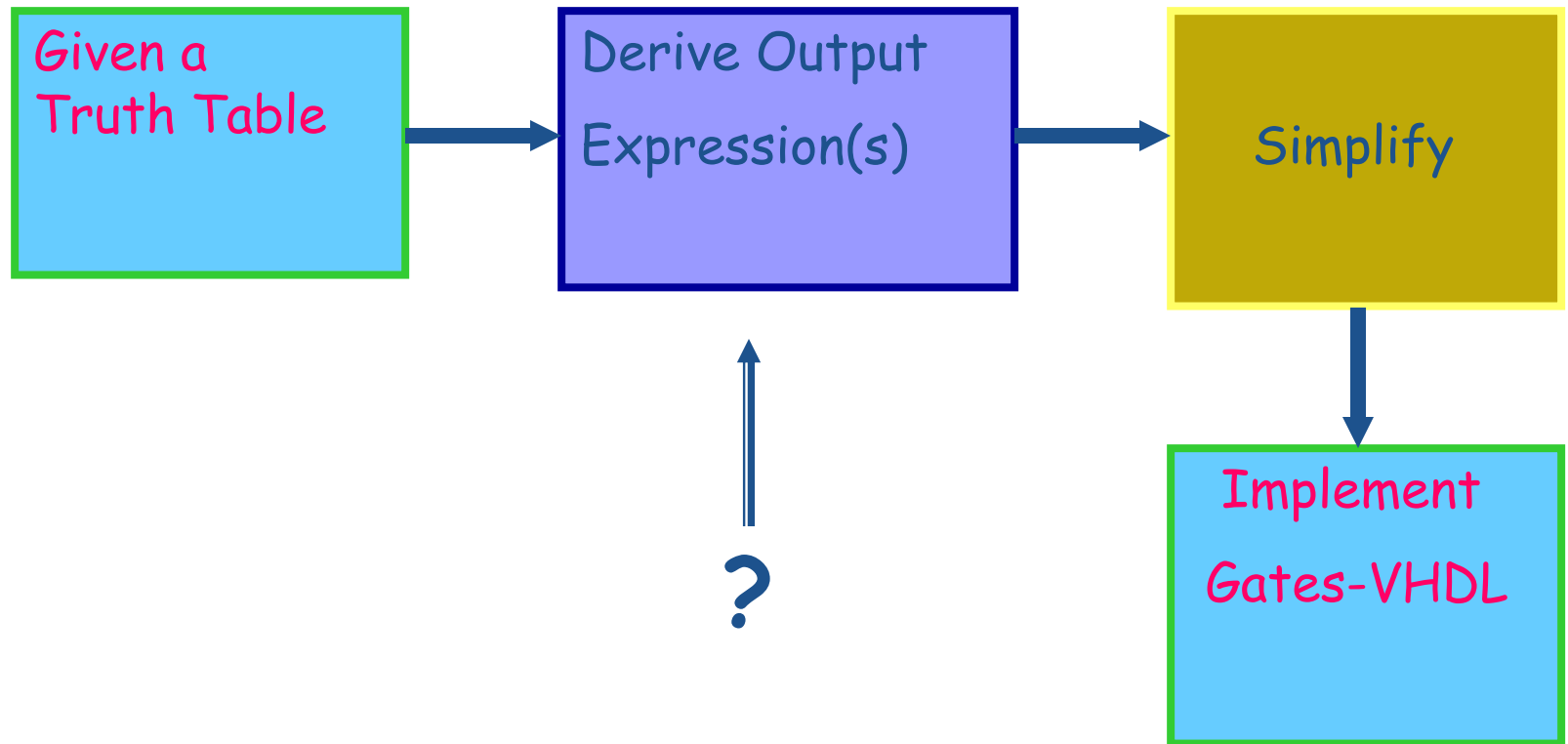



How can we derive an output expression from a Truth Table?

# How can we derive an output expression from a Truth Table?

## Algorithm:

1. Write an AND term (Boolean expression) for each case in the truth table the output is logic 1.

Algorithm is an anagram of logarithm ?

Truth table  $\rightarrow$  output logic expression(s)

### Algorithm:

1. Write an AND term (Boolean expression) for each case in the truth table the output is logic 1.
2. All the AND terms are then ORed together to produce the final output expression

# Example: Derive the Truth Table

## **Word Problem:**

For a three-input (A,B,C) binary system. If we have more than one high(1) inputs the output (X) is 1, otherwise is zero(0).

# Example: Truth Table

A	B	C	X
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

## Word Problem:

For a three-input (A,B,C) binary system. If we have more than one high(1) inputs the output (X) is 1, otherwise is zero(0).

# Example: Truth Table (done)



A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

## Word Problem:

For a three-input (A,B,C) binary system. If we have more than one high(1) inputs the output (X) is 1, otherwise is zero(0).

# Example: Write Terms

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$\overline{A} B C$

$A \overline{B} C$

$A B \overline{C}$

$A B C$

# Example: Output expression (SOP)

A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

SOP = Sum-Of-Products

$$\overline{A} B C$$

$$A \overline{B} C$$

$$A B \overline{C}$$

$$A B C$$

===== ➡  $X = \overline{A} B C + A \overline{B} C + A B \overline{C} + A B C$



# Simplify the logic expression

$$X = \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$

# Add two ABC terms


$$\begin{aligned} X &= \overline{A} BC + A \overline{B} C + A B \overline{C} + A B C \\ &= \overline{A} BC + \overline{A} \overline{B} C + A \overline{B} \overline{C} + A B C + \overline{A} B C + A B C \end{aligned}$$

# Result

$$\begin{aligned} X &= \overline{A} BC + A \overline{B} C + A B \overline{C} + A B C \\ &= \overline{A} BC + \overline{A} \overline{B} C + A \overline{B} \overline{C} + A B C + \overline{A} B C + A \overline{B} C \\ &= BC(\overline{A} + A) + AC(\overline{B} + B) + AB(\overline{C} + C) \\ &= BC + AC + AB \end{aligned}$$



# Implementation: Logic Circuit

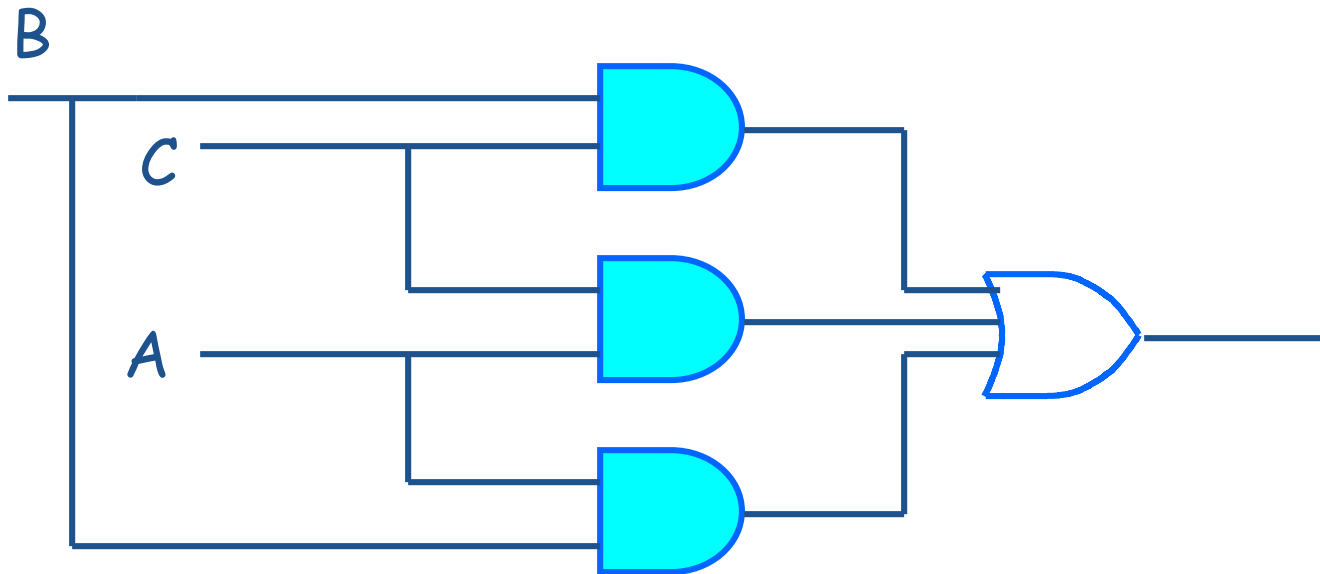

$$BC + AC + AB$$


# Conclusion

The algebraic simplification procedure is very  
**unsystematic...**

## A “more” systematic way...

- There is a more systematic way to simplify logic expressions: **Karnaugh maps** or **K-maps**.

# Karnaugh maps ( K-maps )

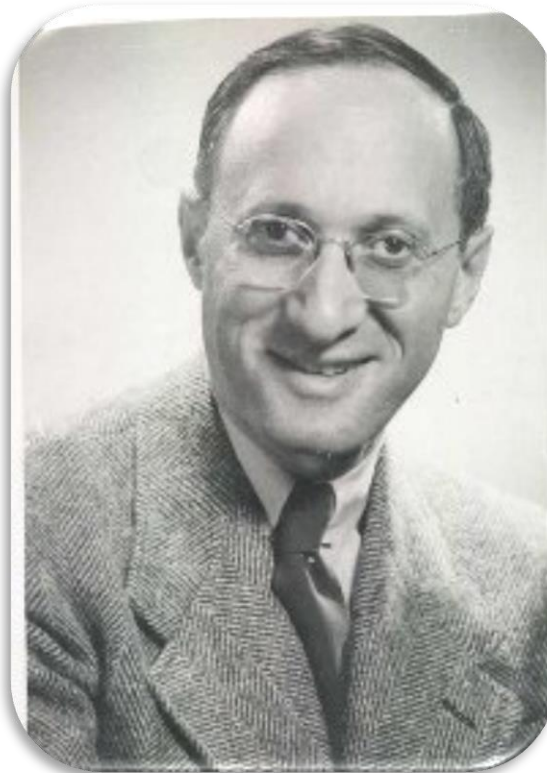

**Maurice Karnaugh, “*The Map Method for Synthesis of Combinational Logic Circuits*”, Trans. AIEE. part I, 72(9):593-599, November 1953.**


# Karnaugh maps ( K-maps )

K-map is a symbolic representation of a truth table that enables us to simplify a logic expression.

- 2-variable K-map
- 3-variable K-map
- 4-variable K-map
- ...



# 2-variable K-map setup

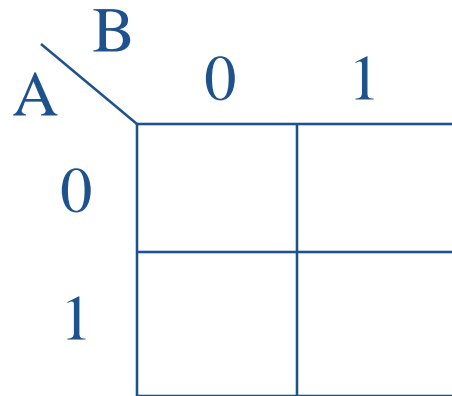

4-cells having values: 0 or 1

# 3-variable K-map setup

		BC			
		00	01	11	10
A	0				
	1				

or ...

# 3-variable K-map setup

		C	
		0	1
AB	00		
	01		
	11		
	10		

The 00, 01, 11, 10 are not in ascending order. This is the **Gray Code**...

# 4-variable K-map setup

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10				

# K-map: 2-variable set up

given:

A \ B	0	1
0		
1		

A	B	X	
0	0	1	→ $\overline{A} \overline{B}$
0	1	0	
1	0	0	
1	1	1	→ $A B$

# K-map: 2-variable set up

A \ B	0	1
0	1	0
1	0	1


# K-map: 3-variable example set-up

AB \ C	C	
	0	1
00		
01		
11		
10		

given:

A	B	C	X	
0	0	0	1	→ $\overline{A}\overline{B}\overline{C}$
0	0	1	1	→ $\overline{A}\overline{B}C$
0	1	0	1	→ $\overline{A}B\overline{C}$
0	1	1	0	
1	0	0	0	
1	0	1	0	
1	1	0	1	→ $AB\overline{C}$
1	1	1	0	

# K-map: 3-variable example set-up

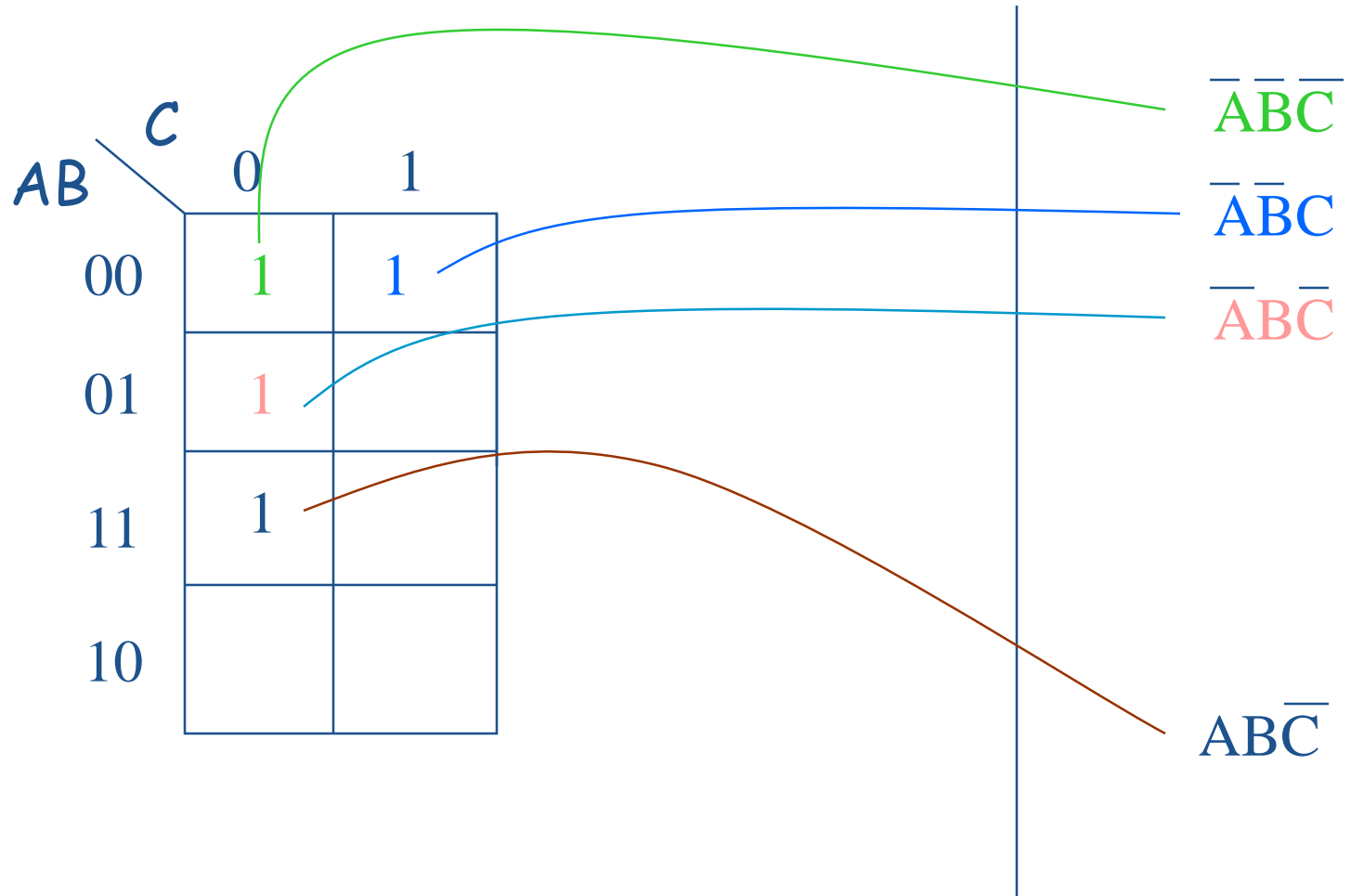



# Four variable K-map: Example

		CD			
		00	01	11	10
A	B				
	00				
	01				
	11				
	10				

$$X = \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}D + A\bar{B}\bar{C}D + ABCD$$

# Four variable K-map: Example

		CD			
		00	01	11	10
A	B				
	00		1		
	01		1		
	11		1		
	10			1	

$$X = \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}D + A\bar{B}\bar{C}D + ABCD$$

# How can we simplify using K-maps?

Use **looping**

**looping** is a process of combining 1's

# Looping: Process of combining 1's

The looping is done in groups of ...

Two (pair)

Four (quad)

Eight (octet)

# 1) Looping: Pair (2 ... 1's)

- Looping a pair of adjacent 1's in a K-map table eliminates **one variable** that appears in *complemented* ( $A'$ ) and *uncomplemented* ( $A$ ) form.

# Uniting Theorem

- Looping a pair of adjacent 1's in a K-map table eliminates **one variable** that appears in *complemented* ( $A'$ ) and *uncomplemented* ( $A$ ) form.


$$B(A' + A) = B$$

# Example1: 2 logically adjacent 1's

AB \ C	C	
	0	1
00		
01	1	
11	1	
10		


$X = ?$



# Example1

		C	
		0	1
AB	00		
	01	1	
	11	1	
	10		
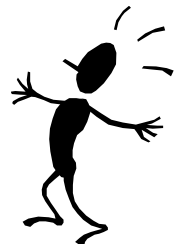
$$\begin{aligned}X &= \overline{A}B\overline{C} + AB\overline{C} \\&= \overline{B}\overline{C}(\overline{A} + A) \\&= \overline{B}\overline{C}\end{aligned}$$





# Logically adjacent ...

- Two terms (minterms) are logically adjacent if they differ in only one variable position (A) (Gray Code)

$$\begin{aligned} X &= \overline{A}BC\overline{C} + A\overline{B}C\overline{C} \\ &= BC(\overline{A} + A) \\ &= BC \end{aligned}$$

- Logically adjacent terms can be looped (combined)
- $A'BC'$ ,  $ABC'$  are minterms (m5, m6)



# Example2

AB \ C	C	
	0	1
00		
01	1	1
11		
10		

$X = ?$

# Example2

		C	
		0	1
AB	00		
	01	1	1
	11		
	10		

$$X = \overline{A} B$$

# Example3

AB \ C	C	
	0	1
00	1	
01		
11		
10	1	

$X = ?$

# Cyclic property...

AB \ C	0	1
00	1	
01		
11		
10	1	

$$X = \overline{B} \overline{C}$$

Top and bottom rows  
are considered to be  
logical adjacent

# Example4

		CD			
		00	01	11	10
A B	00			1	1
	01				
	11				
	10	1			1

$X = ?$


# Cyclic property ... again

		CD			
		00	01	11	10
A B	00			1	1
	01				
	11				
	10	1			1

$$X = A\bar{B}\bar{D} + \bar{A}\bar{B}C$$


Left and right columns are considered to be logical adjacent...

# Adjacent left-right and top-bottom

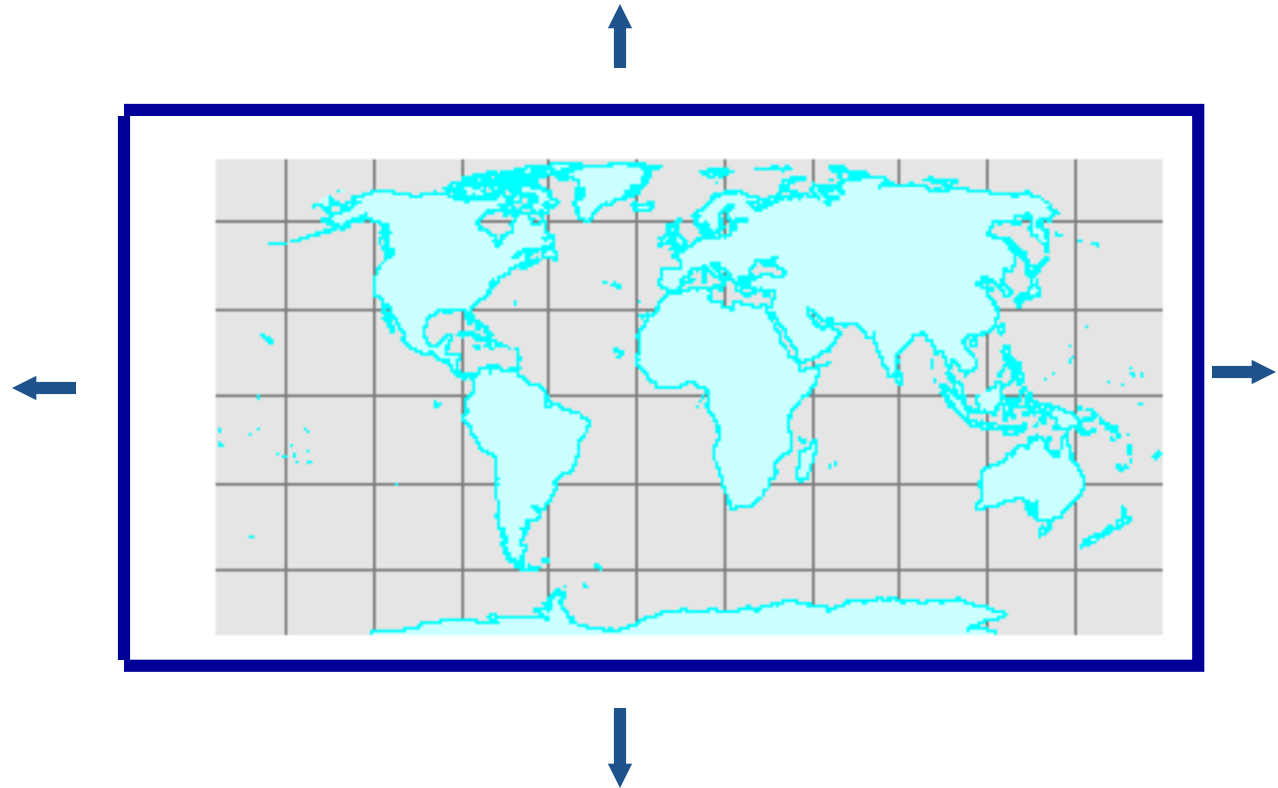



# Earth

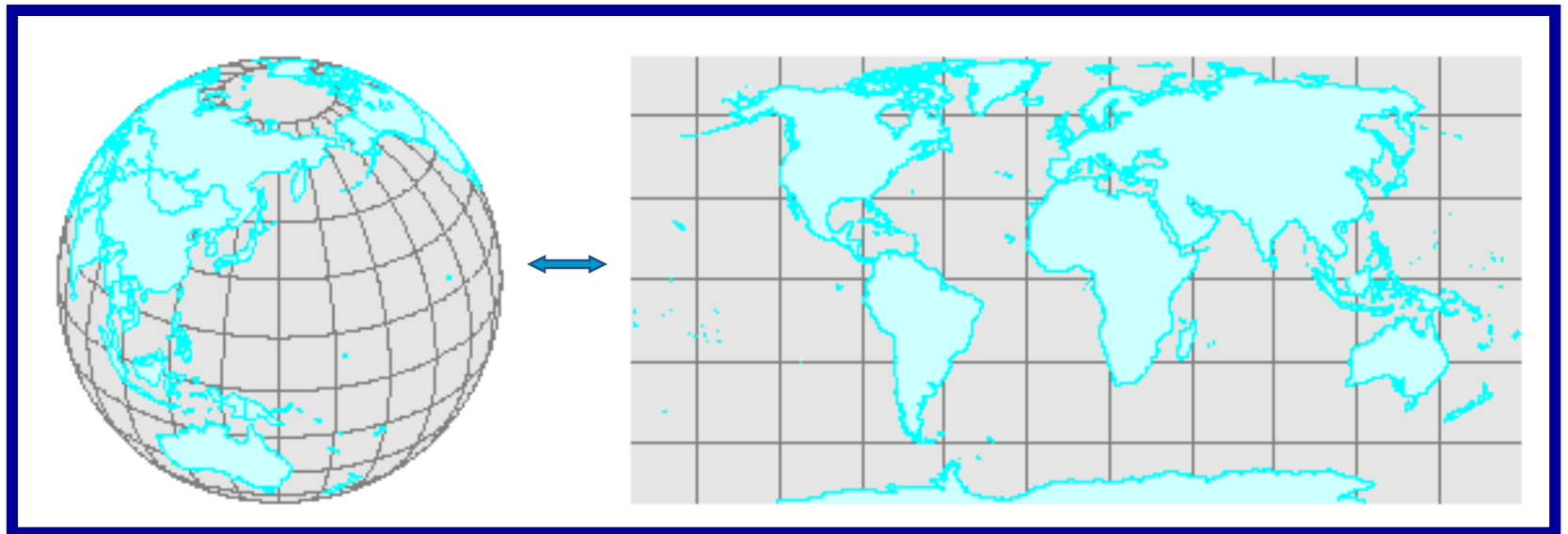

## 2) Looping: Quad (4 ... 1's)

- Looping (Combining) a quad, of logically adjacent 1's in a K-map, eliminates **two variables** that appear in complemented and uncomplemented form.

# 3-variable K-Map: Example1

		C	
		0	1
AB	00		1
	01		1
	11		1
	10		1

$X = ?$

# 3-variable K-Map: Example1

		C	
		0	1
AB	00		1
	01		1
	11		1
	10		1

$$X = C$$

# Four variable K-map: Example2

A B \ CD		CD			
		00	01	11	10
A B	00				
	01				
	11	1	1	1	1
	10				

$X = ?$

# Four variable K-map: Example2

A B \ CD		00	01	11	10
		00	01	11	10
00					
01					
11		1	1	1	1
10					

$$X = AB$$

# Four variable K-map: Example3

		CD			
		00	01	11	10
A B	00				
	01		1	1	
	11		1	1	
	10				

$X = ?$

# Four variable K-map: Example3

A B \ CD		CD			
		00	01	11	10
A B	00				
	01		1	1	
	11		1	1	
	10				

$$X = BD$$



# Four variable K-map: Example4

A B \ CD		00	01	11	10
		00	01	11	10
00					
01					
11		1			1
10		1			1

$X = ?$

# Left and Right pairs are adjacent

A B \ CD		CD			
		00	01	11	10
A B	00				
	01				
	11	1			1
	10	1			1

$$X = A\overline{D}$$

# Four variable K-map: Example5

A B \ CD		CD			
		00	01	11	10
AB	00	1			1
	01				
	11				
	10	1			1

$X = ?$

# Cyclic property: All 1's are adjacent

A 4x4 Karnaugh map for variables A, B, C, and D. The columns are labeled CD (00, 01, 11, 10) and the rows are labeled AB (00, 01, 11, 10). The map shows four 1s at positions (00,00), (10,00), (00,10), and (10,10). Green curved lines connect the 1s in a cycle: (00,00) to (10,00), (10,00) to (10,10), (10,10) to (00,10), and (00,10) back to (00,00), demonstrating the cyclic property.

AB \ CD	00	01	11	10
00	1			1
01				
11				
10	1			1

$$X = \overline{D}\overline{B}$$

### 3) Looping: Octel (8 ... 1's)

- Looping (combining) an octet, of logically adjacent 1's, in a K-map eliminates **three variables** that appear in **complemented** and **uncomplemented** form
- In general, looping  $2^m$  terms...eliminates  $m$  variables.

# Four variable K-map: Example1

		CD			
		00	01	11	10
A B	00				
	01	1	1	1	1
	11	1	1	1	1
	10				

$X = ?$

# Solution

		CD			
		00	01	11	10
A B	00				
	01	1	1	1	1
	11	1	1	1	1
	10				

$$X = B$$

# Four variable K-map: Example2

		CD			
		00	01	11	10
A B	00	1	1		
	01	1	1		
	11	1	1		
	10	1	1		

$X = ?$



# Solution

		CD			
		00	01	11	10
A B	00	1	1		
	01	1	1		
	11	1	1		
	10	1	1		

$$X = \overline{C}$$

# Four variable K-map: Example3

		CD			
		00	01	11	10
A B	00	1	1	1	1
	01				
	11				
	10	1	1	1	1

$X = ?$

# Solution

CD		00	01	11	10
A B	00	1	1	1	1
	01				
	11				
	10	1	1	1	1

$$X = \overline{B}$$

# Four variable K-map: Example4

		CD			
		00	01	11	10
A B	00	1			1
	01	1			1
	11	1			1
	10	1			1

$X = ?$

# Solution

		CD			
		00	01	11	10
A B	00	1			1
	01	1			1
	11	1			1
	10	1			1

$$X = \overline{D}$$

# More Examples-1

		CD			
		00	01	11	10
A B	00		1		
	01		1	1	1
	11	1	1	1	
	10			1	

$X = ?$



# Looping...

		CD			
		00	01	11	10
A B	00		1		
	01		1	1	1
	11	1	1	1	
	10			1	

$$X = \overline{A}\overline{C}D + \overline{A}BC + ABC\overline{C} + ACD + BD$$

# BD is not needed

		CD			
		00	01	11	10
A B	00		1		
	01		1	1	1
	11	1	1	1	
	10			1	


$$X = \overline{A}\overline{C}\overline{D} + \overline{A}BC + ABC\overline{C} + ACD + BD$$



# Optimal Minimal Simplification

		CD			
		00	01	11	10
AB	00		1		
	01		1	1	1
	11	1	1	1	
	10			1	
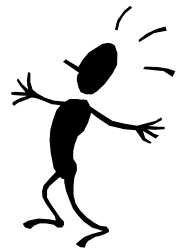
$$X = \overline{A}\overline{C}D + \overline{A}BC + ABC\overline{C} + ACD$$



# More Examples-2

		CD			
		00	01	11	10
A B	00				1
	01		1	1	
	11		1	1	
	10			1	

$X = ?$



# Minimal simplification

		CD			
		00	01	11	10
A B	00				1
	01		1	1	
	11		1	1	
	10			1	

$$X = ACD + BD + \overline{A}\overline{B}\overline{C}\overline{D}$$



# More Examples-3


		CD			
		00	01	11	10
A B	00			1	
	01	1	1	1	1
	11	1	1		
	10				

$X = ?$

# Minimal simplification

		CD			
		00	01	11	10
A B	00			1	
	01	1	1	1	1
	11	1	1		
	10				
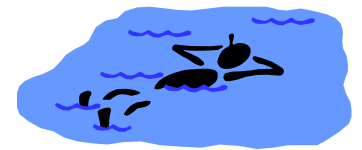
$$X = \overline{A}CD + \overline{A}B + B\overline{C}$$



# Summary: Looping (K-Map)

- Loop the isolated 1's (those not logically adjacent to any other 1's). Look for the 1's that are adjacent to any loops and loop any pair containing such 1's. Each 1 must be looped at least once. However, it may be covered more than once (optimal).
  - Loop any octets (optimal)
  - Loop any quads (optimal)
  - Loop any pairs (optimal)
  - Form the OR sum of all terms in the loops