



Moray, Peru

HIGH SPEED ADDER


Carry-Ripple Adder (CRA)

WHAT WE KNOW ...

S_i ... we derived

C
R
A

x_i	y_i	C_i	S_i	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

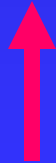

$$S_i = C_i \oplus x_i \oplus y_i$$

Carry out C_{i+1} ?

C

R

A

x_i	y_i	C_i	S_i	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

		C_i	
		0	1
$x_i y_i$	00		
	01		1
	11	1	1
	10		1

New carry out C_{i+1}

C

R

A

x_i	y_i	C_i	S_i	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

		C_i	
		0	1
$x_i y_i$	00		
	01		1
	11	1	1
	10		1

$$C_{i+1} = x_i y_i + x_i C_i + y_i C_i$$

CRA equations (new...)

C

R

A

$$S_i = C_i \oplus x_i \oplus y_i$$

$$C_{i+1} = x_i y_i + x_i C_i + y_i C_i$$

CRA equations; for $i = 0$

$$S_i = C_i \oplus x_i \oplus y_i$$

$$C_{i+1} = x_i y_i + x_i C_i + y_i C_i$$

C

R

A

CRA equations; $i = 0$ (1-bit)

C

R

A

$$S_i = C_i \oplus x_i \oplus y_i$$

$$C_{i+1} = x_i y_i + x_i C_i + y_i C_i$$

For $i = 0$

$$S_0 = C_0 \oplus x_0 \oplus y_0$$


$$\begin{aligned} C_1 &= x_0 y_0 + x_0 C_0 + y_0 C_0 \\ &= x_0 y_0 + C_0(x_0 + y_0) \end{aligned}$$

NEW CRA Implementation

$$S_0 = C_0 \oplus x_0 \oplus y_0$$

1-bit

CRA

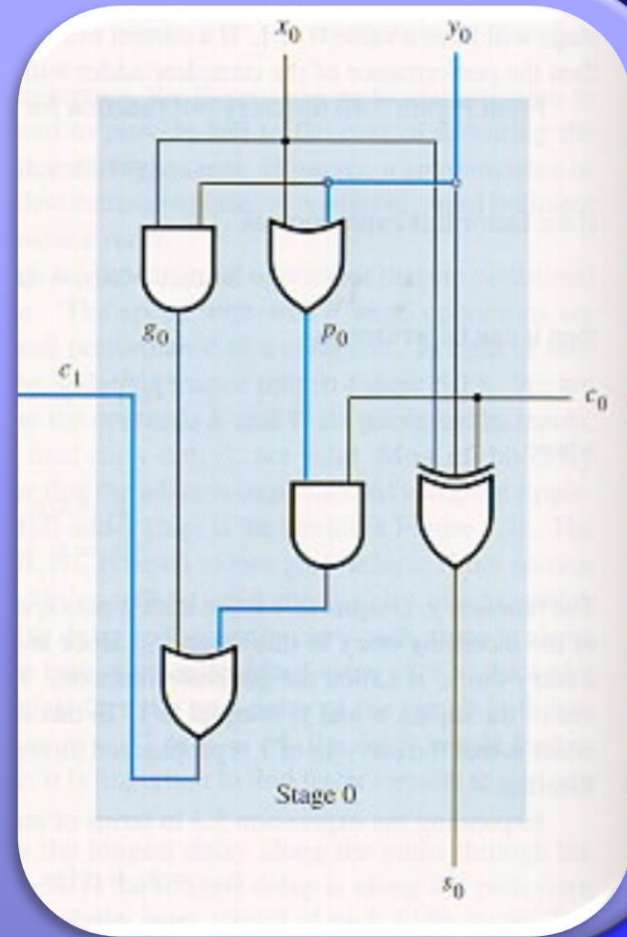


1-bit

C
R
A

$$S_0 = C_0 \oplus x_0 \oplus y_0$$

$$C_1 = x_0 y_0 + C_0(x_0 + y_0)$$

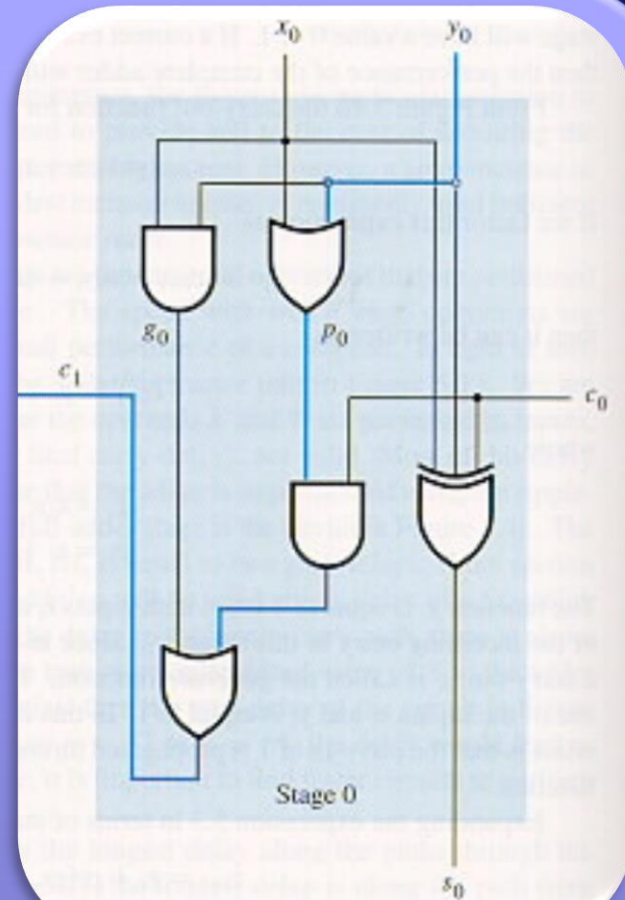

$$S_1 = C_1 \oplus x_1 \oplus y_1$$


$$C_2 = x_1 y_1 + C_1(x_1 + y_1)$$

$$S_0 = C_0 \oplus x_0 \oplus y_0$$

$$C_1 = x_0 y_0 + C_0(x_0 + y_0)$$

2-bit

CRA

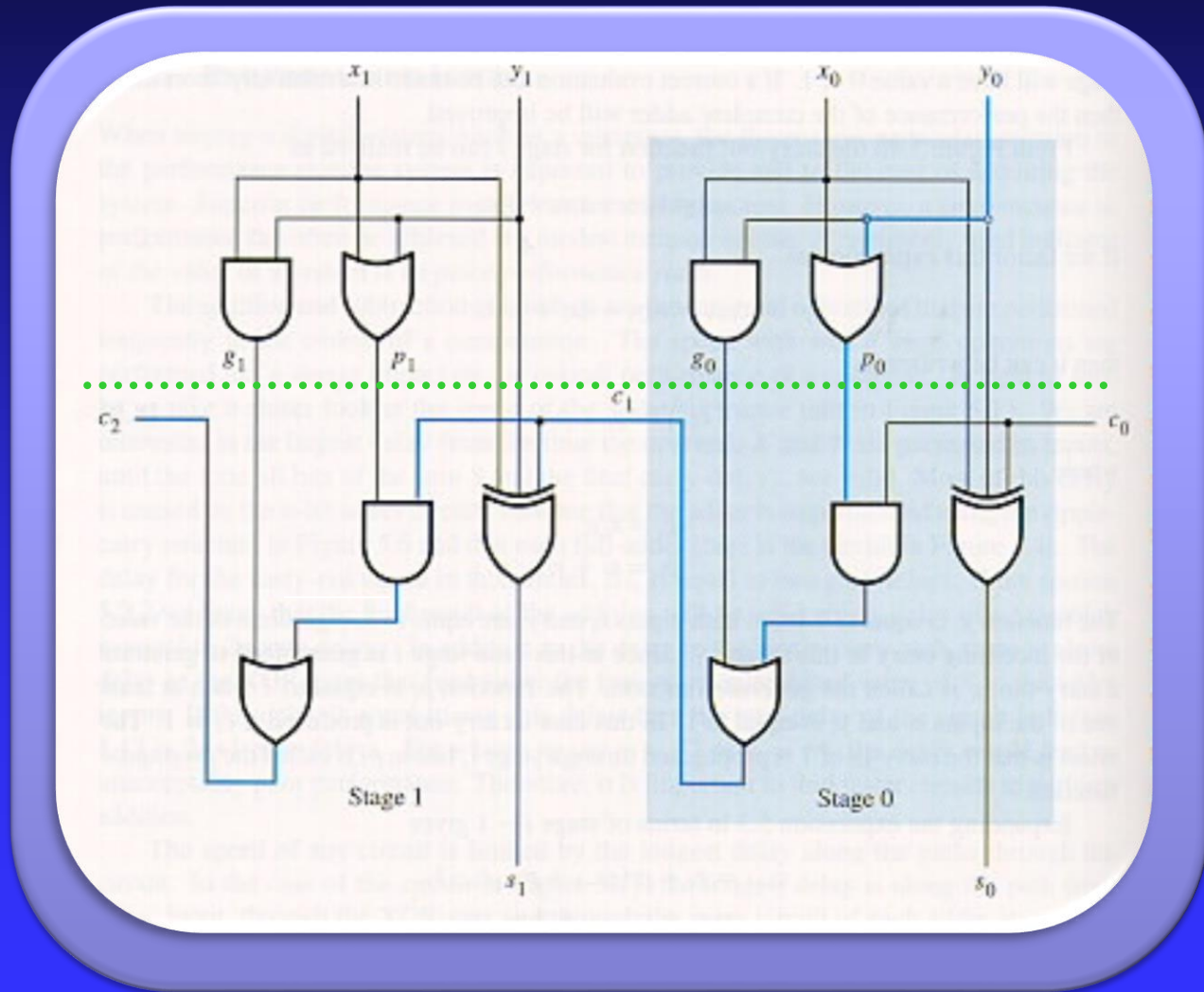

Gate Delay (nsec)

	inputs		
Gate	2	3	4
AND	2.4	2.8	3.2
OR	2.4	2.8	3.2
NAND	1.4	1.8	2.8


Rate of addition

The rate of addition of binary numbers is usually measured by the carry propagation time of the Adder...

$y_0 \dots C_2$ -- the longest path ...

2-bit


C
R
A

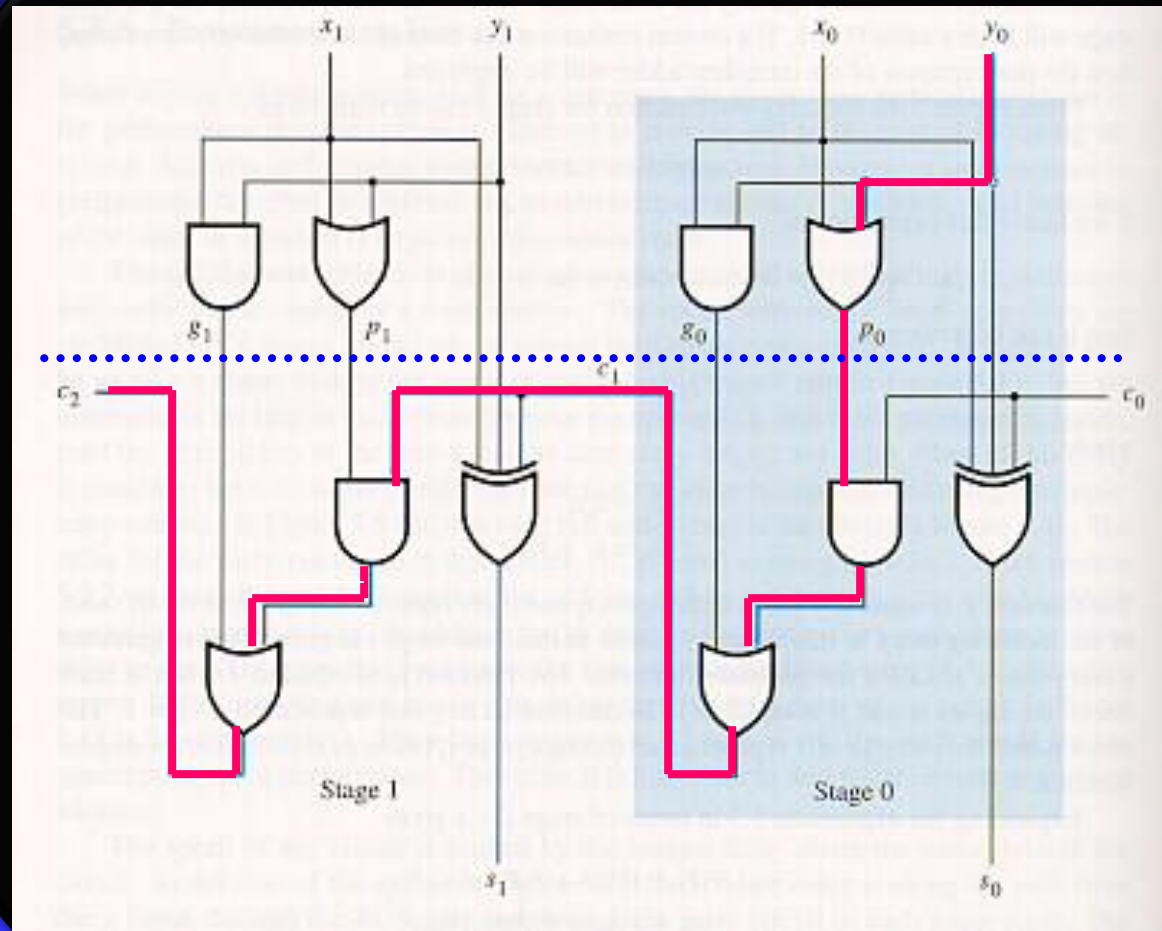

$y_0 \dots C_2 = 12 \text{ nsec}$

2-bit

CRA

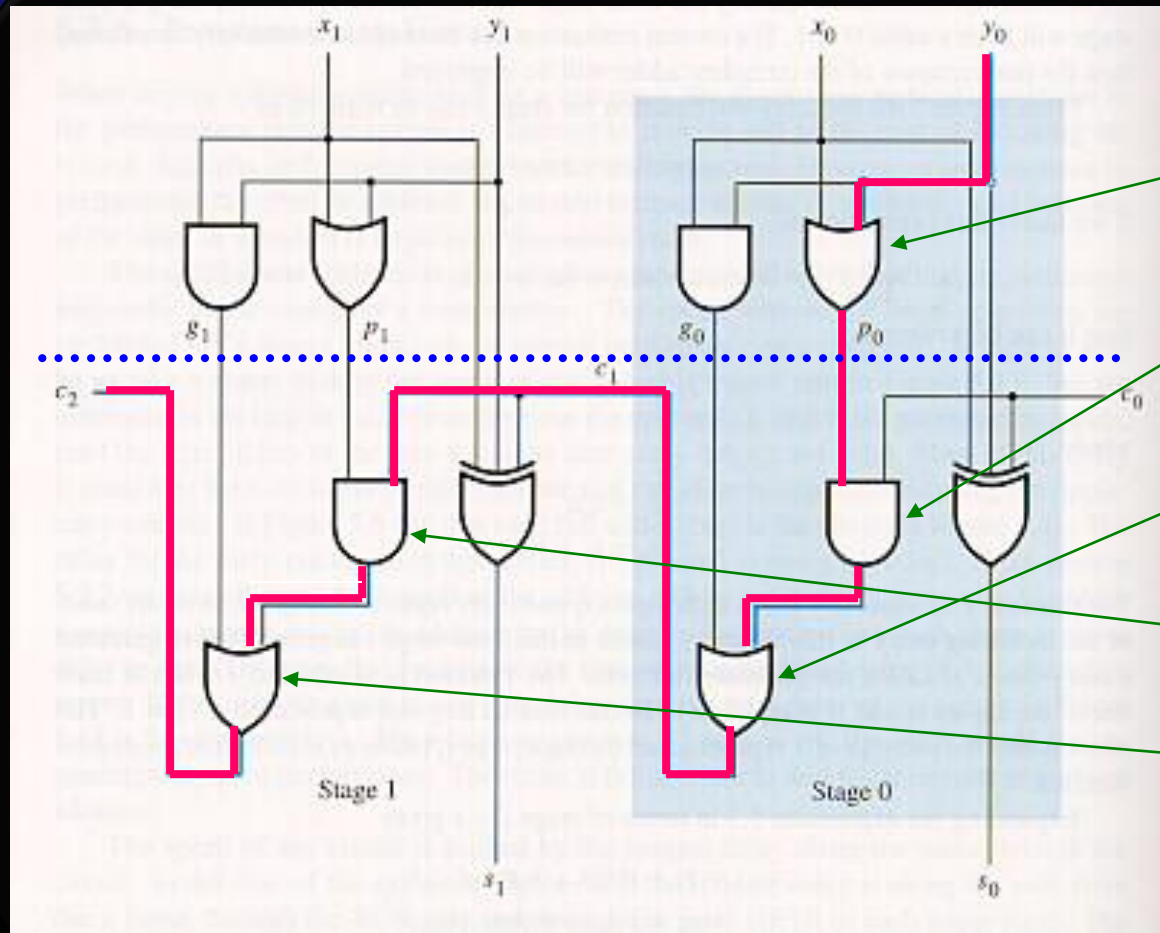

2.4
+
2.4
+
2.4
+
2.4
= 12

Look -Ahead Adder (LAA)


WE WILL LEARN ABOUT A HIGH SPEED ADDER

CRA

1-bit CRA Full adder equations

$$S_0 = C_0 \oplus x_0 \oplus y_0$$

$$C_1 = x_0 y_0 + C_0(x_0 + y_0)$$

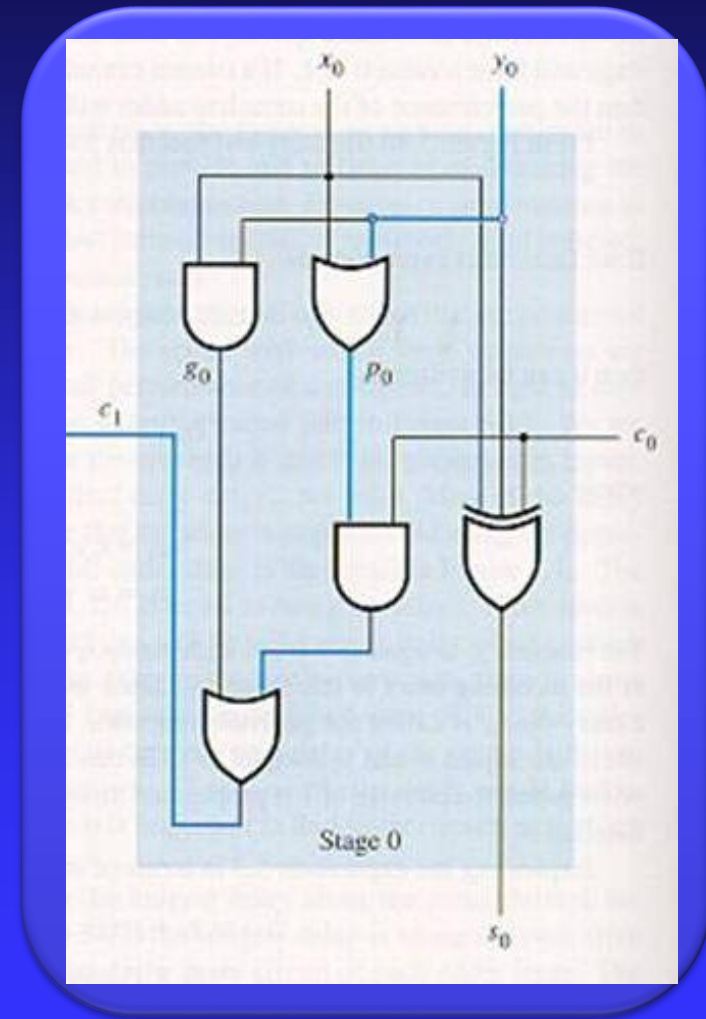

$p_0 - g_0$

C

R

A


$$S_0 = C_0 \oplus x_0 \oplus y_0$$

$$C_1 = x_0 y_0 + C_0(x_0 + y_0)$$

if,

$$g_0 = x_0 y_0$$

$$p_0 = x_0 + y_0$$

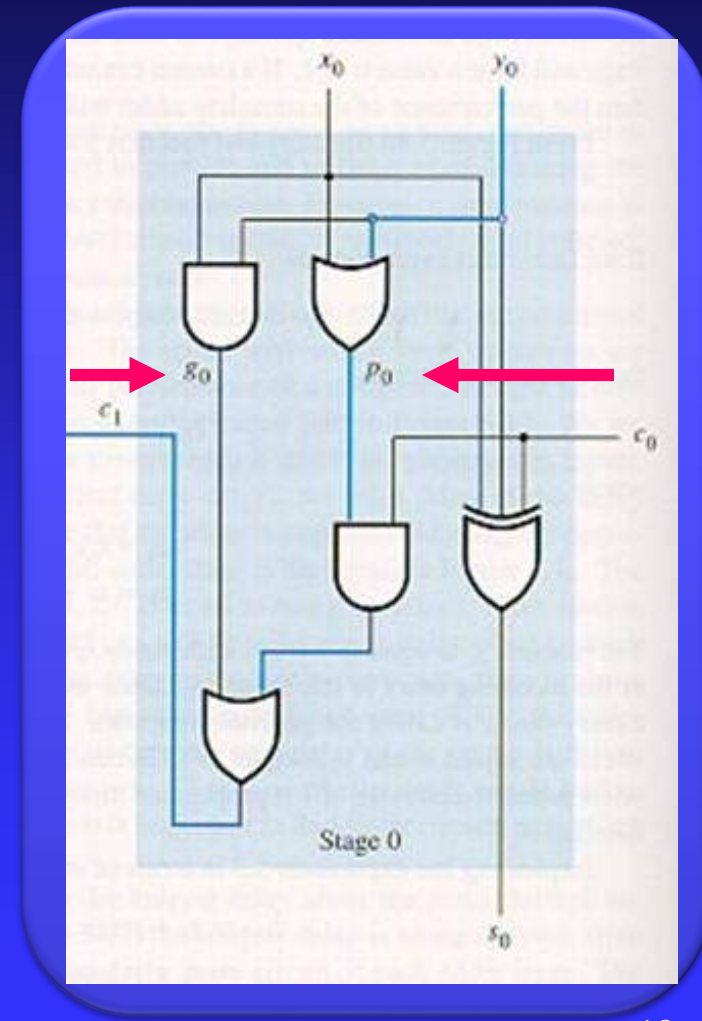

p_0 = internal propagated carry
 g_0 = internal generated carry

C

$$S_0 = C_0 \oplus x_0 \oplus y_0$$

$$C_1 = x_0 y_0 + C_0(x_0 + y_0)$$

R

if,


$$g_0 = x_0 y_0$$

$$p_0 = x_0 + y_0$$

A

then,

$$C_1 = g_0 + C_0 p_0$$

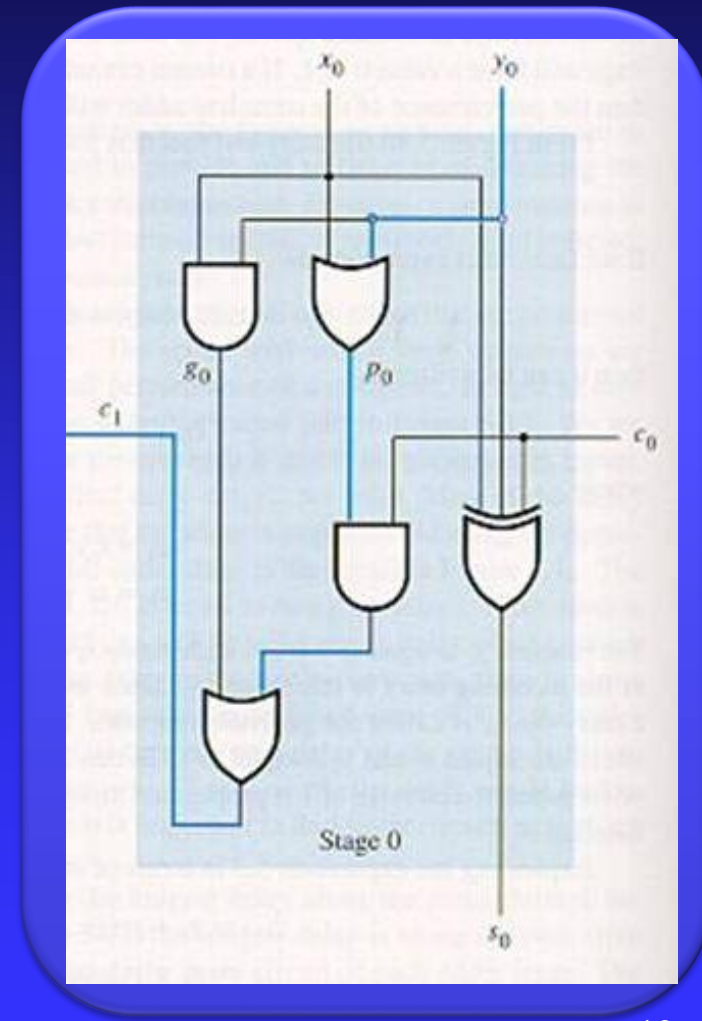

go - po ... an explanation

Full adder: Truth table

x_i	y_i	C_i	S	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Observations

x_i	y_i	C_i	S	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Observations

x_i	y_i	C_i	S	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Carry is **P**ropagated for **y_i**

Carry is **P**ropagated for **x_i**

Observations

x_i	y_i	C_i	S	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Carry is **P**ropagated for y_i

Carry is **P**ropagated for x_i

Carry is **G**enerated

Propagated Carry...

x_i	y_i	C_i	S	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

P

P

G



Generated Carry

x_i	y_i	C_i	S	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

P

P

G

$$P_i = \bar{x}_i \cdot y_i + x_i \cdot \bar{y}_i$$

$$P_i = y_i \oplus x_i$$

$$G_i = x_i \cdot y_i$$

The logical trick ... for P_i

x_i	y_i	C_i	S	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

P

P

G

x_i	y_i	$y_i \oplus x_i$	
0	1	?	
1	0	?	

$$P_i = y_i \oplus x_i$$

$$G_i = x_i \cdot y_i$$

Therefore ...

x_i	y_i	C_i	S	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

P

P

G

x_i	y_i	$y_i \oplus x_i$	$y_i + x_i$
0	1	1	?
1	0	1	?

$$P_i = y_i \oplus x_i$$

$$G_i = x_i \cdot y_i$$



Therefore ...

x_i	y_i	C_i	S	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

P

P

G

x_i	y_i	$y_i \oplus x_i$	$y_i + x_i$
0	1	1	1
1	0	1	1

$$P_i = y_i \oplus x_i = y_i + x_i$$

$$G_i = x_i \cdot y_i$$



Pi and Gi ...

$$P_i = y_i + x_i$$

$$G_i = x_i \cdot y_i$$

Derive and implement the LAA

Sum and Carry out equations

$$S_i = C_i \oplus x_i \oplus y_i$$

$$C_{i+1} = C_i(x_i + y_i) + x_i y_i$$

... and the new internal Carries

$$S_i = C_i \oplus x_i \oplus y_i$$

$$C_{i+1} = C_i(x_i + y_i) + x_i y_i$$

$$P_i = x_i + y_i$$

$$G_i = x_i y_i$$

Then, $C_{i+1} = f(C_i, P_i, G_i)$ is

$$S_i = C_i \oplus x_i \oplus y_i$$

$$C_{i+1} = C_i(x_i + y_i) + x_i y_i$$

$$P_i = x_i + y_i$$


$$G_i = x_i y_i$$

$$C_{i+1} = C_i P_i + G_i$$

LAA Equations

L

$$S_i = C_i \oplus x_i \oplus y_i$$

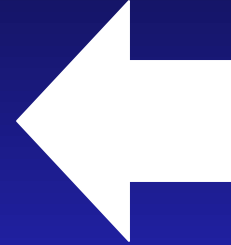


A

$$P_i = x_i + y_i$$

$$G_i = x_i y_i$$

A

$$C_{i+1} = C_i P_i + G_i$$

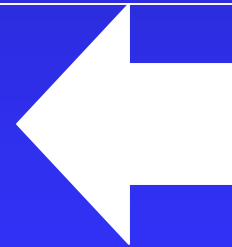

Next we will derive the LAA equations
for two-bits or two-stages

C_{i+1} for $i = 0, 1, 2, 3, \dots = C_1$

L

A

A

$$C_{i+1} = C_i P_i + G_i$$

$$i = 0, C_1 = C_0 P_0 + G_0$$

C_{i+1} for $i = 0, 1, 2, 3, \dots = C_2$

L

A

A

$$C_{i+1} = C_i P_i + G_i$$

$$i = 0, C_1 = C_0 P_0 + G_0$$

$$i = 1, C_2 = C_1 P_1 + G_1$$

C_{i+1} for $i = 0, 1, 2, 3, \dots = C_2$

L

A

A

$$C_{i+1} = C_i P_i + G_i$$

$$i = 0, C_1 = C_0 P_0 + G_0$$

$$i = 1, C_2 = C_1 P_1 + G_1$$

$$= (C_0 P_0 + G_0) P_1 + G_1$$

C_{i+1} for $i = 0, 1, 2, 3, \dots = C_2$

L

A

A

$$C_{i+1} = C_i P_i + G_i$$

$$i = 0, C_1 = C_0 P_0 + G_0$$

$$i = 1, C_2 = C_1 P_1 + G_1$$

$$= (C_0 P_0 + G_0) P_1 + G_1$$

$$= C_0 P_0 P_1 + G_0 P_1 + G_1$$

Expanded LAA equations

L

$$C_{i+1} = C_i P_i + G_i$$

$$i = 0, C_1 = C_0 P_0 + G_0$$

A

$$i = 1, C_2 = C_1 P_1 + G_1$$

$$= (C_0 P_0 + G_0) P_1 + G_1$$

$$= C_0 P_0 P_1 + G_0 P_1 + G_1$$

A

$$S_i = C_i \oplus x_i \oplus y_i$$

Expanded 2-bit LAA equations

L

$$C_{i+1} = C_i P_i + G_i$$

$$C_1 = C_0 P_0 + G_0$$

← $i = 0$

A

$$S_i = C_i \oplus x_i \oplus y_i$$

$$S_0 = C_0 \oplus x_0 \oplus y_0$$

← $i = 0$

A

Expanded 2-bit LAA equations

L

$$C_{i+1} = C_i P_i + G_i$$

$$C_1 = C_0 P_0 + G_0$$



$i = 0$

$$C_2 = C_0 P_0 P_1 + G_0 P_1 + G_1$$



$i = 1$

A

$$S_i = C_i \oplus x_i \oplus y_i$$

$$S_0 = C_0 \oplus x_0 \oplus y_0$$



$i = 0$

$$S_1 = C_1 \oplus x_1 \oplus y_1$$



$i = 1$

A

Expanded 2-bit LAA equations

L

A

A

$$C_{i+1} = C_i P_i + G_i$$

$$C_1 = C_0 P_0 + G_0$$

$$C_2 = C_0 P_0 P_1 + G_0 P_1 + G_1$$

$$S_i = C_i \oplus x_i \oplus y_i$$

$$S_0 = C_0 \oplus x_0 \oplus y_0$$

$$S_1 = C_1 \oplus x_1 \oplus y_1$$

$$P_i = x_i + y_i$$

$$\leftarrow i = 0 \rightarrow P_0 = x_0 + y_0$$

$$G_i = x_i y_i$$

$$\leftarrow i = 0 \rightarrow G_0 = x_0 y_0$$

Expanded 2-bit LAA equations

L

A

A

$$C_{i+1} = C_i P_i + G_i$$

$$C_1 = C_0 P_0 + G_0$$

$$C_2 = C_0 P_0 P_1 + G_0 P_1 + G_1$$

$$S_i = C_i \oplus x_i \oplus y_i$$

$$S_0 = C_0 \oplus x_0 \oplus y_0$$

$$S_1 = C_1 \oplus x_1 \oplus y_1$$

$$P_i = x_i + y_i$$

$$\leftarrow i = 0 \rightarrow P_0 = x_0 + y_0$$

$$\leftarrow i = 1 \rightarrow P_1 = x_1 + y_1$$

$$G_i = x_i y_i$$

$$\leftarrow i = 0 \rightarrow G_0 = x_0 y_0$$

$$\leftarrow i = 1 \rightarrow G_1 = x_1 y_1$$

2-bit LAA equations

L

A

A

$$C_1 = C_0 P_0 + G_0$$

$$C_2 = C_0 P_0 P_1 + G_0 P_1 + G_1$$

$$S_0 = C_0 \oplus x_0 \oplus y_0$$

$$S_1 = C_1 \oplus x_1 \oplus y_1$$

$$P_0 = x_0 + y_0$$

$$P_1 = x_1 + y_1$$

$$G_0 = x_0 y_0$$

$$G_1 = x_1 y_1$$

2-bit LAA equations; both stages

L

A

A

$$C_1 = C_0 P_0 + G_0$$

$$C_2 = C_0 P_0 P_1 + G_0 P_1 + G_1$$

$$S_0 = C_0 \oplus x_0 \oplus y_0$$

$$S_1 = C_1 \oplus x_1 \oplus y_1$$

$$P_0 = x_0 + y_0$$

$$P_1 = x_1 + y_1$$

$$G_0 = x_0 y_0$$

$$G_1 = x_1 y_1$$

Implement

First stage

L

A

A

$$C_1 = C_0 P_0 + G_0$$


$$S_0 = C_0 \oplus x_0 \oplus y_0$$

$$P_0 = x_0 + y_0$$

$$G_0 = x_0 y_0$$

.....▶
Implement

1-bit LAA @ CRA (same)

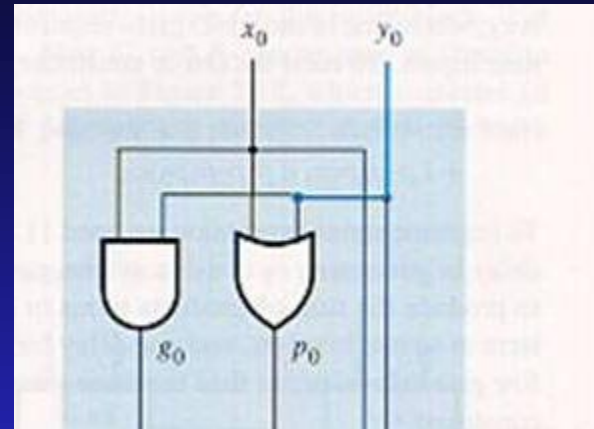

$$p_0 = x_0 + y_0$$

$$g_0 = x_0 y_0$$


1-bit LAA @ CRA (same)

$$c_1 = c_0 p_0 + g_0$$

$$S_0 = c_0 \oplus x_0 \oplus y_0$$

$$p_0 = x_0 + y_0$$

$$g_0 = x_0 y_0$$

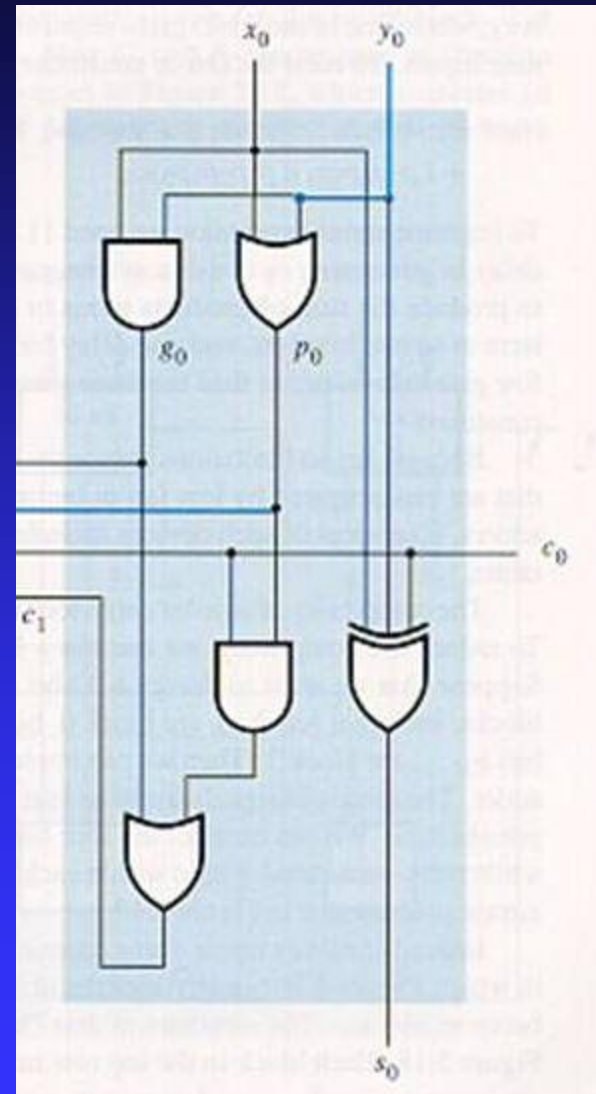

Second stage

L

A

A

$$c_2 = c_0 p_0 p_1 + g_0 p_1 + g_1$$

$$s_1 = c_1 \oplus x_1 \oplus y_1$$

$$p_1 = x_1 + y_1$$

$$g_1 = x_1 y_1$$


.....▶
Implement

2-bit

L
A
A

$$g_1 = x_1 y_1$$

$$p_1 = x_1 + y_1$$

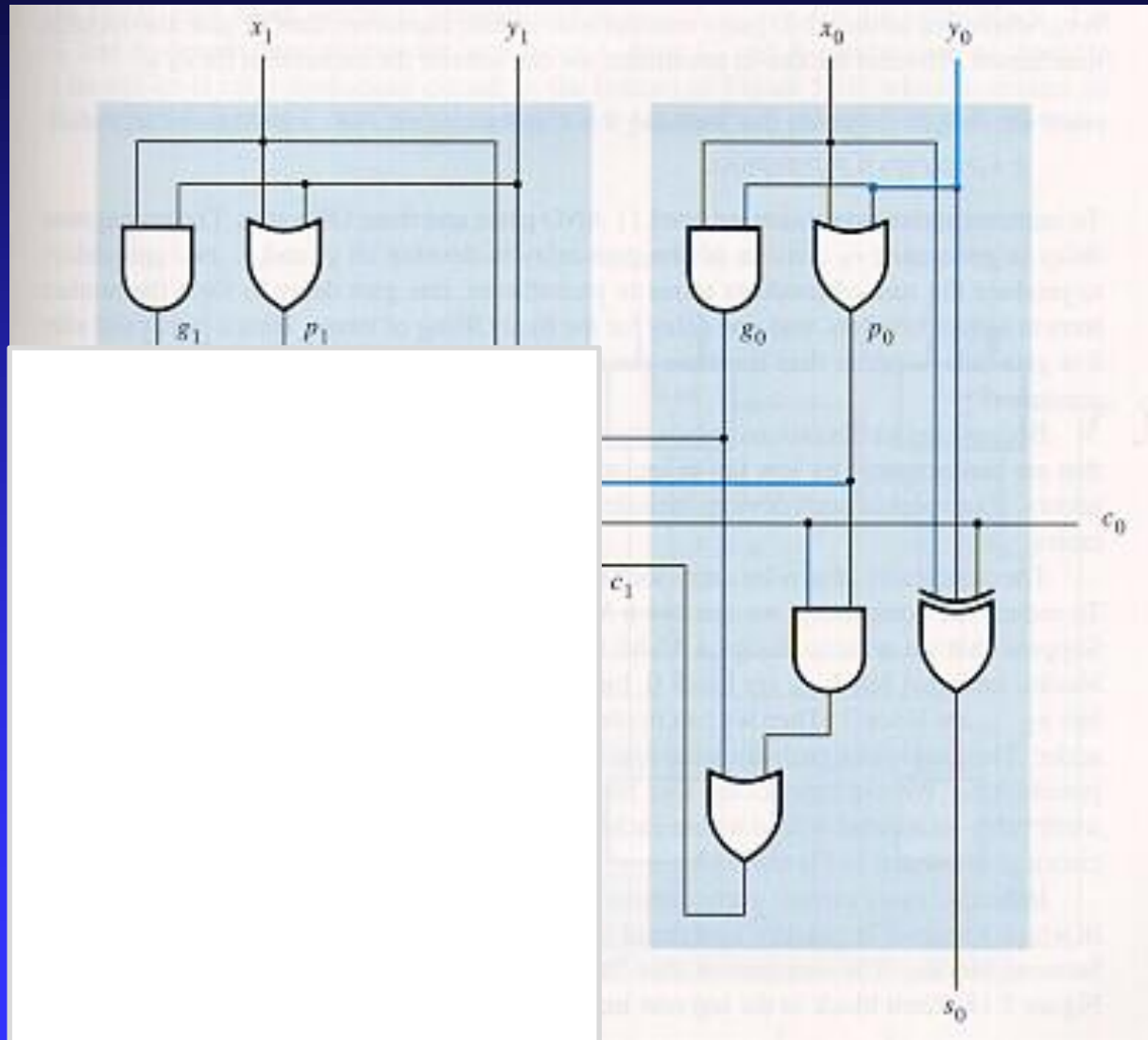

2-bit


$$s_1 = c_1 \oplus x_1 \oplus y_1$$

$$c_2 = c_0 p_0 p_1 + g_0 p_1 + g_1$$

L A A

$$g_1 = x_1 y_1$$


$$p_1 = x_1 + y_1$$

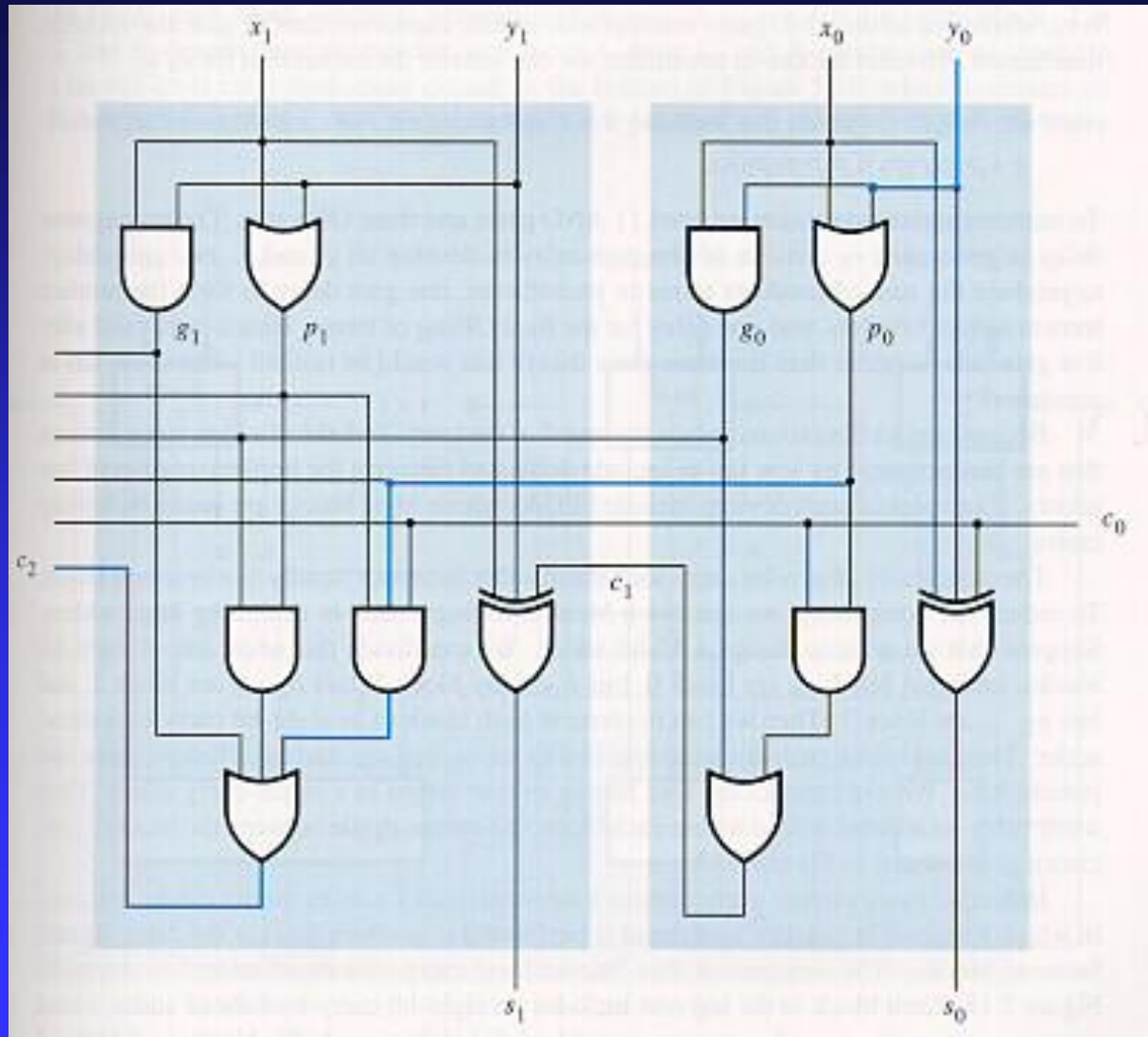

$y_0 \dots C_2$ - the longest path ...

2-bit


C
R
A

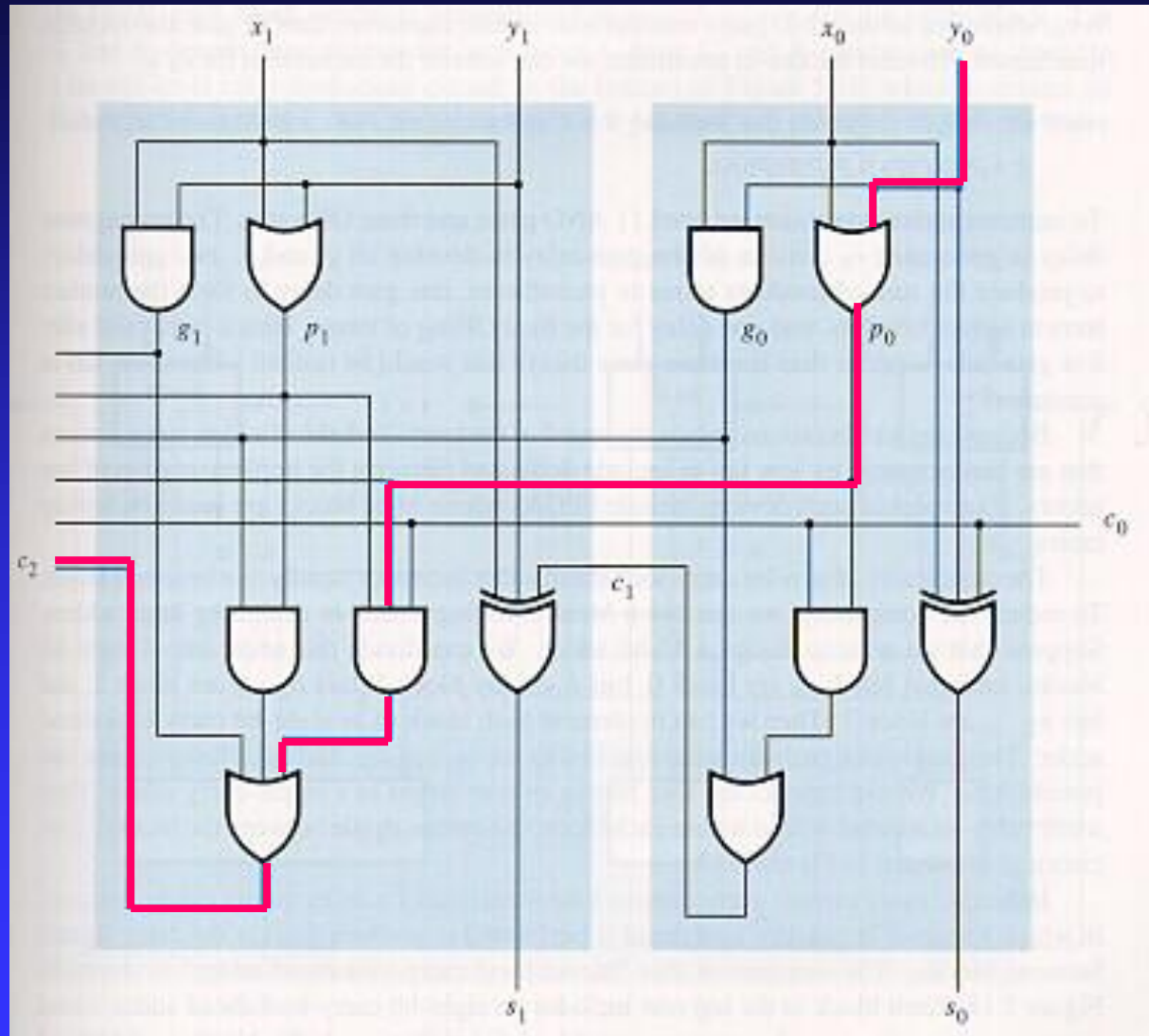

$$y_0 \dots C_2 = 8 \text{ nsec}$$

2-bit

CRA

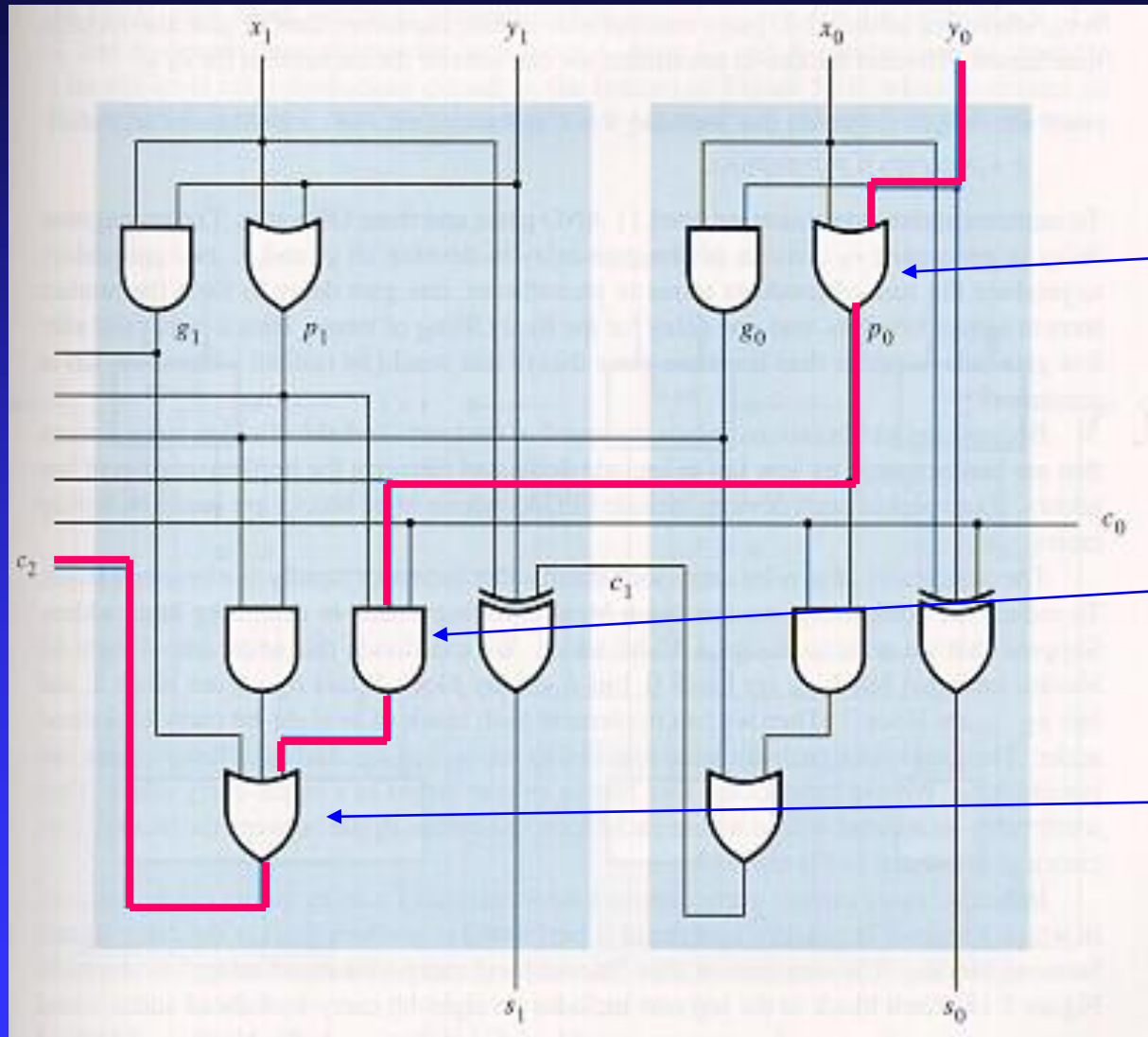

2.4

+

2.8

+

2.8

=

8.0


Comparison → 33.3%

2-bit Carry-Ripple Adder = 12 nsec


2-bit Look-Ahead Carry Adder = 8 nsec

LAA has an extra gate than CRA; but LAA is 33.3% faster than CRA


CRA

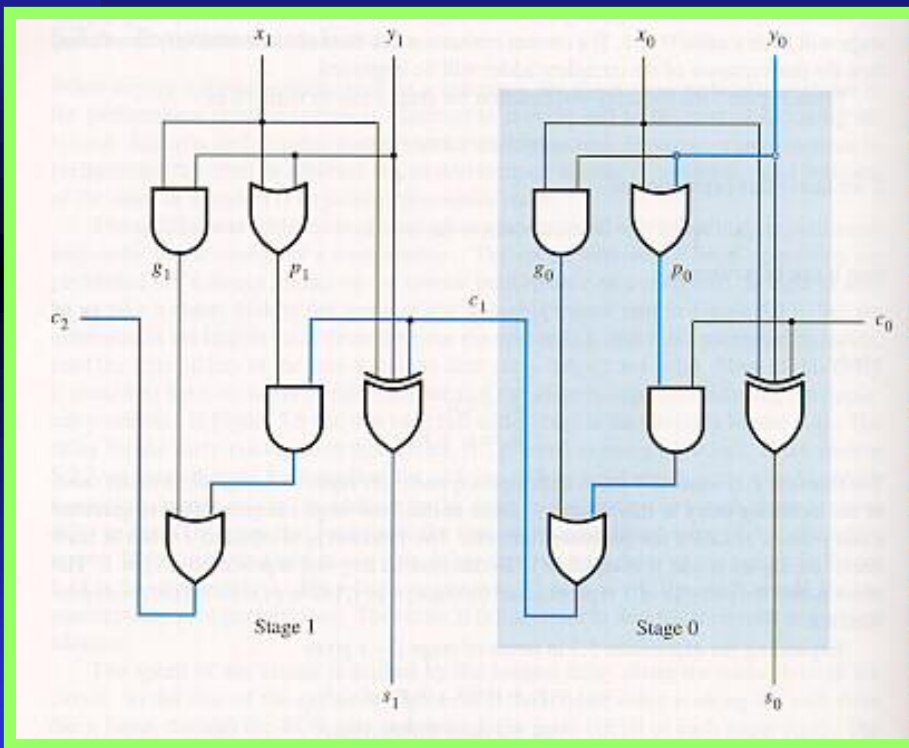


LAA

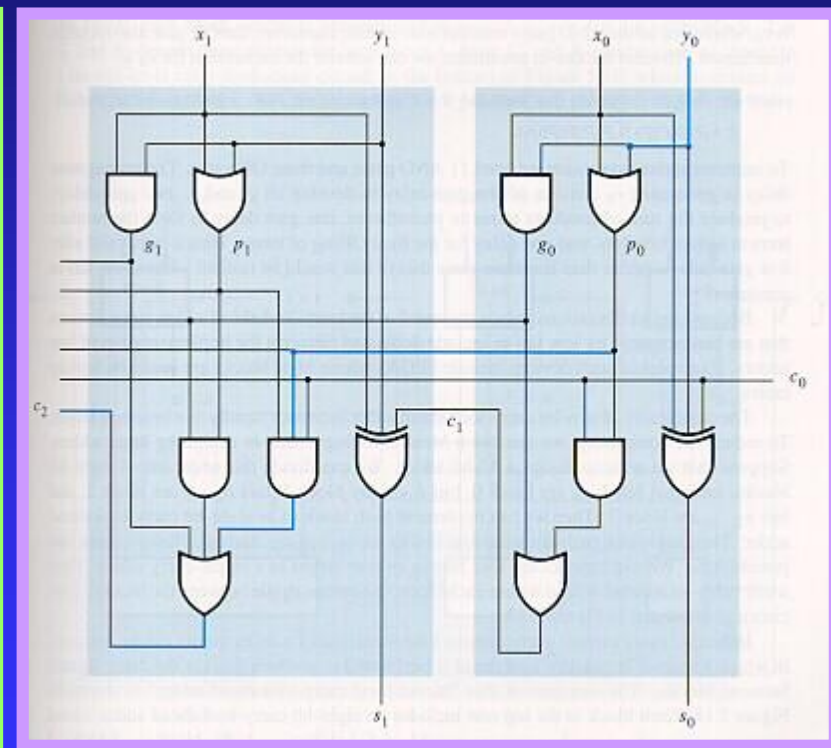

VHDL ... LAA

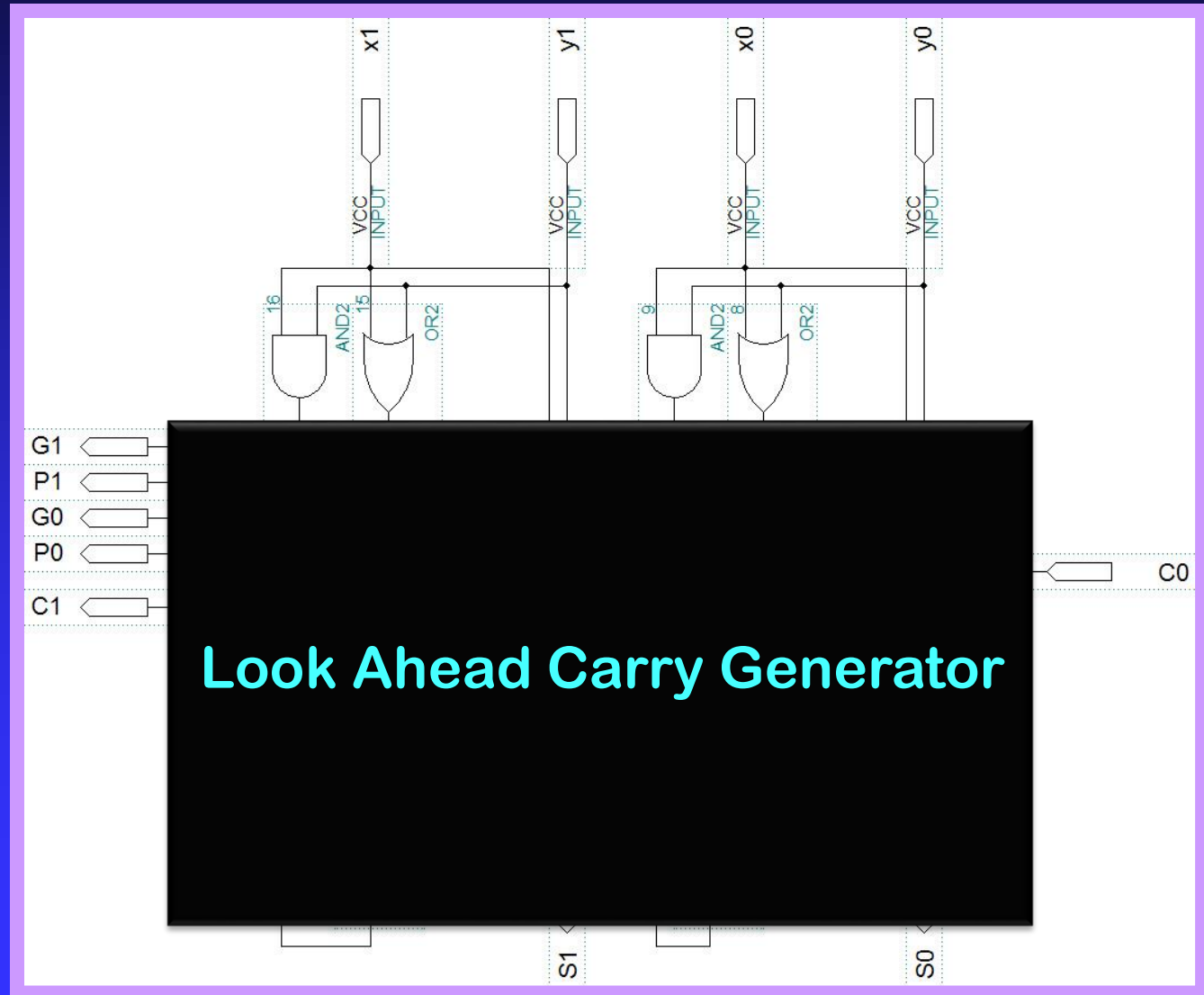


VHDL ... LAA

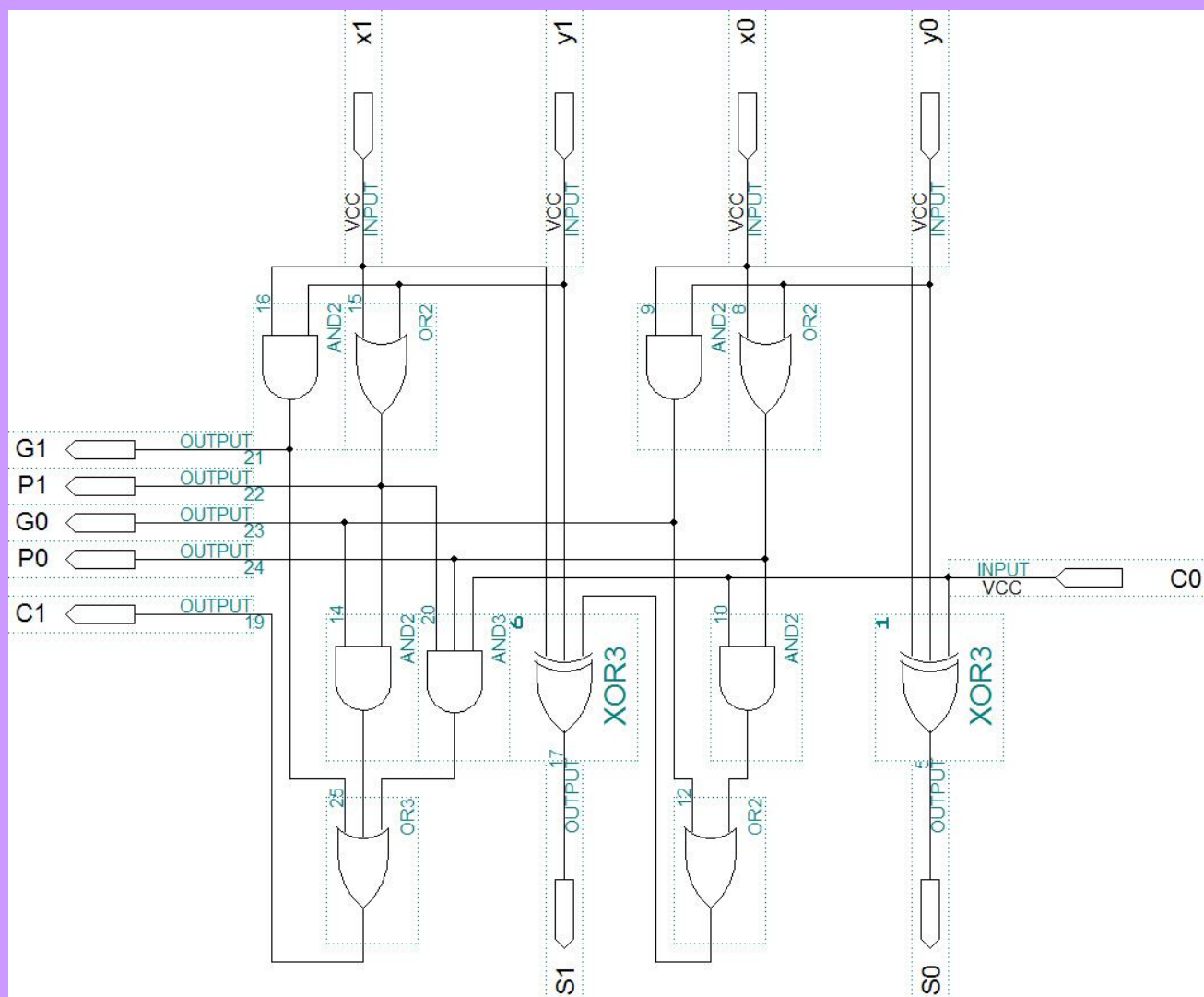


LAA limitation ..

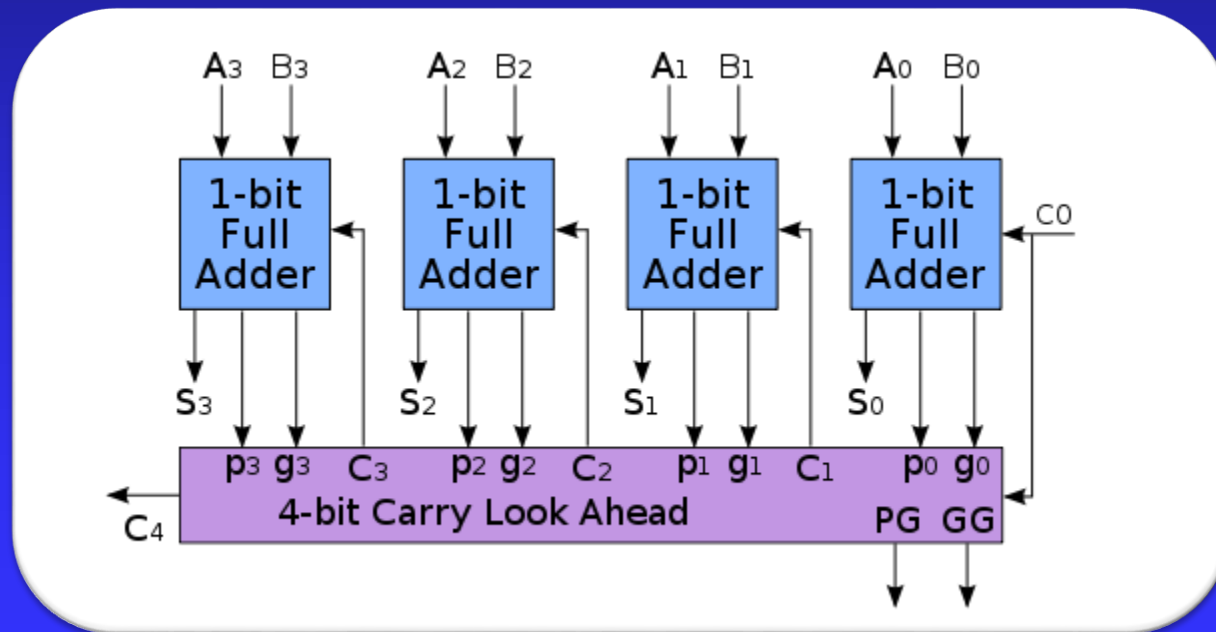- LAA cannot go beyond 4 bits of look-ahead




16-bit LAA

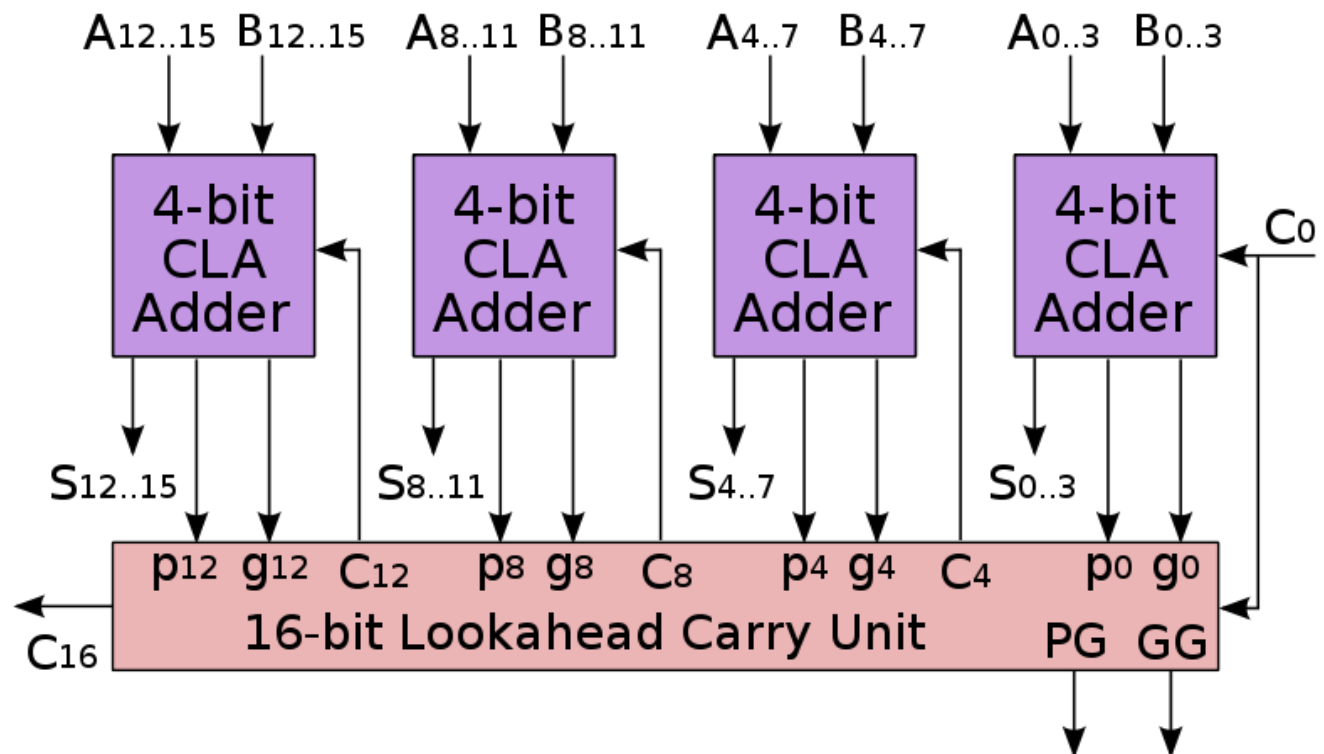- For a 16bit LAA, 4x4 LAA's should be used




64-bit LAA

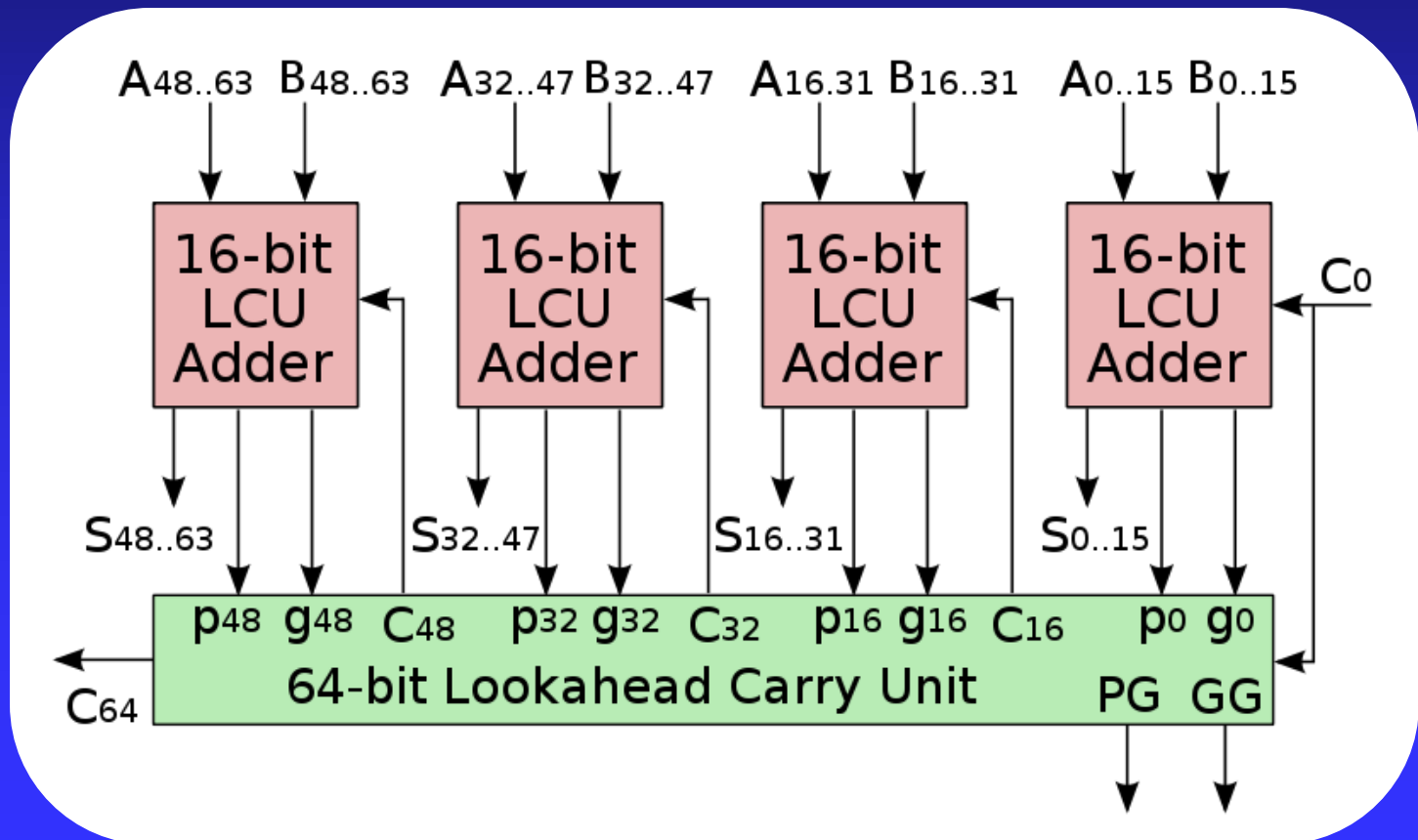- For a 64 bit LAA, 16x4 LAA's should be used



Adder part of the ALU

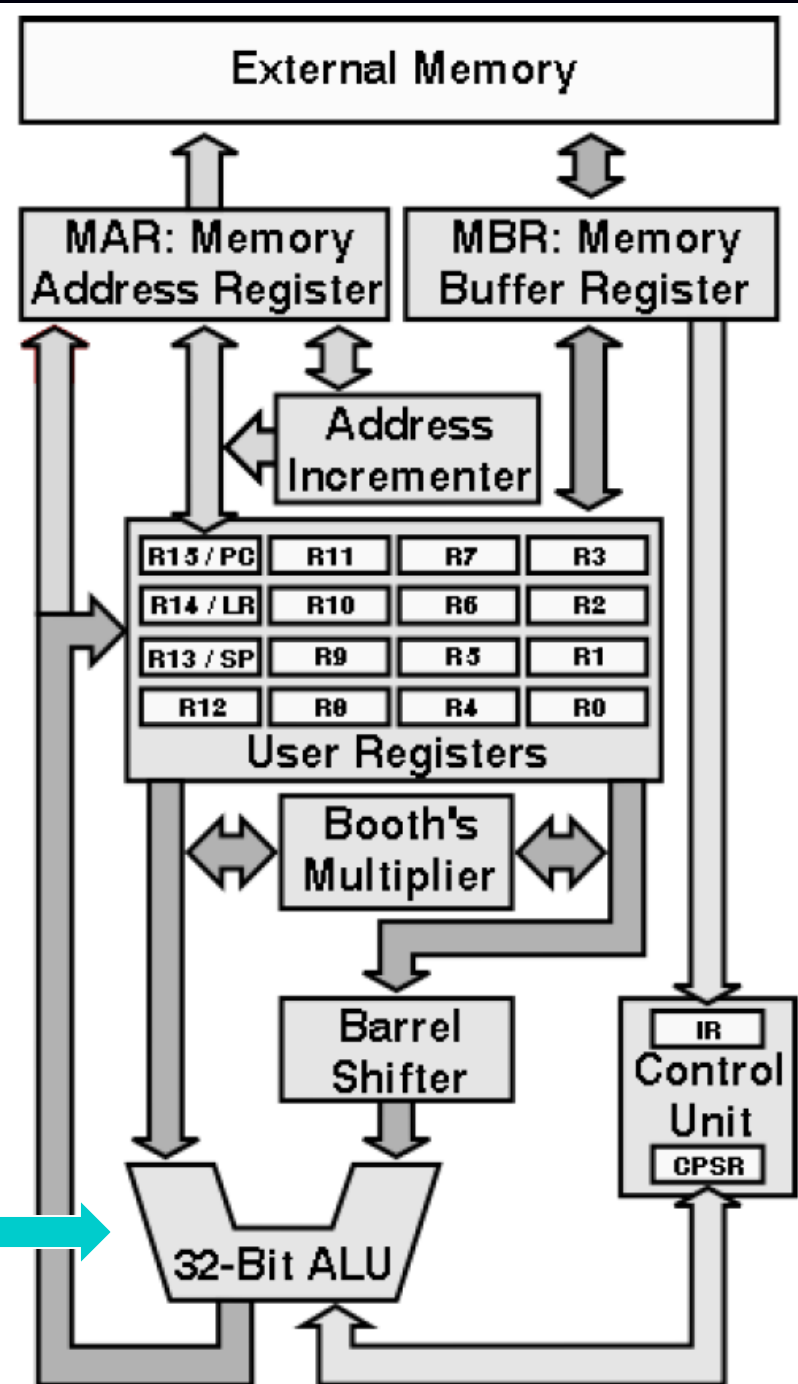

We will design ALU's

