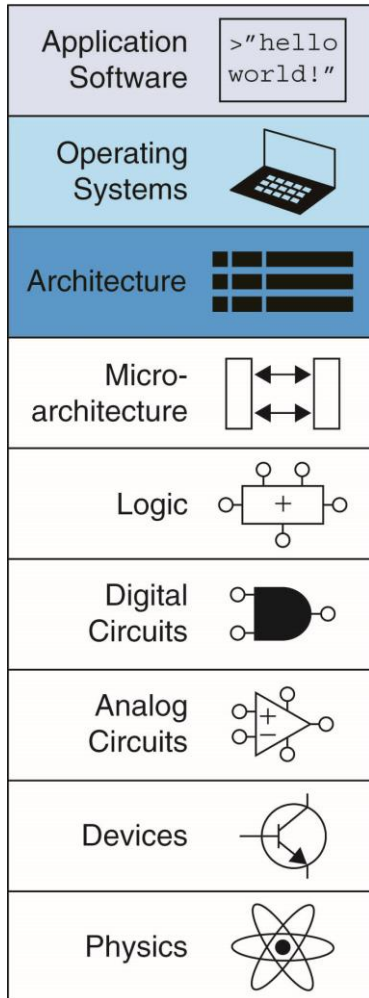


# Microarchitecture

*MIPS*

# Computer Architecture/Microarchitecture




**Architecture:** the programmer's view of the computer

- Defined by instructions (operations) and operand locations


**Microarchitecture:** how to implement an **architecture** in hardware

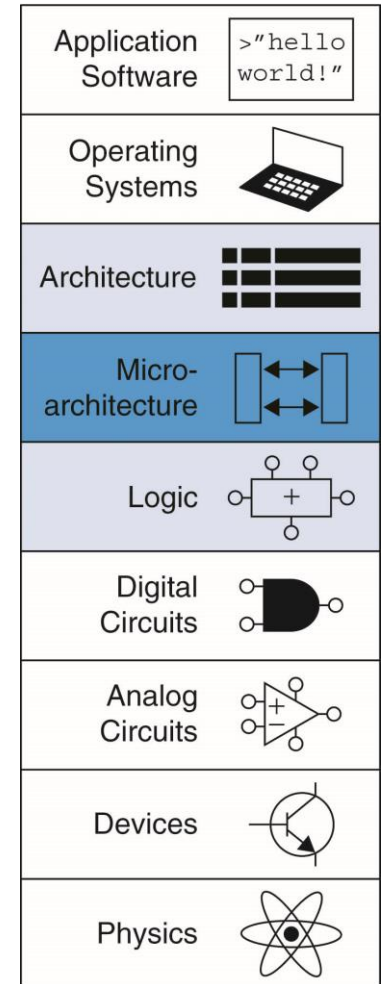- The microarchitecture is built out of "logic" circuits and memory elements




# Computer System Architecture (CPU)



---

 


# Computer System Architecture (CPU)

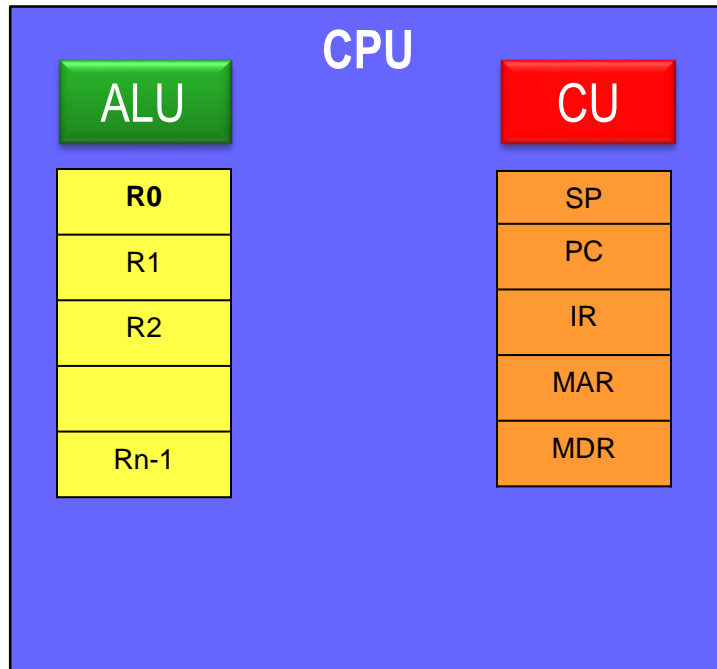


# Computer System Architecture (CPU+M)

 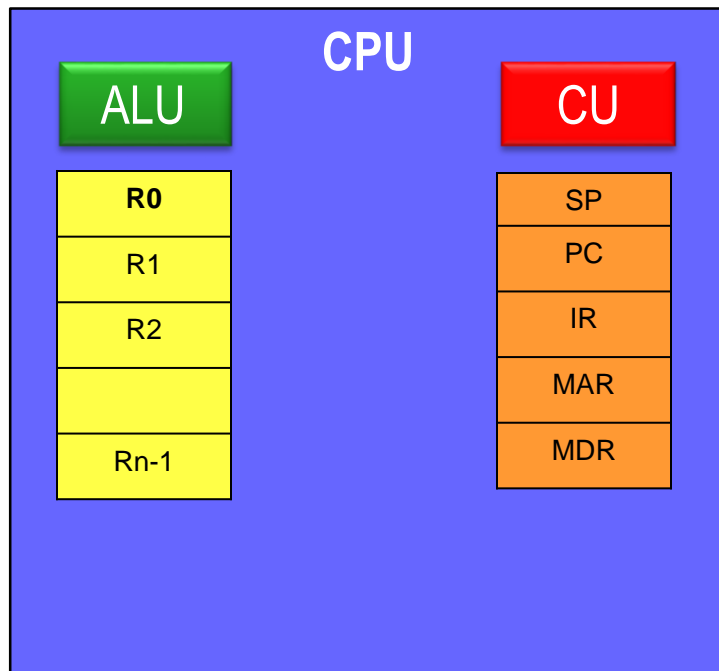



# Computer System Architecture

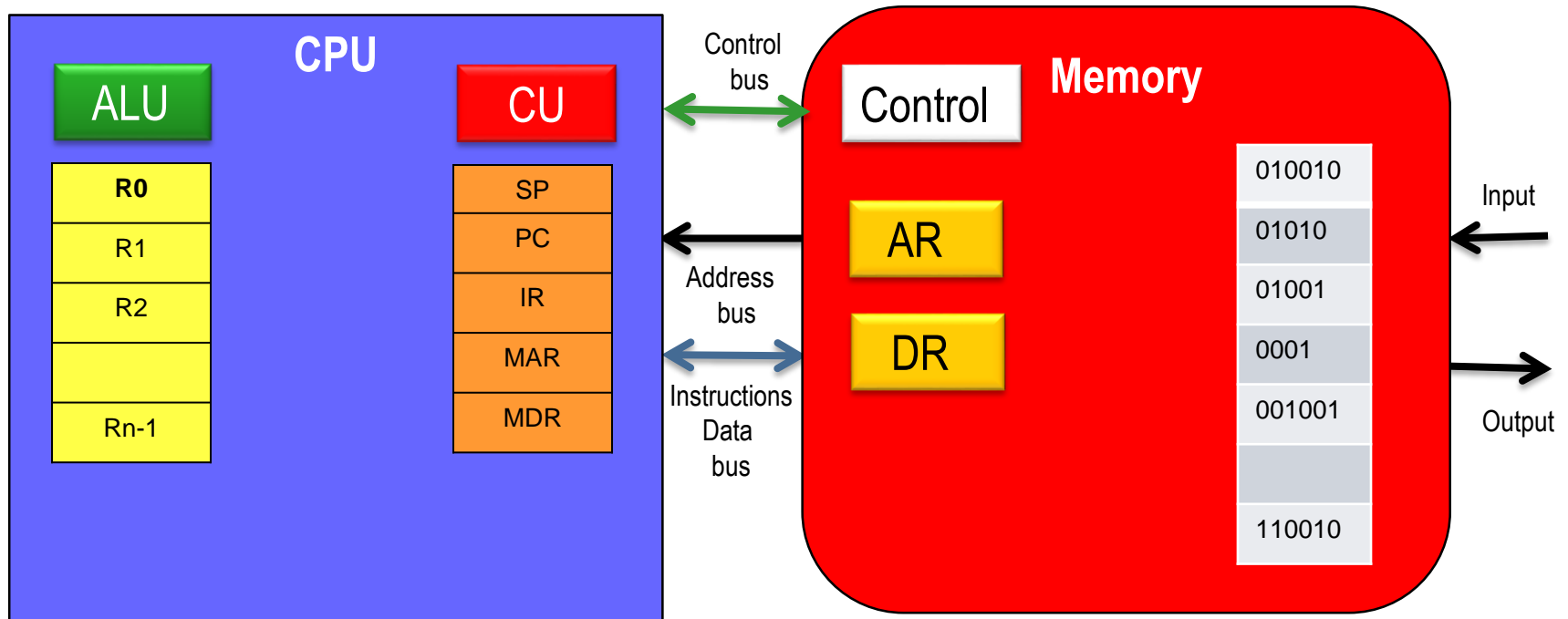

# Buses

 


M68000

 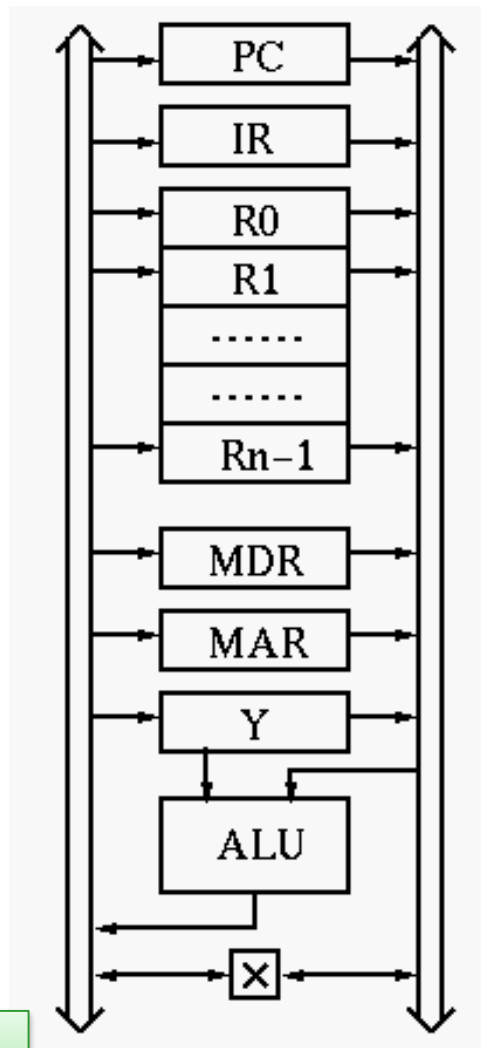


MIPS

## ARM®

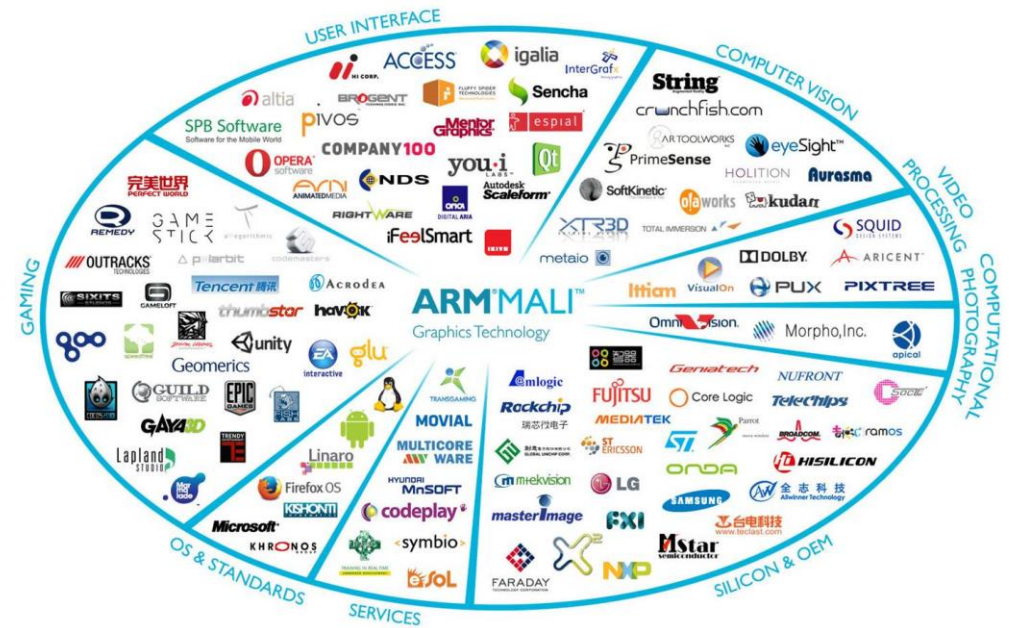



# MIPS Architecture

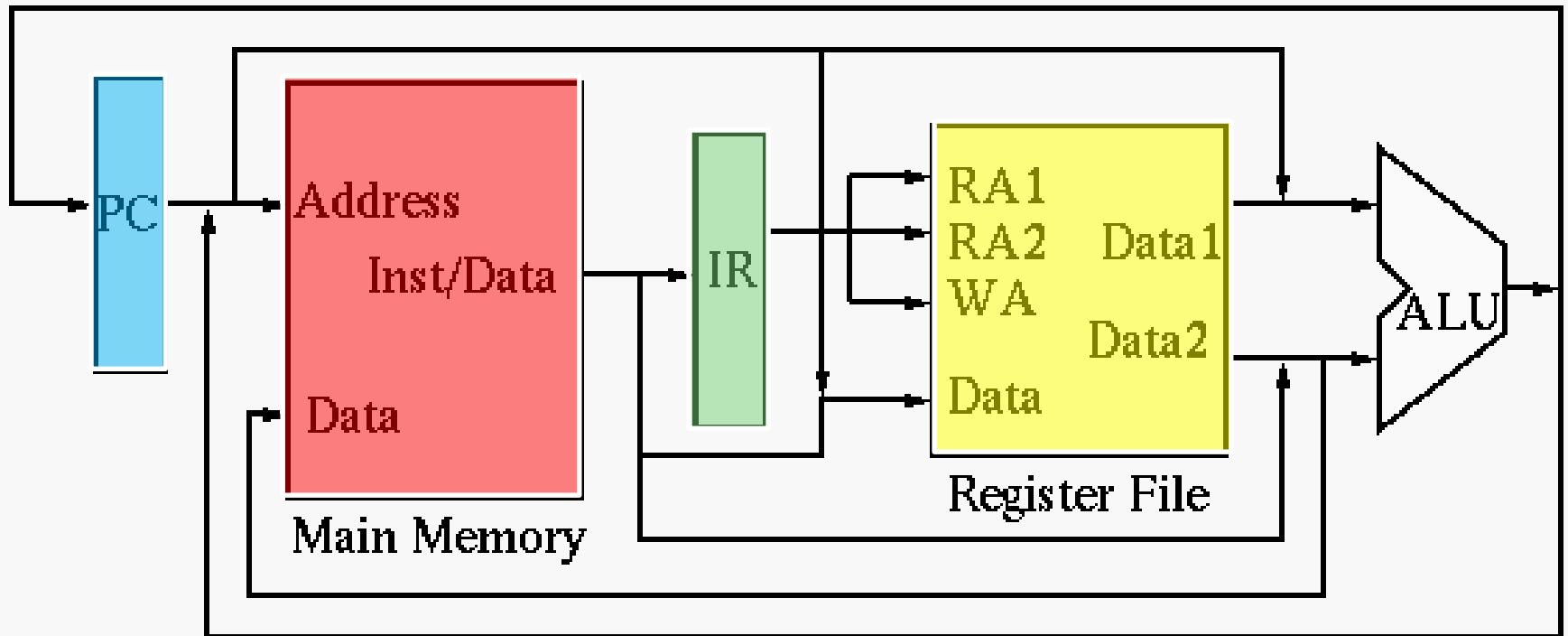


# Components of the MIPS System

---

- DataPath (Registers ... ALU)
  - Major functional hardware components (connected with buses)
- Control Unit
  - Controls the hardware components of the dataPath
  - Control signals (sent to hardware components)
  - Condition signals (receives from the components)
  - Selects the MUX lines to switch between buses
- Memory
- I/O

# Components of the MIPS System

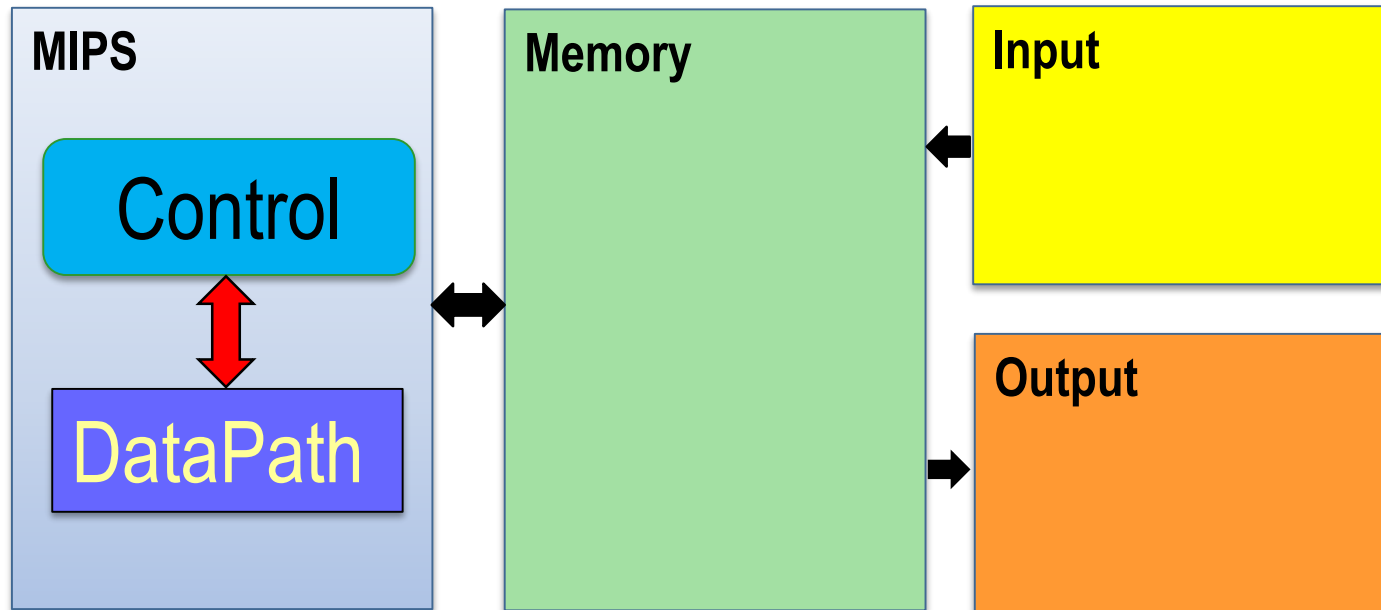

# DataPath components and Memory


---

- Program Counter (PC)
- Instruction-Register (IR)
- Register-File (RegF)
- Arithmetic Logic Unit (ALU)
- Memory
  - Instruction memory (IM)
    - Stores the machine-code program
  - Data memory (DM)
    - Stores data
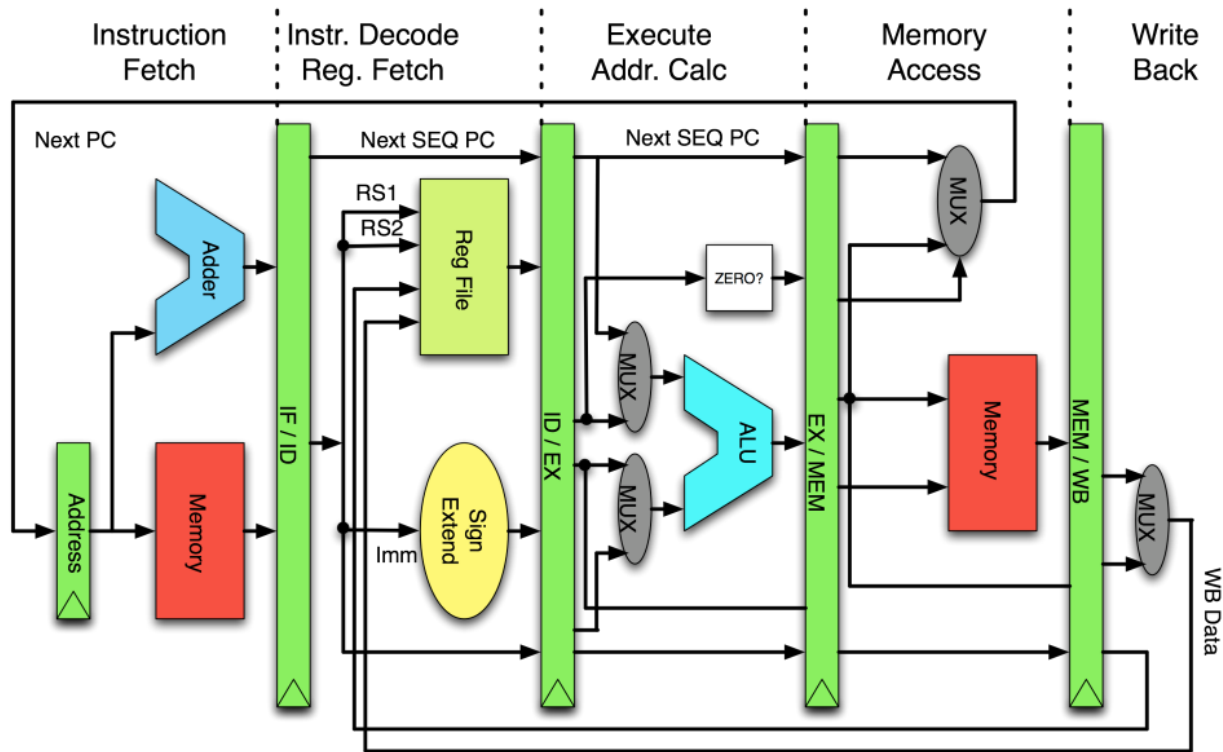
# DataPath and Control Unit

---

- DataPath; It is the path of instructions and data in the Microprocessor
- DataPath hardware follows the cycle:
  1. Fetch Instruction
  2. Decode
  3. Execute
  4. Memory Access
  5. Write-back
- Control Unit
  - Controls the DataPath hardware




# MIPS Processor

Microprocessor without Interlocked Pipeline Stages


5 Cycles
 
# Microarchitecture

- **Single-Cycle**: each instruction executes in a single CPU cycle
- **Multiple-Cycle**: each instruction is broken into series of shorter steps
- **Pipelined**: each instruction broken up into series of steps & multiple instructions execute at once:




# Single Cycle CPU

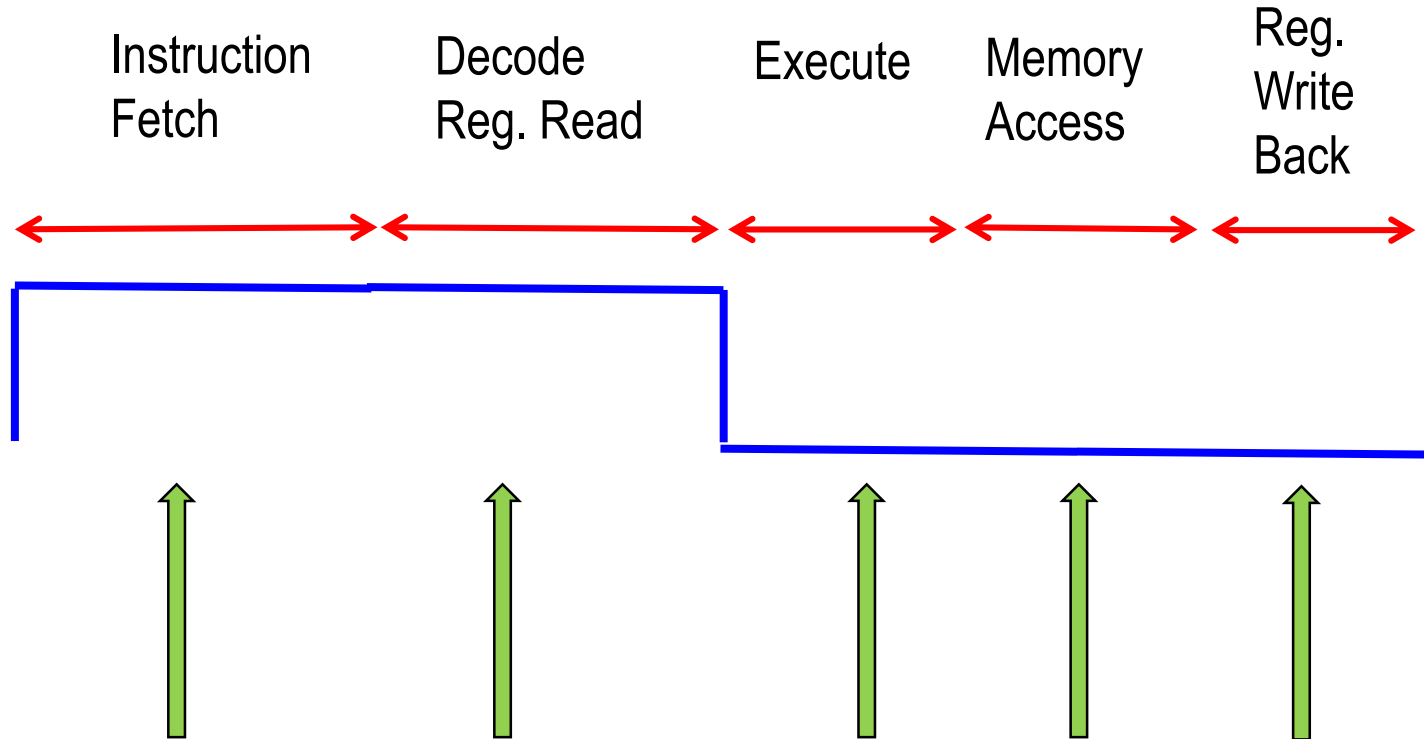

Each **instruction** executes in a **single cycle**





# Multiple Cycle

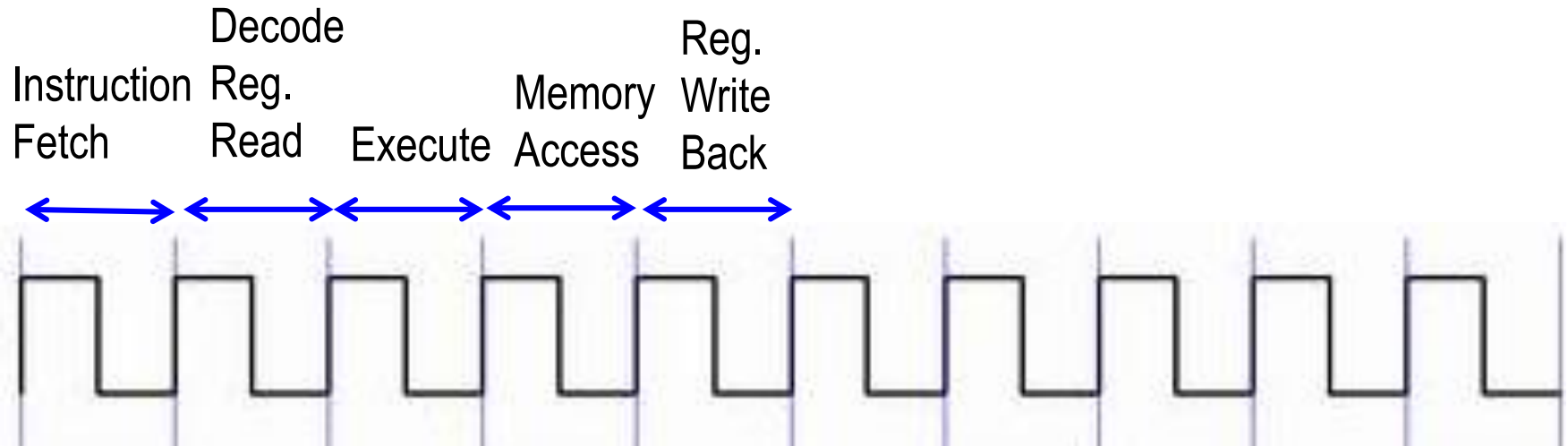

Only one stage of instruction per clock cycle

# Multiple and Single Cycle

  


# Combinational and State logic elements

---


- Combinational
  - $\mathcal{F}$  [logic inputs]
  - (gates)
- State
  - $\mathcal{F}$  [logic Inputs, time (state)]
  - (flip-flops)

# State elements of MIPS Processor

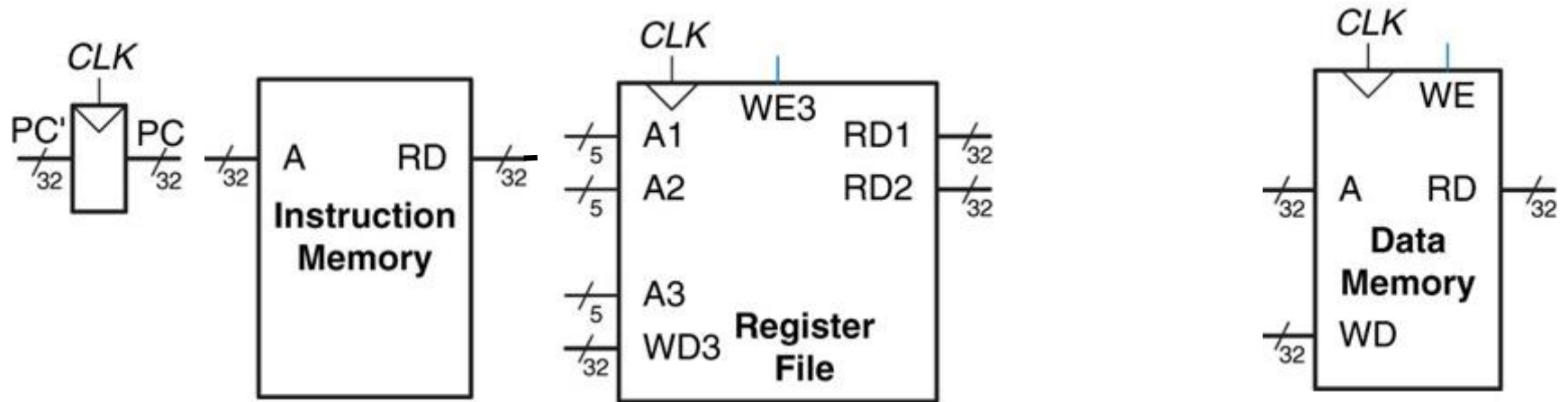
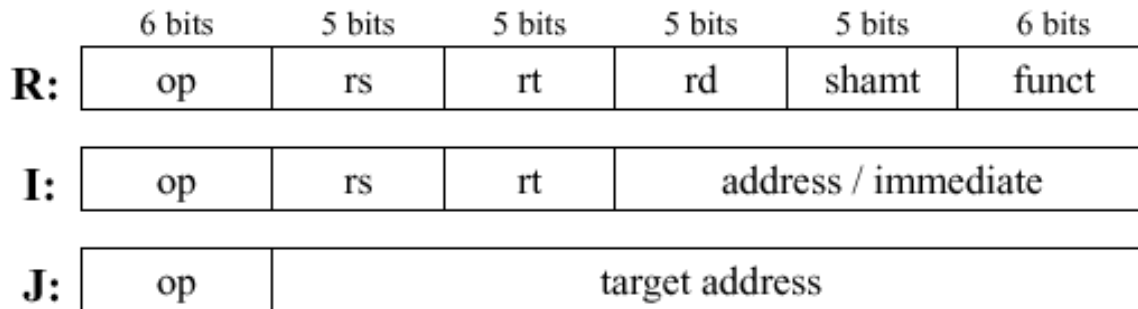
# MIPS Instructions types

- R-Type: Register operands
- I-Type: Immediate operand
- J-Type: for Jumping



op: basic operation of the instruction (opcode)

rs: first source operand register

rt: second source operand register

rd: destination operand register


shamt: shift amount

funct: selects the specific variant of the opcode (function code)

address: offset for load/store instructions ( $\pm 2^{15}$ )


immediate: constants for immediate instructions

# Instruction Fetch

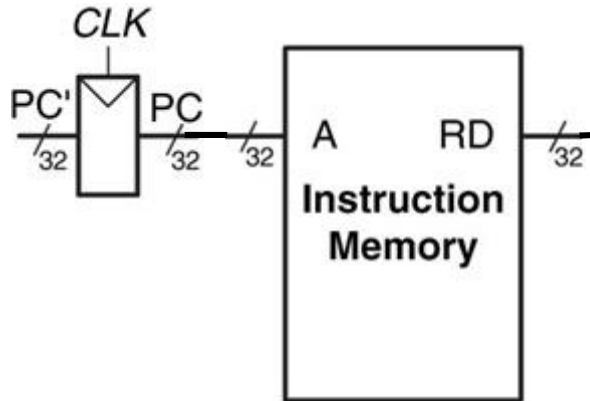

Program Counter (PC) Register stores the address of the next instruction

# Instruction Fetch

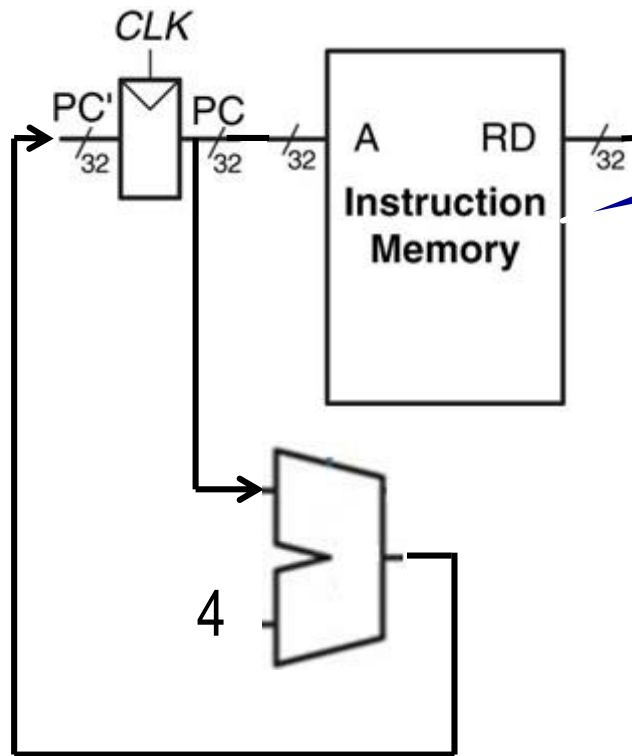

Instruction: [ Instruction Register: Holds the instruction currently being processed (decoded) ]


```
3      .data
4  Array: .space 8
5      .text
6      #-----
7      la $t0, Array
8      #-----
9      li $t1, 5
10     sw $t1, 0($t0)
11     li $t1, 6
12     sw $t1, 4($t0)
13     #-----
14     lw $t2, 0($t0)
15     move $a0, $t2
16     li $v0, 1
17     syscall
18
19     lw $t3, 4($t0)
20     move $a0, $t3
21     li $v0, 1
22     syscall
23     #-----
24     li $v0, 10
25     syscall
26
```

The address of the next instruction is:  $PC + 4$

$(32/8 = 4)$

# R-Type Arithmetic/Logic Instructions

6 Fields	Opcode	src reg 1	src reg 2	dst reg	shamt	funct
# bits	6 (31-26)	5 (25-21)	5 (20-16)	5 (15-11)	5 (10-6)	6 (5-0)

 

**add** rd, rs, rt


#  $r[d] = r[s] + r[t]$

**sub** rd, rs, rt

#  $r[d] = r[s] - r[t]$




# R-Type Arithmetic/Logic Operations

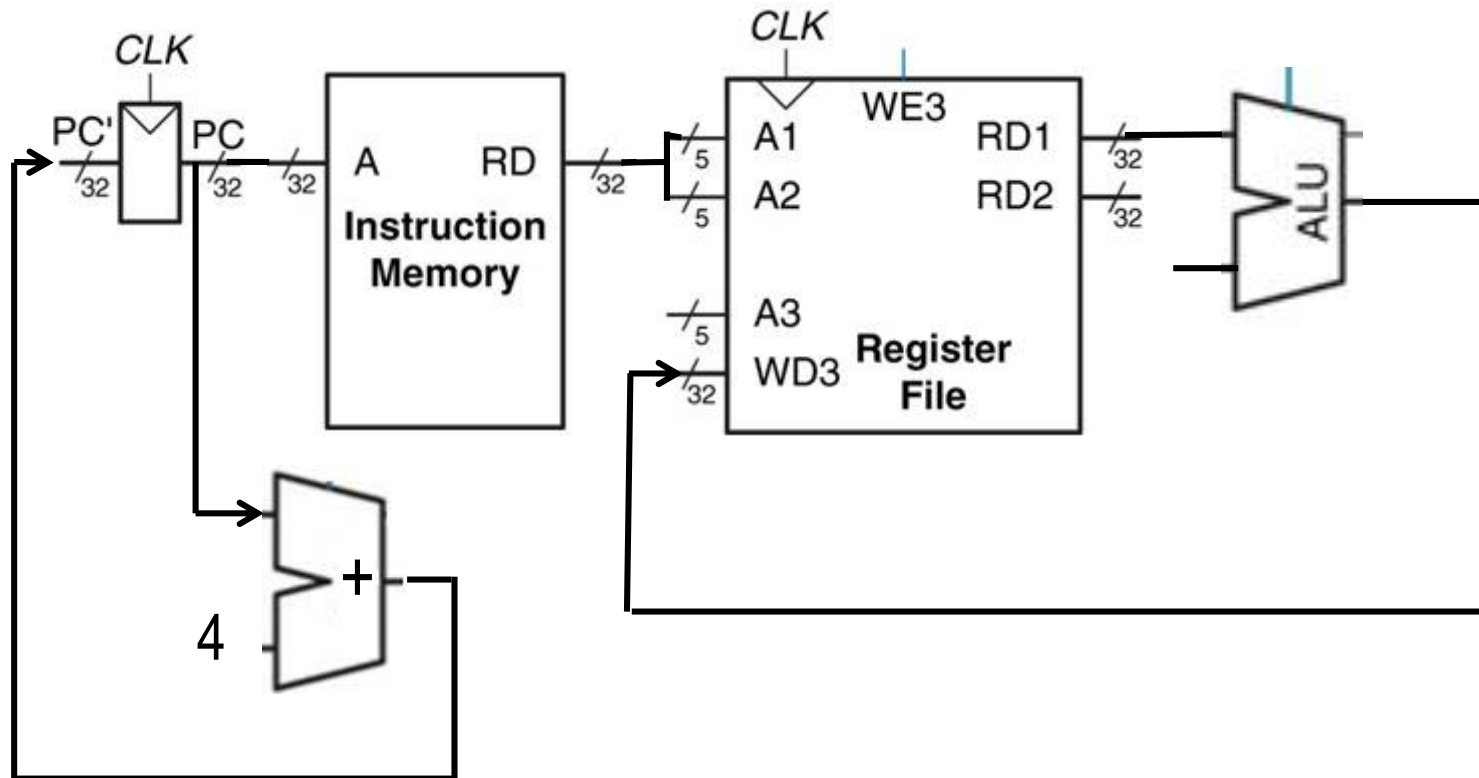


```
add rd, rs, rt  
sub rd, rs, rt
```


# Fetch

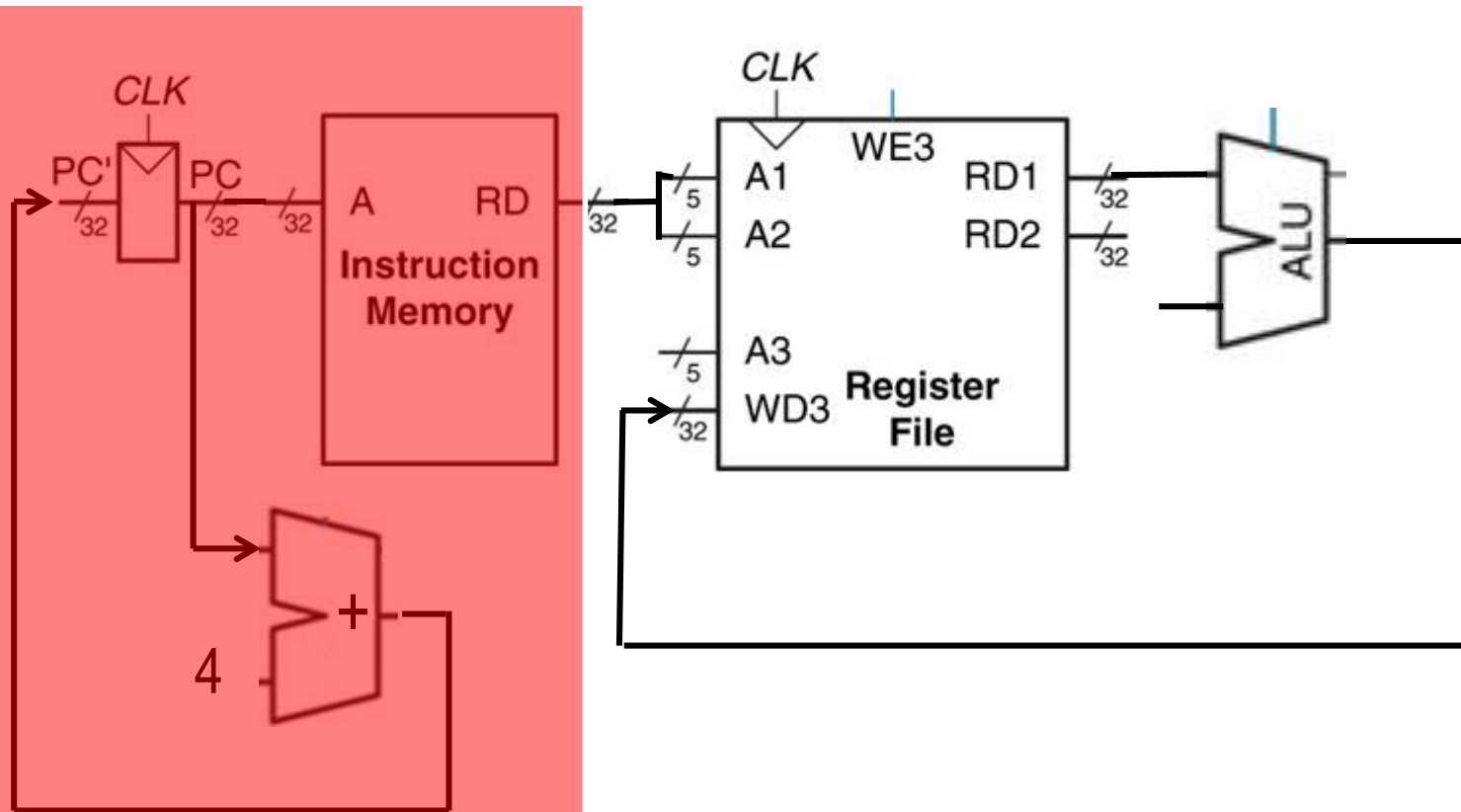


# Decode

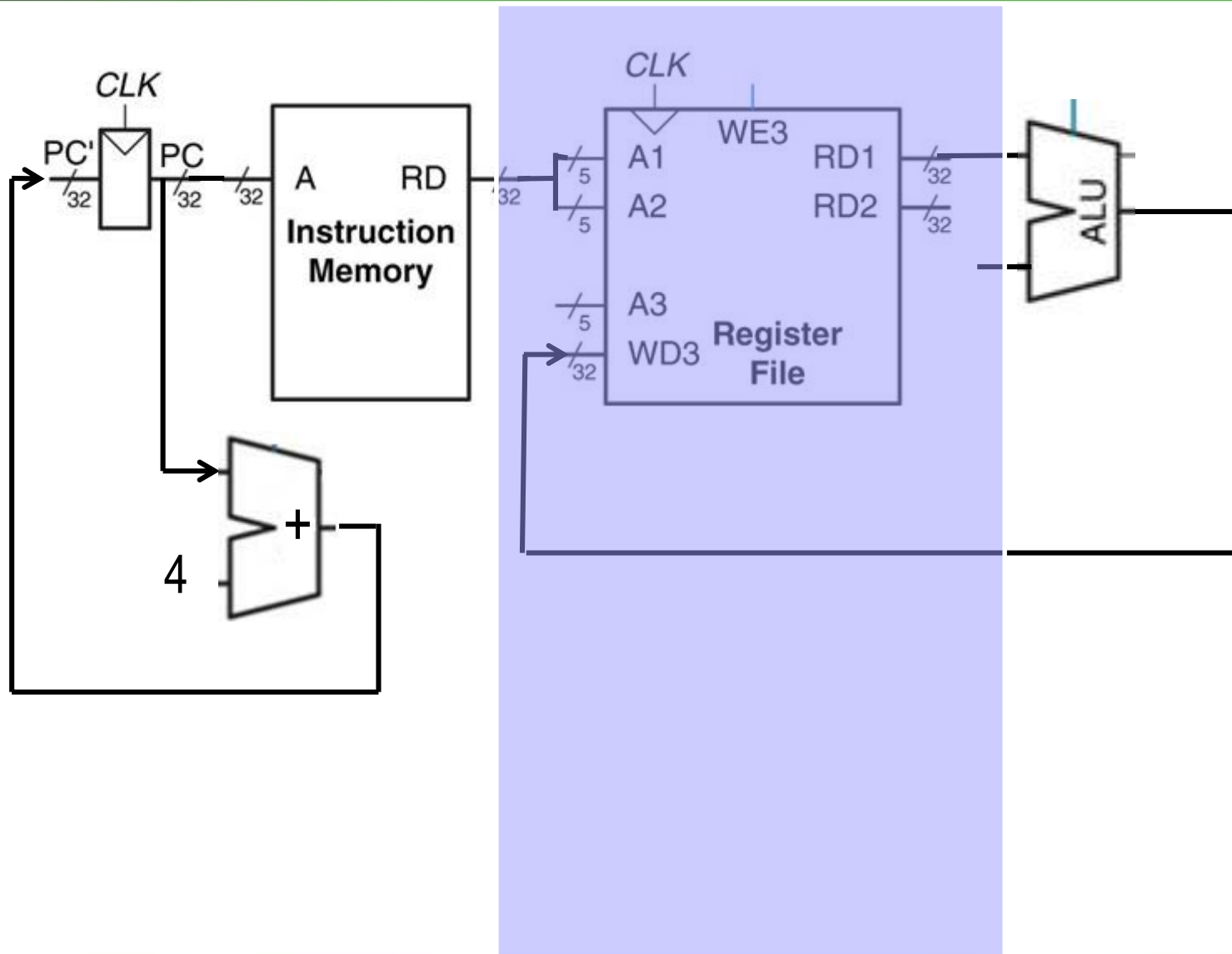

# Execute

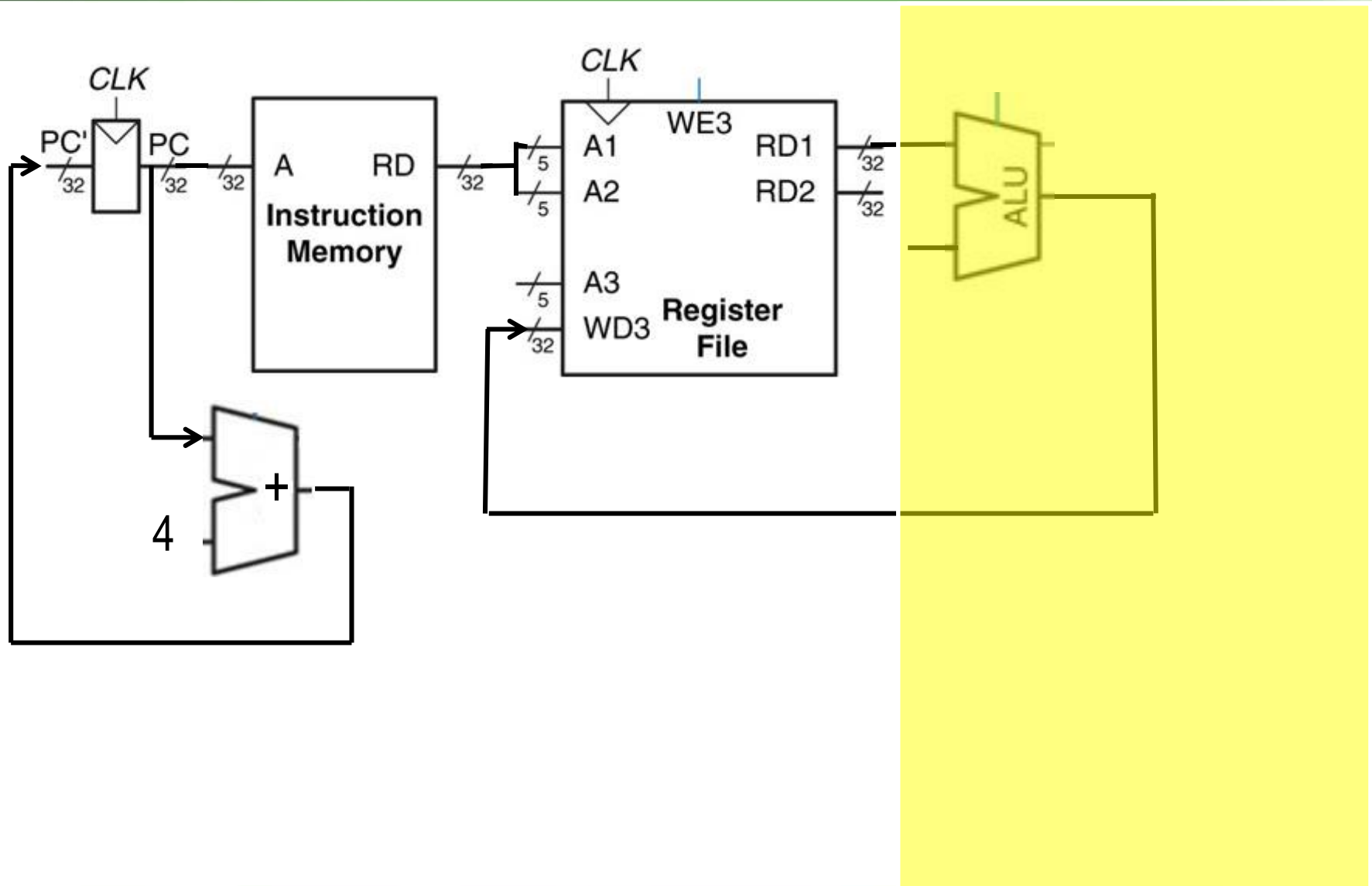


# No Memory access

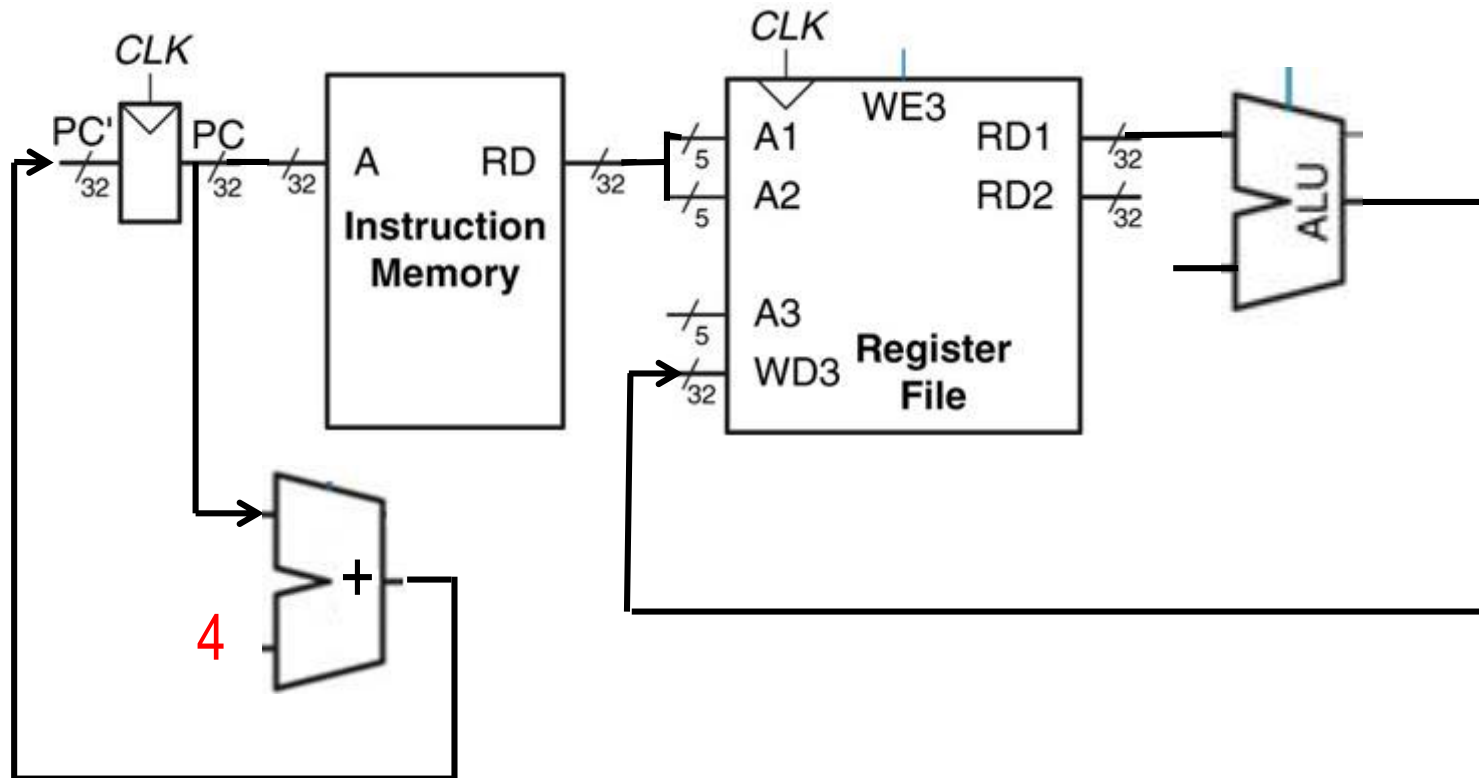

**add rd, rs, rt**

- $\text{mem}[\text{PC}]$  Fetch the instruction from memory
- $R[\text{rd}]: R[\text{rs}] + R[\text{rt}]$  The actual operation
- $\text{PC}: \text{PC} + 4$  Calculate the next instruction's address

# Write Back to Register-File

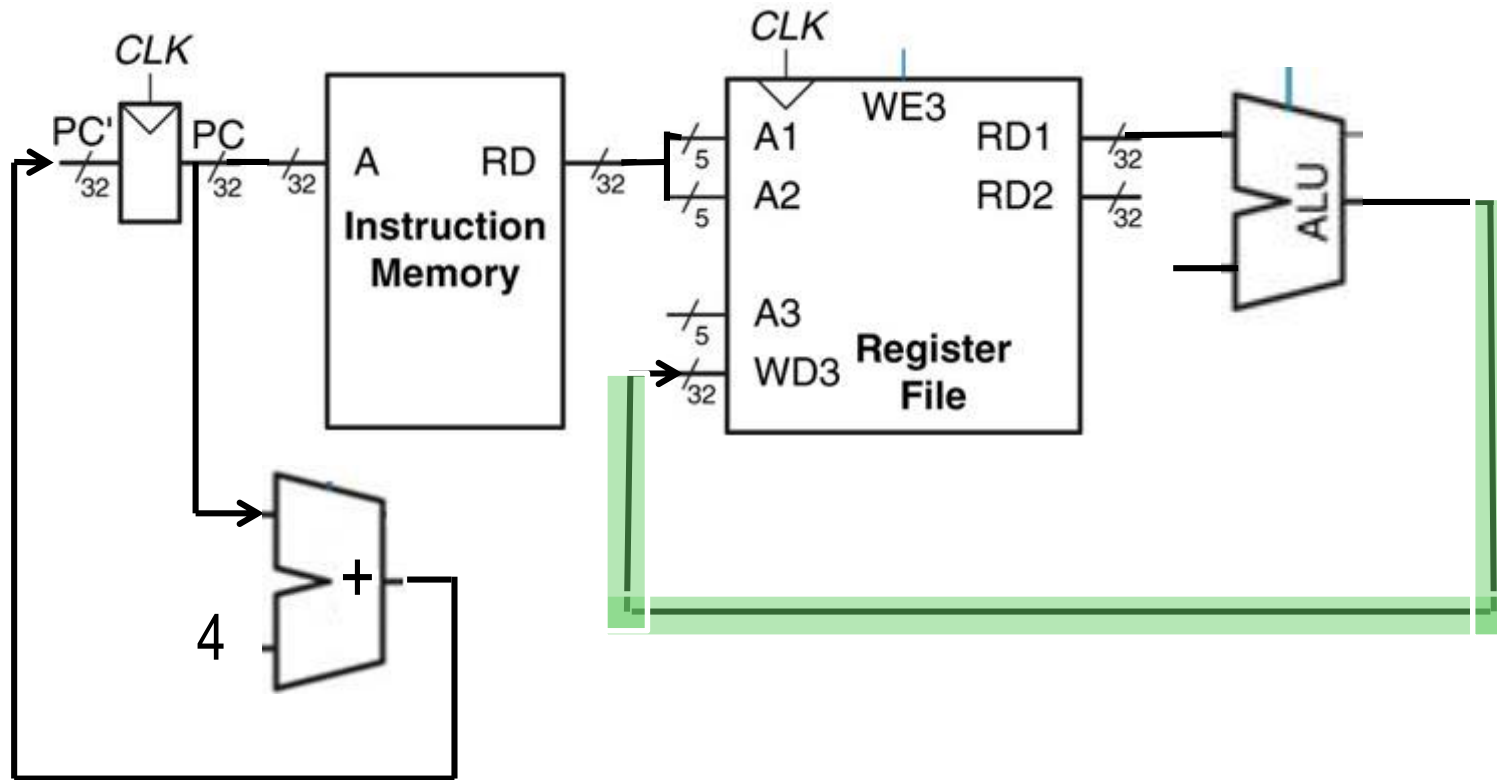


# I-type: Load and Store instructions

- Load word from Memory:


- `lw rt,rs, imm16`      # `rt = Memory[rs+offset]`
- `lw rt, imm16(rs)`

- Store word in Memory:

 - `sw rt,rs, imm16`      # `Memory[rs+offset] = rt`
- `sw rt,imm16(rs)`





**lw** **rt,rs, imm16**

 

Load (Read ) data from memory and write it back to Register-File




# Single-Cycle Datapath

  



Fetch Instruction (**lw**)

# Single-Cycle Datapath

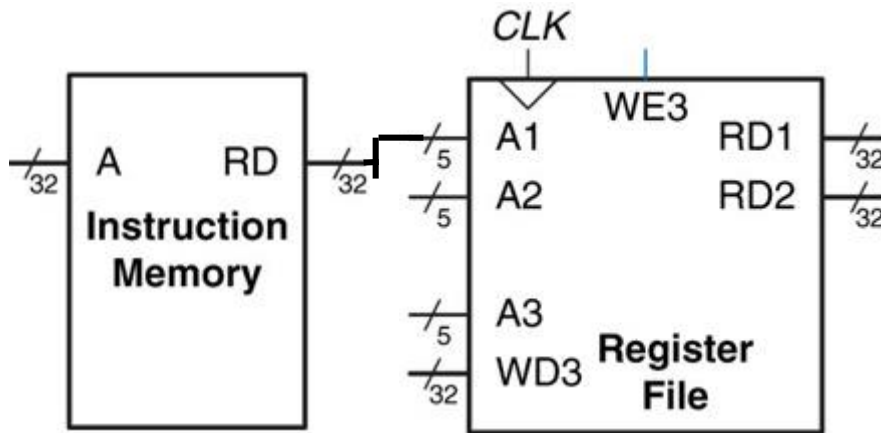


Read source operands from the **Register-File** (Register read)

# Single-Cycle Datapath

 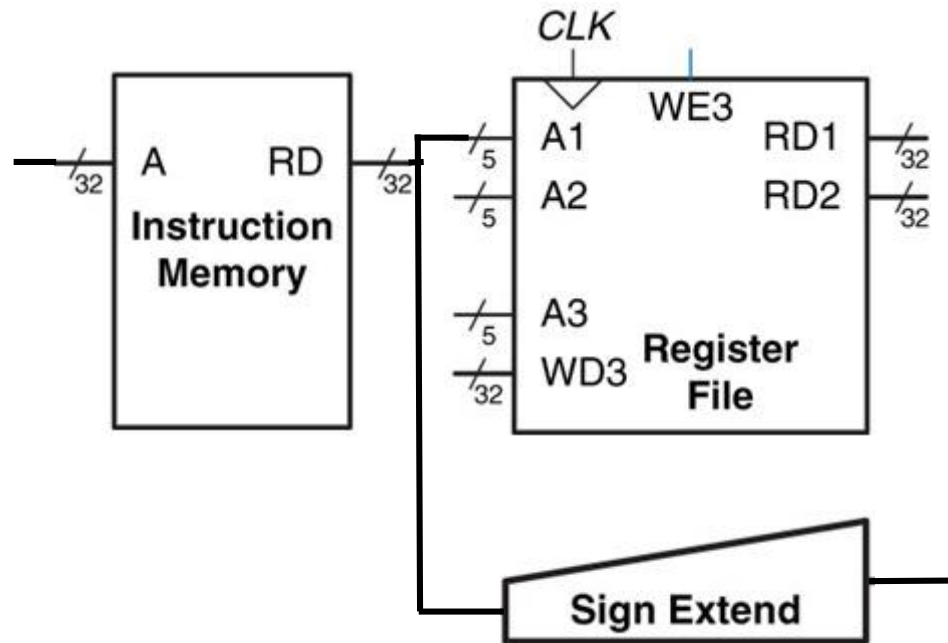


Sing-extend the immediate (**lw** Immediate)

# Single-Cycle Datapath

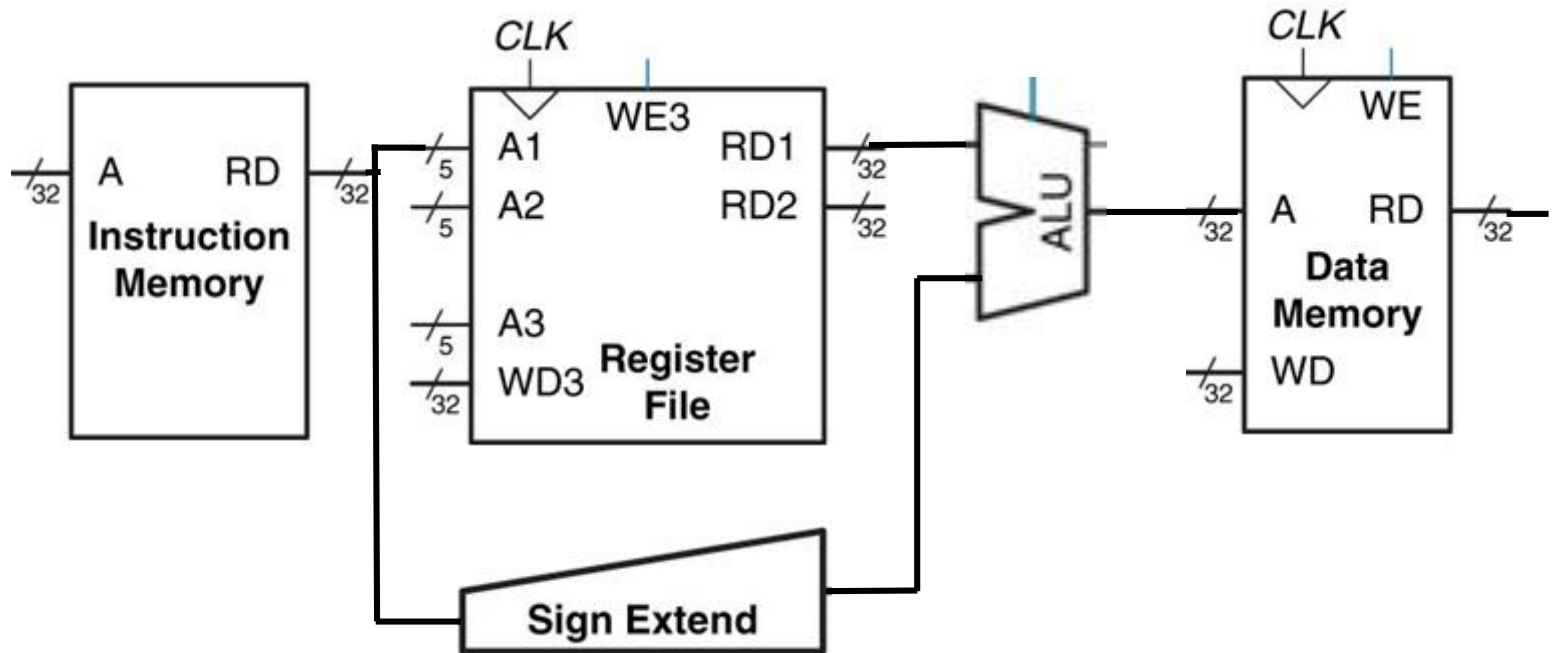


Compute the memory address (**lw** address)

# Single-Cycle Datapath

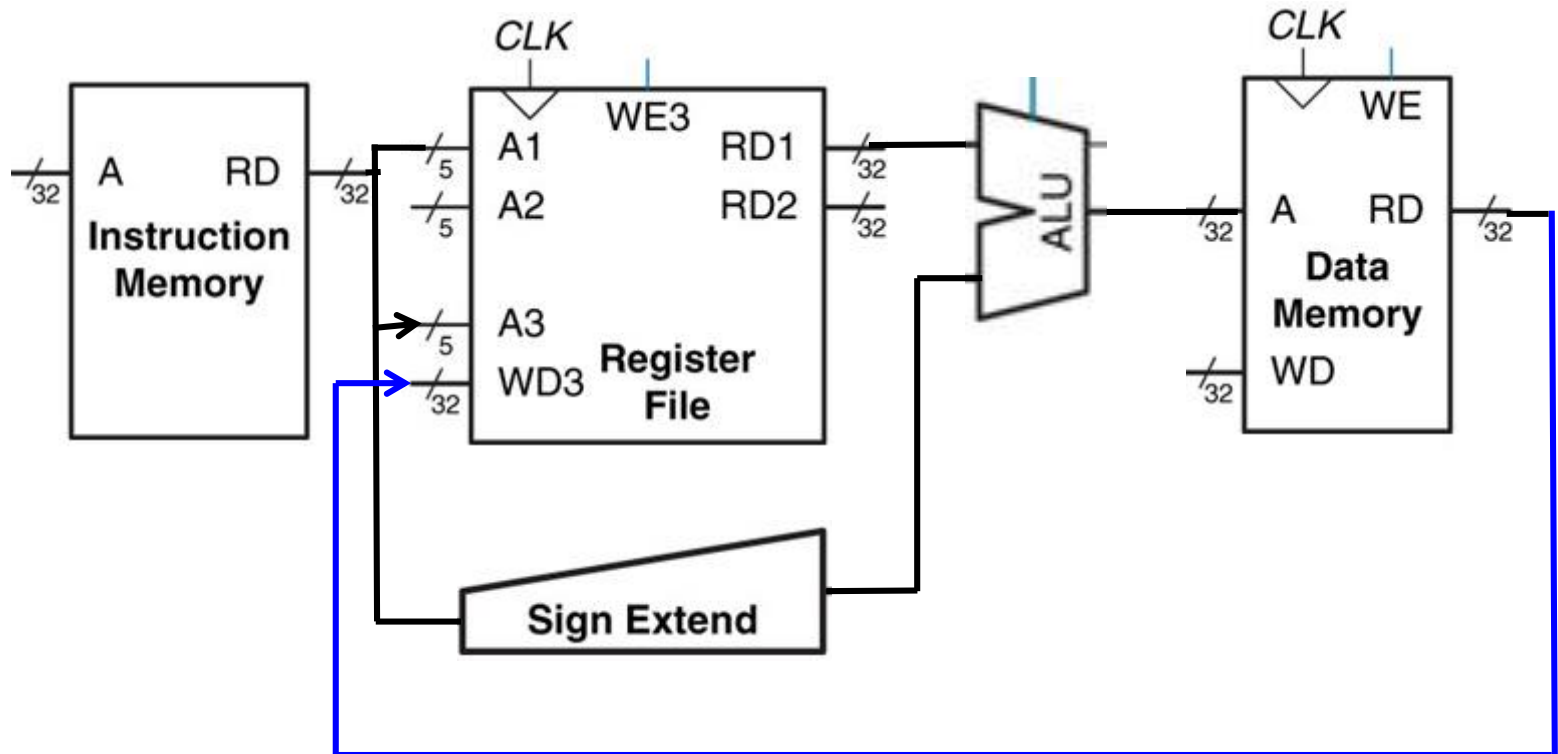

Read data from memory and write it back to Register-File (**lw** Memory Read)

# Plus the Fetch-part

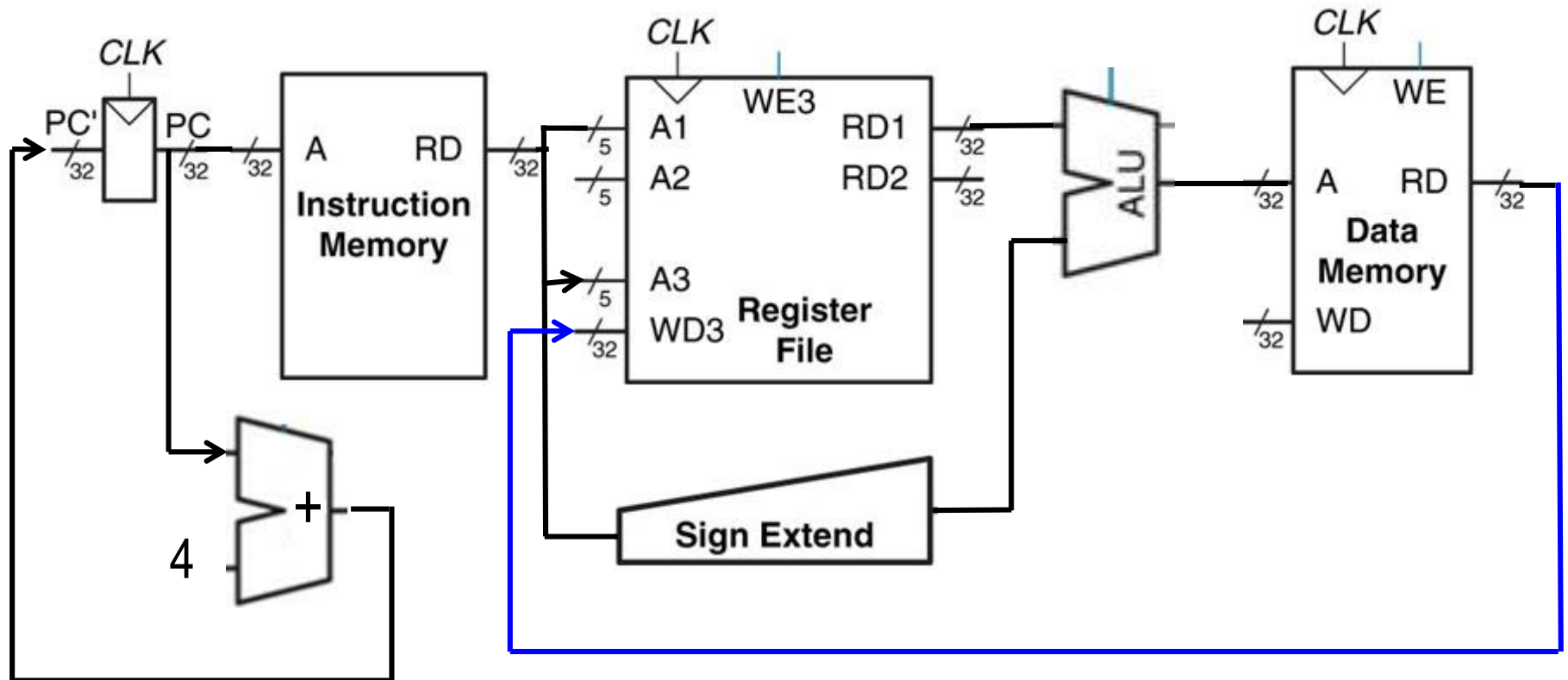


Read data from memory and write it back to Register-File (**lw** Memory Read)

# Instruction execution cycle

1. (IF): *Fetch Instruction*
2. (ID): *Decode*
3. (EX): *Execute*
4. (MEM): *Memory Access*
5. (WB): *Write-back*


- IF; **I**nstruction **F**etch machine code retrieved from memory
- ID; **I**nstruction **D**ecode set control signals, load source registers
- EX; **E**xecute Perform ALU operation
- MEM; **M**emory Read/write from/to memory
- WB; **W**rite-**B**ack Result written back into register file

# Fetch instruction

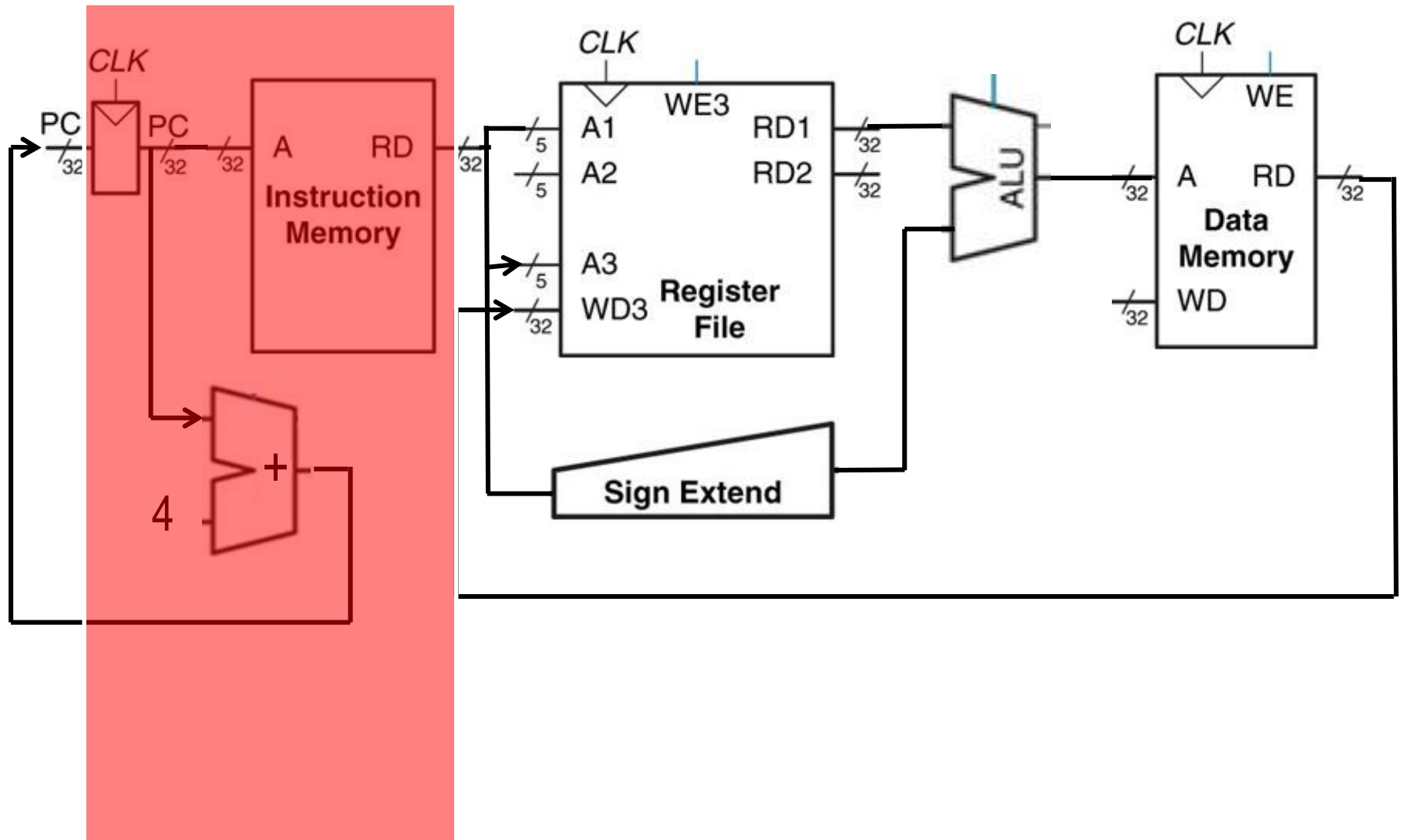





# Decode

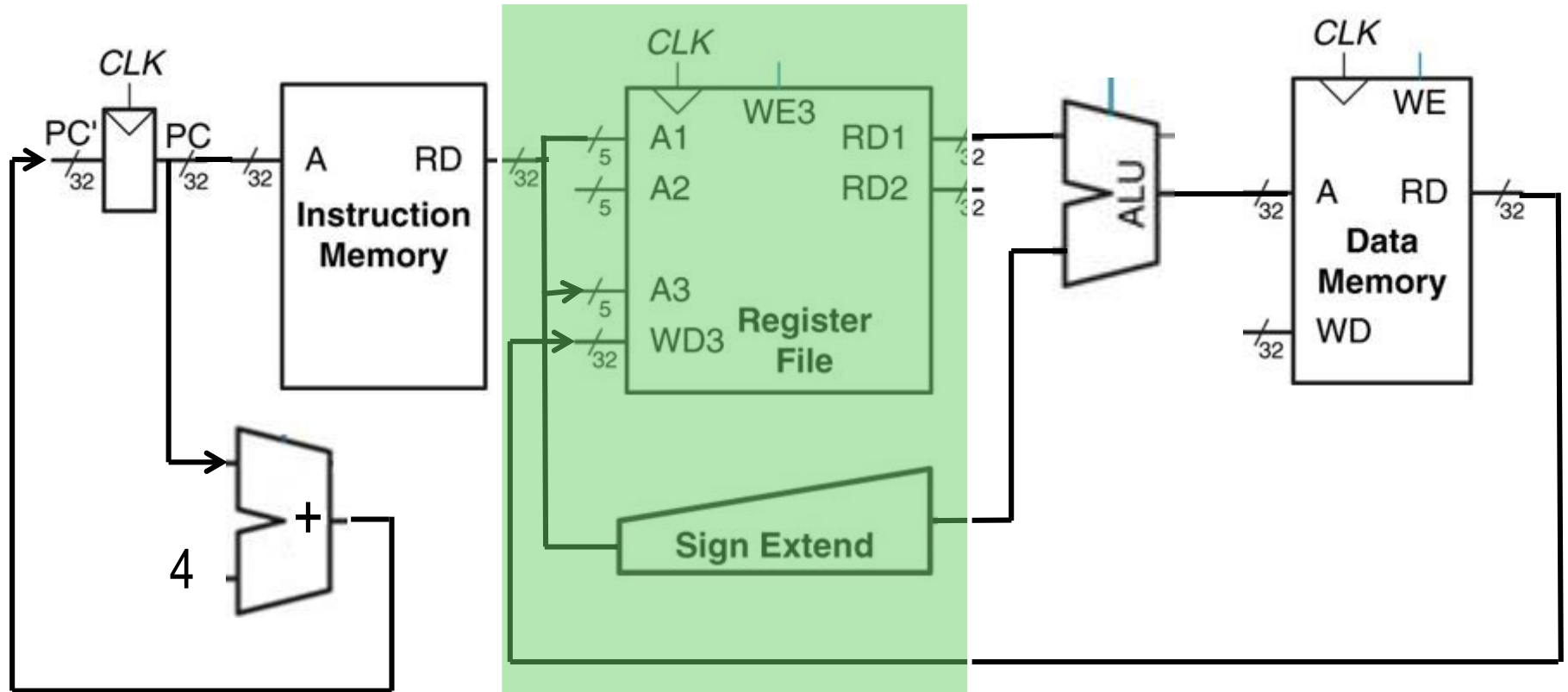


# Execute

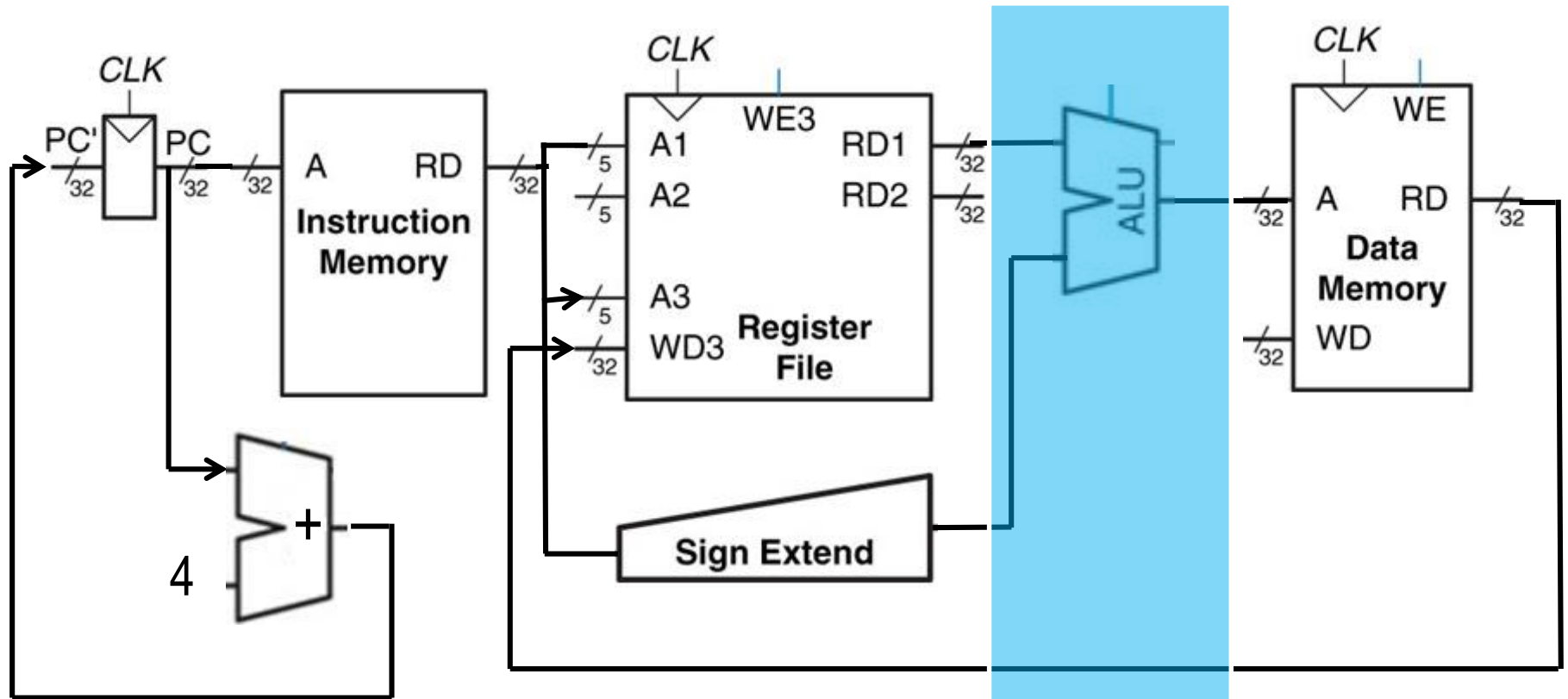


# Memory Access

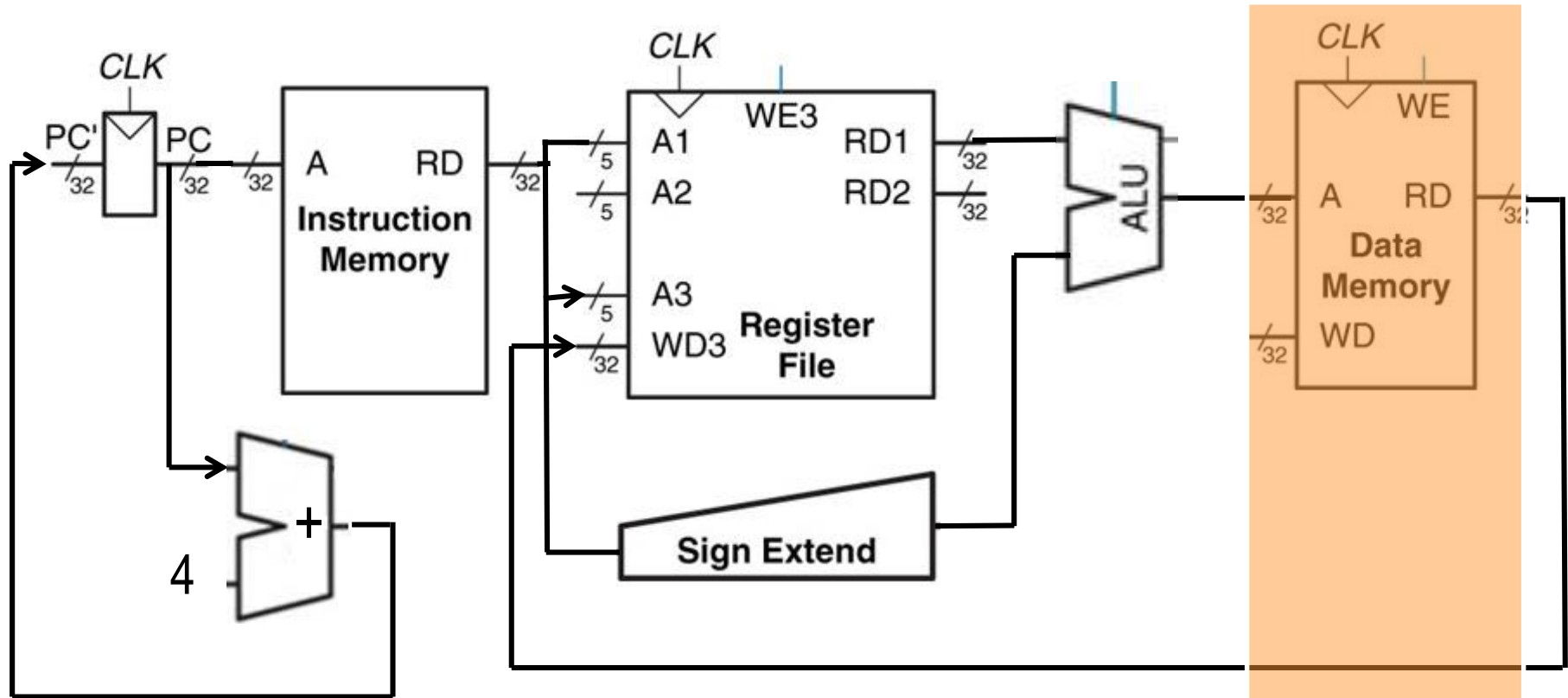

# Write Back to Register-File

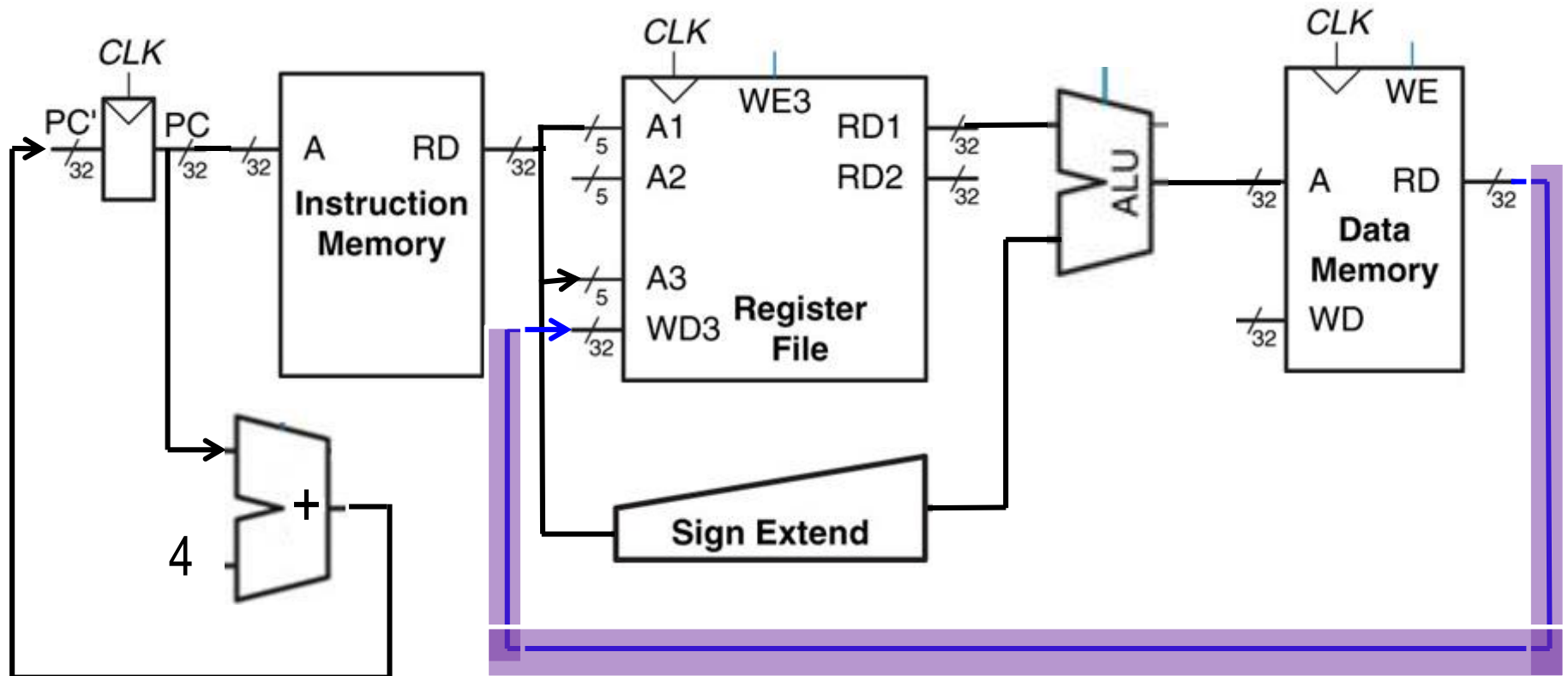


# Microarchitecture: Another view

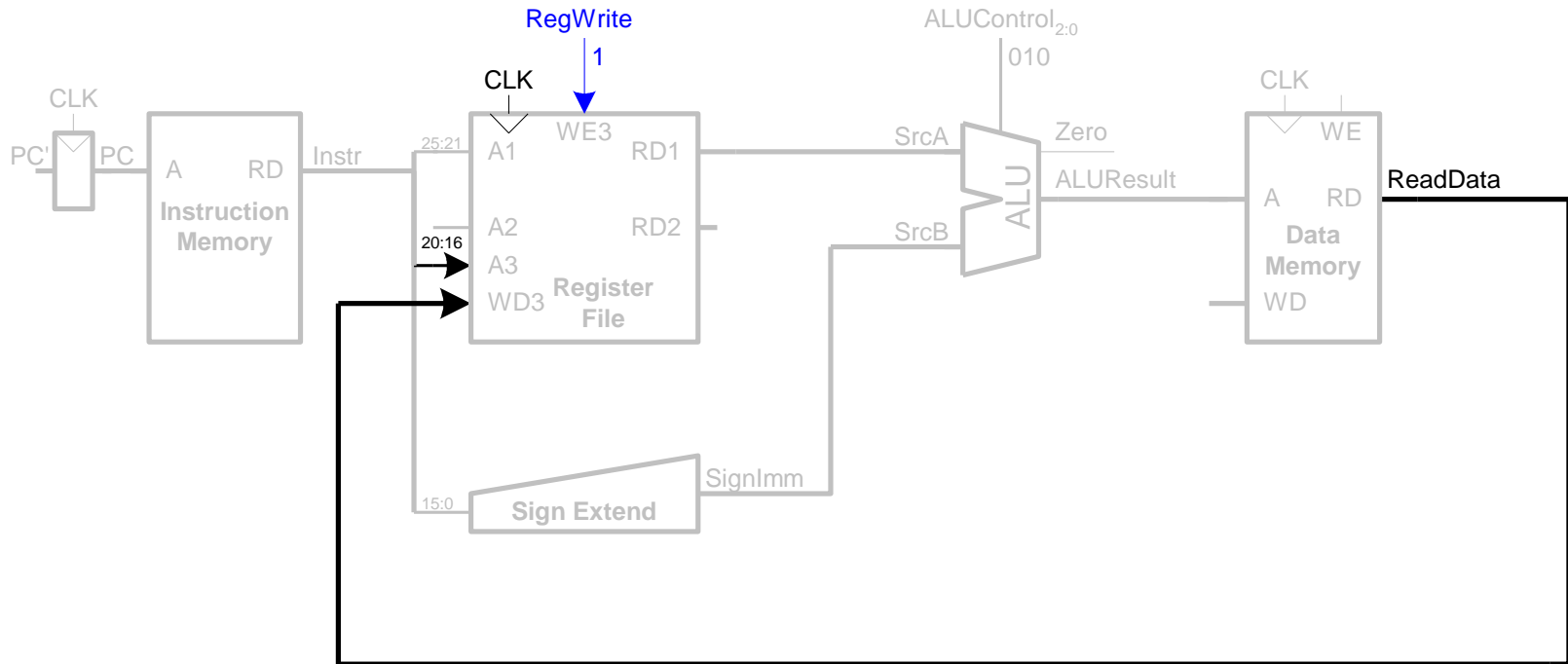


**lw** **rt,rs, imm16**
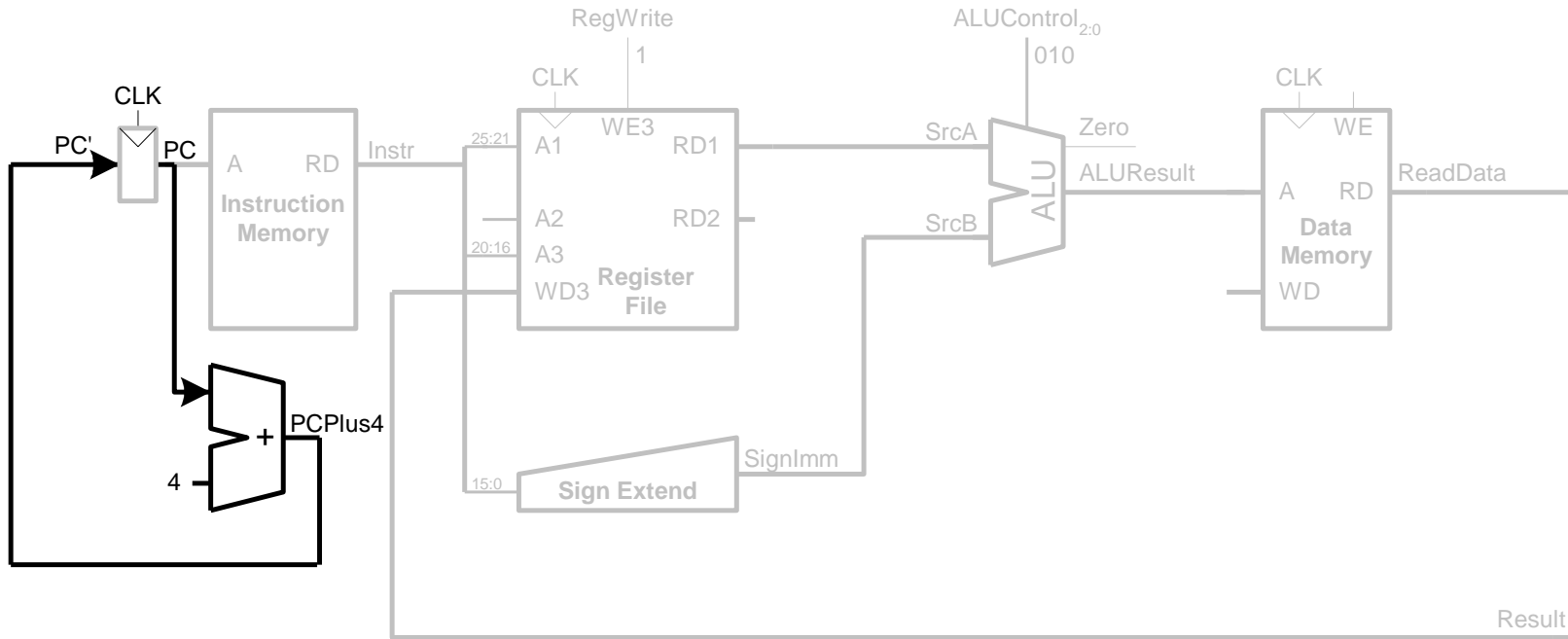
# Next (second) instruction; PC increment




# Write data in **rt** to memory

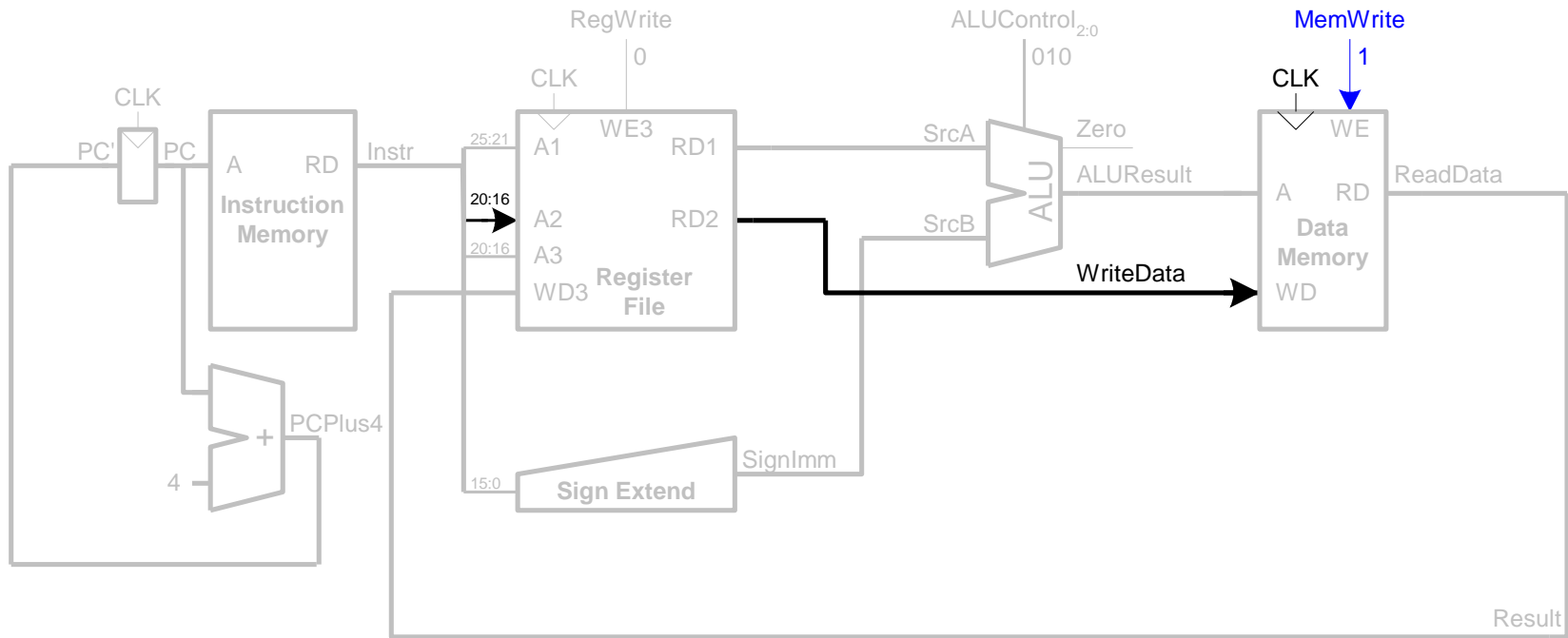

**sw** **rt**,**rs**, **imm16**

# (R-type) instructions

 

**add** rd, rs, rt

#  $r[d] = r[s] + r[t]$


**sub** rd, rs, rt

#  $r[d] = r[s] - r[t]$



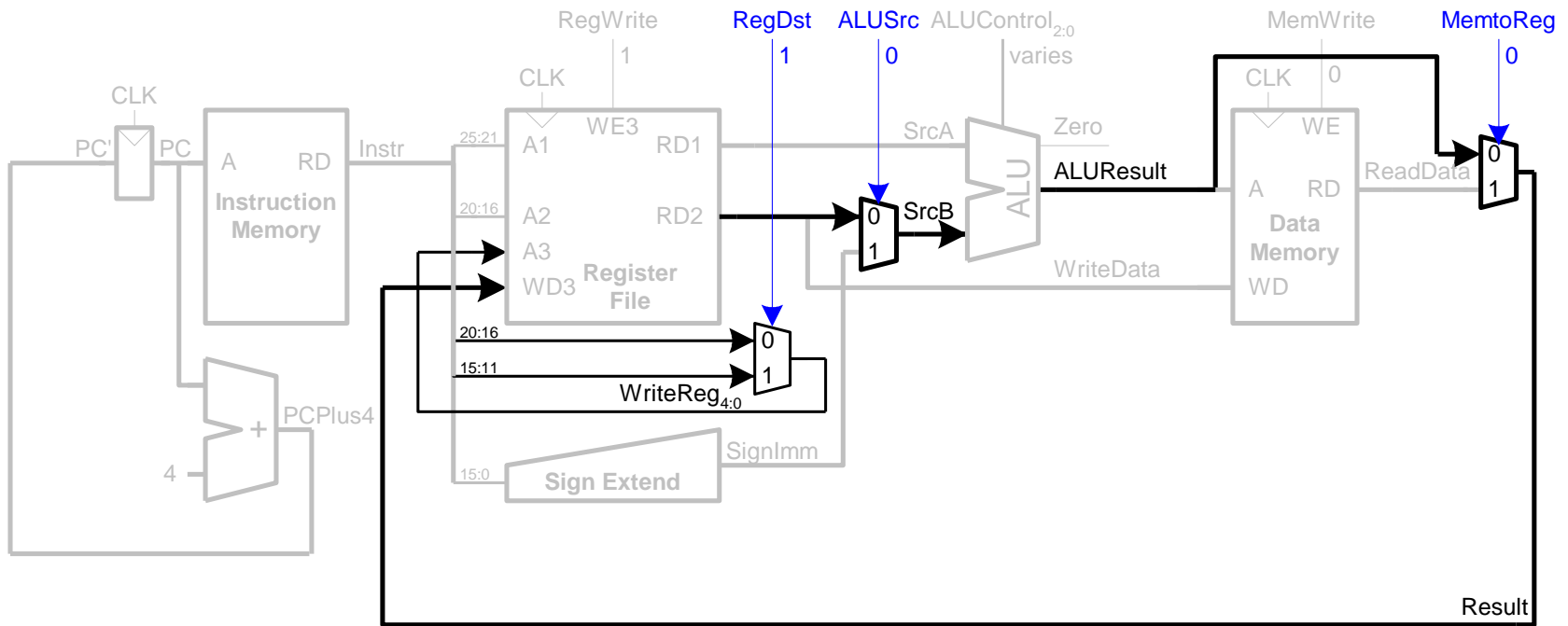
# Datapath (R-type): add

- Read from **rs** and **rt**
- Write *ALUResult* to register file
- Write to **rd** (instead of **rt**)



# (J-type) instructions

 


**beq** *rs*, *rt*, *imm16*      # if \$rs = \$rt, \$pc = imm16

Means the next instruction is at the address specified by label (imm16)

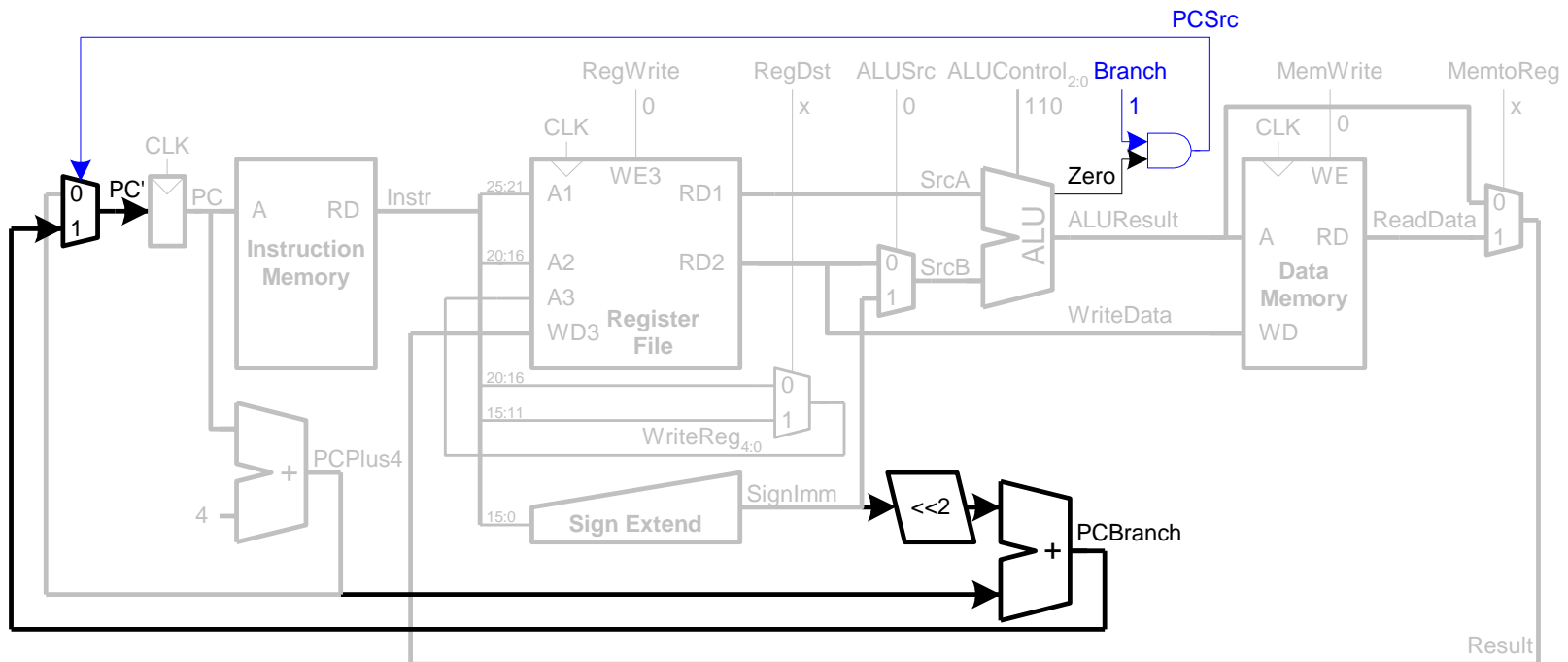
# Datapath (J-type): **beq**

- Determine whether values in **rs** and **rt** are equal
- Calculate branch target address (BTA):

$$\text{BTA} = (\text{sign-extended immediate} \ll 2) + (\text{PC}+4)$$



# Single-Cycle Processor

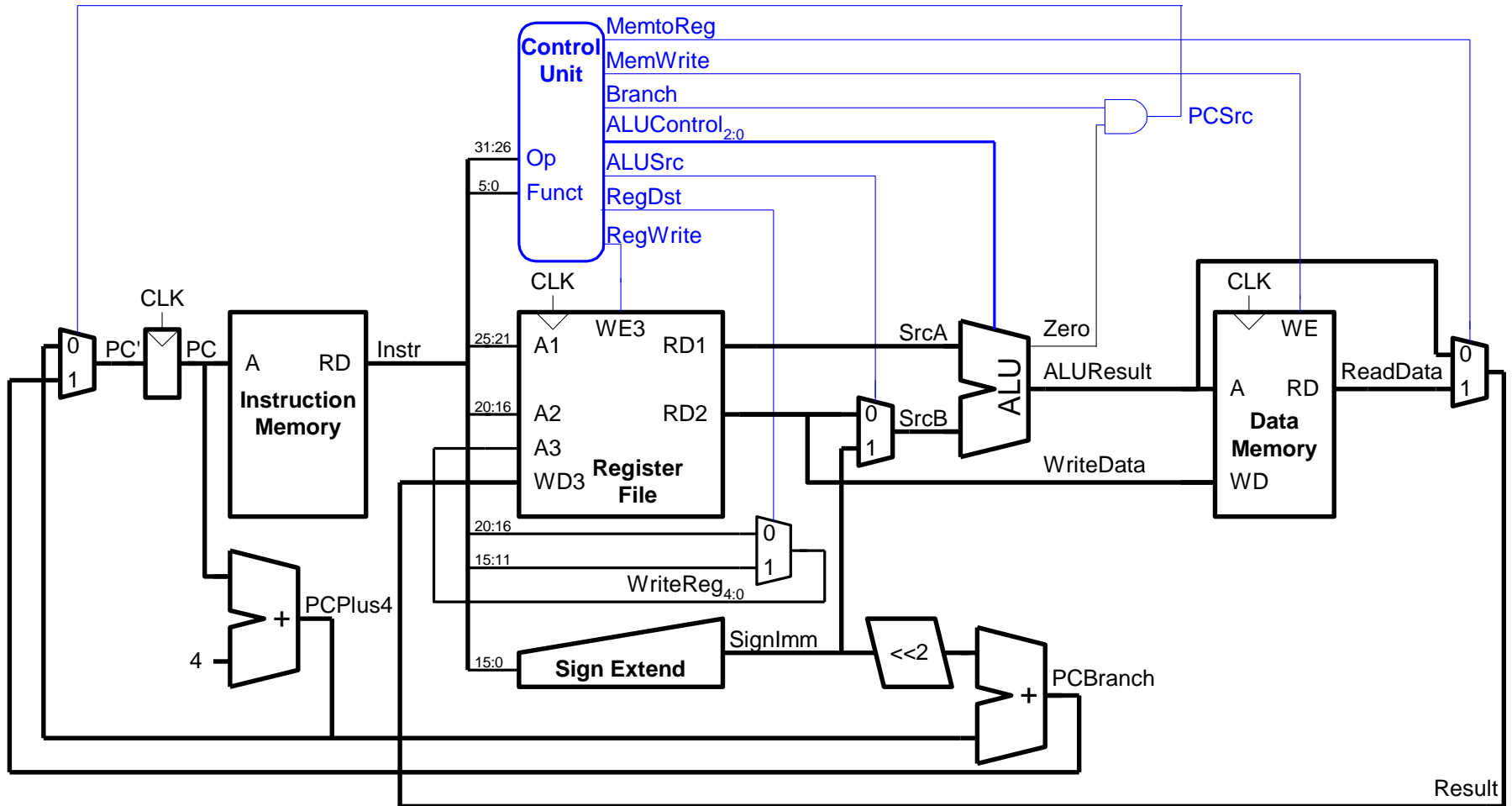

# MIPS is a **Load/Store** Architecture

---

- Since the MIPS is a **Load/Store** architecture, all instructions except **Load and Store** get their operands from CPU registers and store their result in a CPU register
- Hence, the instruction cycle for all instructions except, load and store, is somewhat simpler. Therefore ... it is easier ...
  - To implement (hardware)
  - To understand Computer Assembly/Architecture
  - To educate.

THE END









